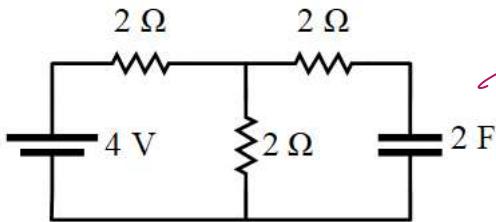


# End Semester Examination

End Sem Exam for EE113

1. 1. What is the time constant of this circuit? (1 mark)



Marks: 1  
Type: IMAGE\_ANSWER\_TYPE


$$R_{th} = 2 \parallel 2 = 1 \Omega$$
$$C = 2 F$$
$$\Rightarrow \tau = R_C = 6 s$$

Rubrics:

Comments:

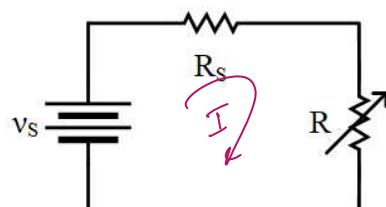2. 2. For the circuit shown below write the expression for power dissipated in 'R' as a function of supply voltage  $v_s$ ,  $R_s$  and  $R$  (0.5 mark)

- At what value of 'R' power supplied by the source is maximum? if  $v_s=10 V$  and  $R_s=10 \Omega$  what is the value of this power? (0.5 mark)
- Instead if  $R=5 \Omega$  and ' $R_s$ ' is variable, what is its value for which power transferred to 'R' is maximum? (1 mark)



Marks: 2  
Type: IMAGE\_ANSWER\_TYPE

$$P_R = I^2 R = \left(\frac{v_s}{R_s + R}\right)^2 \cdot R = \frac{v_s^2 \cdot R}{(R_s + R)^2}$$

(a)  $P_{source} = \left(\frac{v_s}{R_s + R}\right)^2 = \left(\frac{v_s}{R_s + 0}\right)^2$

maximum when  $R = 0$ ,

$$P_{source} = \left(\frac{10}{10}\right)^2 = 1 W$$

(b)  $P_R = \left(\frac{v_s}{R_s + R}\right)^2 \cdot R = \left(\frac{v_s}{R_s + 5}\right)^2 \cdot 5$

This is maximum when  $R_s = 0$

Rubrics:


Comments:

3. Determine the current flowing through the voltage source of this circuit. (3 mark)

Marks: 3

*Number of ways to solve this problem:*

Type: IMAGE\_ANSWER\_TYPE

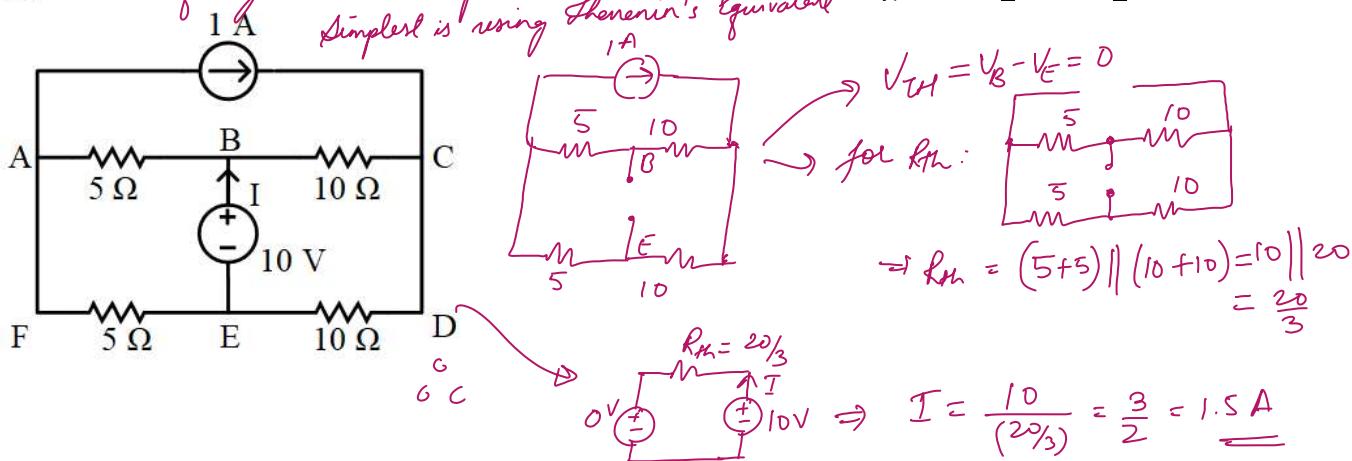


Rubrics:

Comments:

4. Determine the value of  $i_B$  (in  $\mu\text{A}$ ) and  $i_C$  (in mA). Assume  $V_{BE}=0.7$  V (3 mark)


Marks: 3

Type: IMAGE\_ANSWER\_TYPE

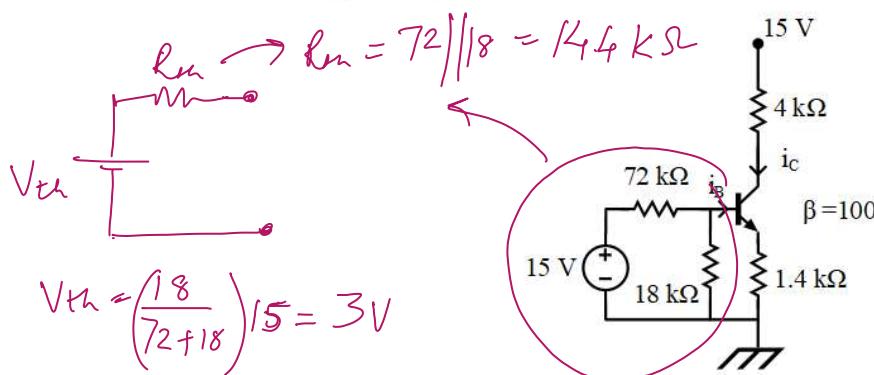

Rubrics:

Comments:

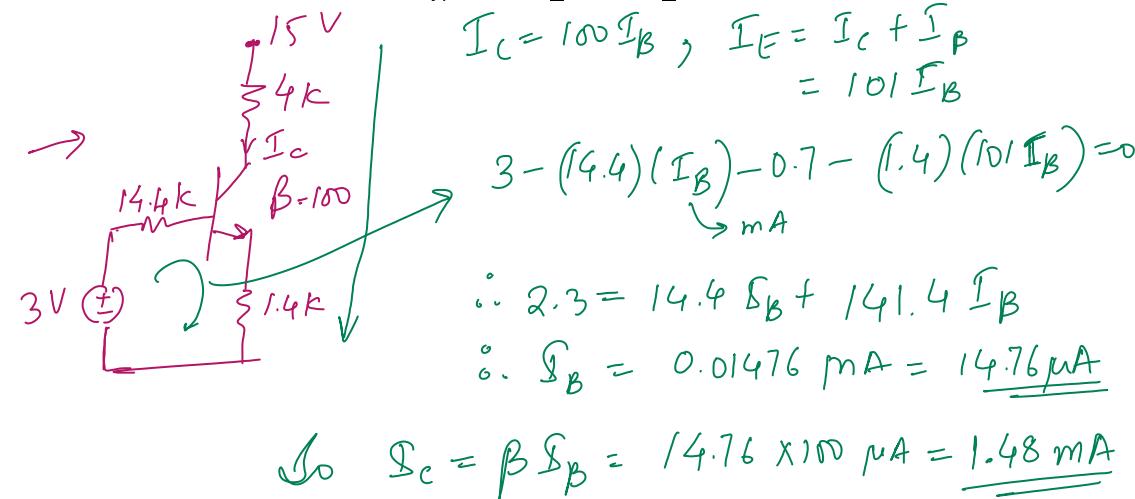


5.

5. Assume that OP-AMP in the circuit is working in the linear range

Marks: 2

- Obtain  $V_o$  in terms of  $v_s$ . (1 mark)
- Obtain  $i_L$ . (1 mark)

Type: IMAGE\_ANSWER\_TYPE

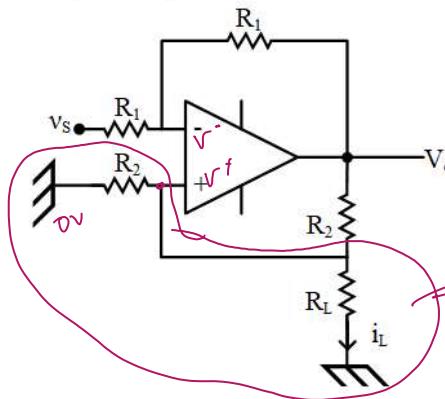

$$\frac{V_s - v^-}{R_1} = \frac{v^- - V_o}{R_2} \Rightarrow V_o = 2v^- - V_s \quad \text{--- ①}$$

These two are in parallel  $\Rightarrow R_{eq} = \frac{R_2 \cdot R_L}{R_2 + R_L}$

using ① and ② and

$$v^- = v^+ \Rightarrow V_o = 2 \left( \frac{R_L}{R_{eq} + R_L} \right) V_o - V_s \quad \text{--- ②}$$

$$\therefore V_o \left( 1 - 2 \frac{R_L}{R_{eq} + R_L} \right) = -V_s$$

$$\therefore V_o \left( \frac{R_L - R_{eq}}{R_{eq} + R_L} \right) = -V_s$$

$$\Rightarrow V_o = - \left( \frac{R_{eq} + R_L}{R_L - R_{eq}} \right) V_s$$

Rubrics:

Comments:

6.

$$i_L = \frac{v^+}{R_L} = \frac{R_{eq} \cdot V_o}{(R_{eq} + R_2)} \quad \text{---}$$

6. Stepper motor (rotates in steps) has 4 coils. For motor to rotate properly coil 1 and 2 must always be in opposite states, so are coils 3 and 4 (If coil 1 is ON, coil 2 is OFF). It is desired to control this motor using 2-bit synchronous counter. For clockwise rotation the required sequences are 11, 10, 00 & 01, and for counter clockwise rotation it is 11, 01, 00 & 10. Direction of rotation can be reversed using a control bit D (D=0 for clockwise and D=1 for counter-clockwise rotation)

Bit A (given in table below) is used to turn ON/OFF coil 1 and 2 while B is used to turn ON/OFF coil 3 and 4.

Design the synchronous counter. (5 mark)


Present States			Next State		$J_B$	$K_B$	$J_A$	$K_A$
D	B	A	B	A	O	x	1	x
0	0	0	O	1	O	x	1	x
0	0	1	1	1	1	x	x	0
0	1	0	O	O	x	1	0	x
0	1	1	1	O	x	0	x	1
<hr/>			1	O	1	x	0	x
1	0	1	O	O	0	x	x	1
1	1	0	1	1	x	0	1	x
1	1	1	O	1	x	1	x	0

## Rubrics:

Draw the k-map for the above table


## **Comments:**

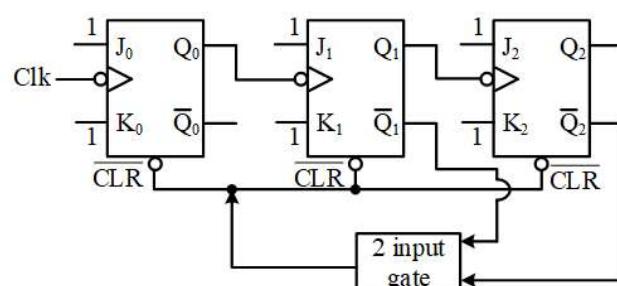7. In the modulo-6 ripple counter shown in figure the output through 2-input gate is used to clear the J-K flip-flop. Name this 2 input gate. Assume J=1 and K=1 for all Flip-Flops (**1 mark**)



$$\begin{array}{ccc} \overline{\mathbb{Q}}_2 & \overline{\mathbb{Q}}_1 & \overline{\mathbb{C}\mathbb{L}\mathbb{R}} \\ | & | & | \\ | & 0 & | \\ 0 & 1 & | \\ 0 & 0 & 0 \end{array}$$

Marks: 5			
Type: IMAGE_ANSWER_TYPE			
$J_B = D \oplus A$	$K_B = \overline{D} \oplus A$	$J_A = D \oplus B$	$K_A = D \oplus \overline{B}$

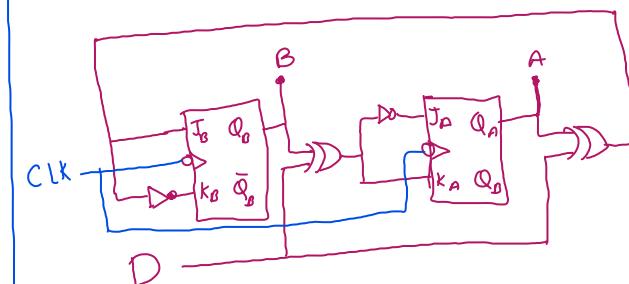


Marks: 1  
Type: IMAGE\_ANSWER\_TYPE

Modulo 6 means once the state reaches 110 it is reset to 000. Also the J-K FF's are active low hence when the O/P of 2-IP gate is 0 it will be reset.

$\alpha, \alpha_1, \alpha_2$

110

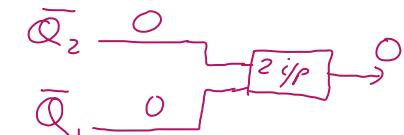A hand-drawn diagram showing a central vertical line with three horizontal branches extending to the right. The top branch is labeled with the Greek letter  $\alpha$ , the middle branch with  $\beta$ , and the bottom branch with  $\gamma$ .



$\therefore$  2 i/p gate is OR gate


**Rubrics:**

**Comments:**

- 
8. 8. Determine the output voltage  $V_o$  of a 4 bit DAC shown below. (3 marks)

Marks: 3

Type: IMAGE\_ANSWER\_TYPE

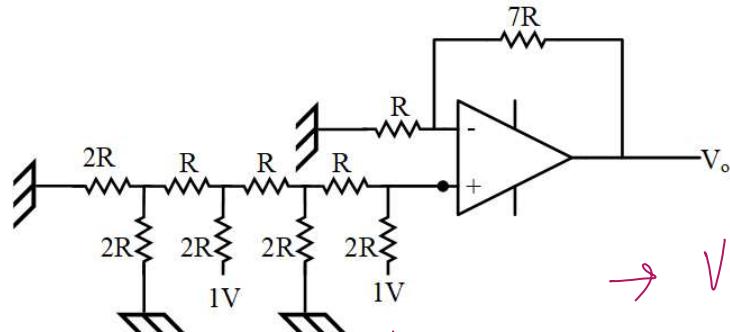

$$\rightarrow V_o = \left( \frac{1}{8} + \frac{1}{2} \right) \times 8 = \frac{5}{8} \times 8 = 5V$$

**Rubrics:** Eq..


$$\frac{1}{8}V$$

$$\frac{1}{2}V$$

**Comments:**

- 
- 9.

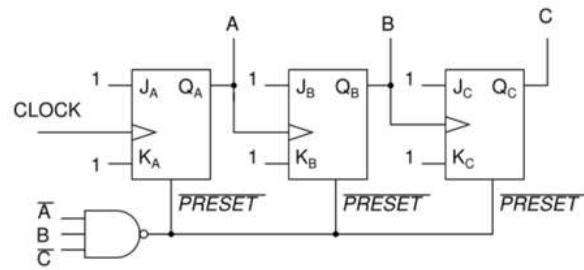9. The circuit diagram of a Mod-N Ripple counter is shown below. The counter uses positive edge triggered JK flip flops. The JK flip-flops also have active-low  $\overline{PRESET}$  inputs, i.e. when the  $\overline{PRESET} = '0'$ , the Q output of the corresponding JK flip-flop will be '1' irrespective of the Clock.



**Answer the following:**

- a) Write the sequence of stable states (CBA) of the above counter. You may assume the initial state (CBA) of the counter to be '000'. Based on the sequence of stable states, state the value of N of this Mod-N counter, where N is the number of stable states. **(2 mark)**
  - b) Sketch the A, B, and C outputs of the Ripple counter with respect to the Clock for at least 10 Clock periods. **(3 mark)**

$$\begin{aligned}
 x(t) &= 1 \quad \text{for } t \in \left[-\frac{1}{2}, \frac{1}{2}\right] \\
 \langle x(t), \exp(j 2\pi f t) \rangle &= \int_{-\frac{1}{2}}^{\frac{1}{2}} x(t) \exp(-j 2\pi f t) dt \\
 &= \left[ \frac{e^{-j 2\pi f t}}{-j 2\pi f} \right]_{-\frac{1}{2}}^{\frac{1}{2}} = \frac{\sin(2\pi f)_2}{\pi f}
 \end{aligned}$$

Marks: 5

Type: IMAGE ANSWER TYPE

(Explanation - This is a Ripple counter using +ve edge-triggered JK flip-flops, with the QA output connected as Clock of Flip-flop B, and QB output connected as the Clock input of the C flip-flop. This will be a down counter).

- a) Sequence of states (CBA) will be: 111, 110, 101, 100, 011, 111,... Value of N: 5

**(it is a mod-5 counter)** (Marks: 2)


- ### b) Clock periods.

(Note: It is ok, even if the glitch in waveform A is not shown. Students were asked to start from CBA: 000. So, they should start from '000' and show 10 clock

(Marks: 3)

(Total Marks : 10)

)

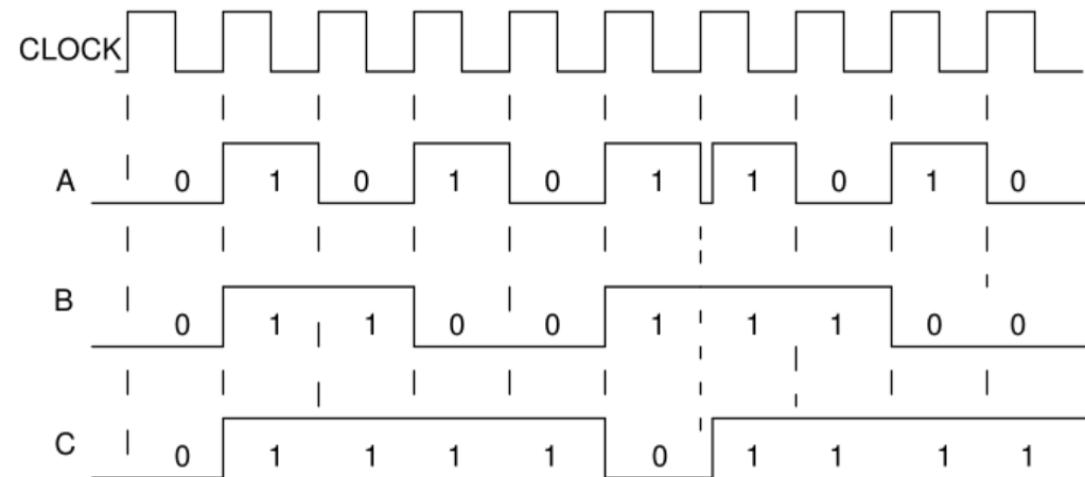


Marks: 5

Type: IMAGE ANSWER TYPE

10. The frequency content of a signal  $x(t)$  at a frequency of  $f$  Hz can be computed as  $X(f) = \langle x(t), \exp(j 2 \pi f t) \rangle$ . For the signal  $x(t) = 1$  in  $-0.5 \leq t \leq 0.5$  and zero everywhere else,, find the set of frequencies at which  $-X(f)$  (i.e. negative of  $X(f)$ ) is the maximum. (5 mark)

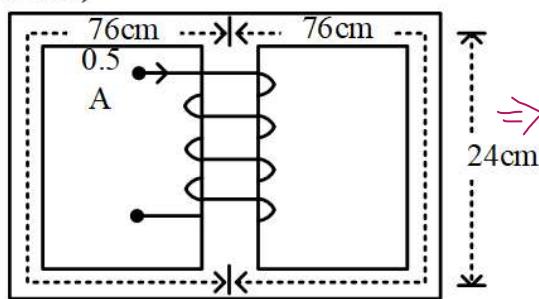11. In the magnetic circuit shown in figure, the cross sectional area of the central limb is  $12 \text{ cm}^2$  and the cross sectional area of rest of the core is  $6 \text{ cm}^2$ . A coil having 750 turns and carrying a current of 0.5 A produces a flux of 5 mwb in the central limb. Find  $\mu_r$  of the core for this operating condition. Also what could be the reason for having the cross sectional area of the central limb at twice the other limbs. (3 mark)



Marks: 3  
Type: IMAGE\_ANSWER\_TYPE

$$\Phi = 5 \text{ mwb} \quad N = 750 \quad I = 0.5 \text{ A} \quad A = 12 \text{ cm}^2$$

$$A_c = 6 \text{ cm}^2$$

$$R_c = \frac{24 \times 10^{-2}}{\mu_r \mu_0 \times 6 \times 10^{-4}} = \frac{1266.67}{\mu_r \mu_0}$$

$$R = \frac{24 \times 10^{-2}}{\mu_r \mu_0 \cdot 12 \times 10^{-4}} = \frac{200}{\mu_r \mu_0}$$

$$\text{MMF}_{AB} = NI - \Phi R = 375 - \frac{200 \times 5}{\mu_r \mu_0}$$

$$\text{Also } \text{MMF}_{AB} = \Phi_1 R_c \quad \text{and } \text{MMF}_{AB} = (\Phi - \Phi_1) R_c \Rightarrow \Phi_1 = \frac{\Phi}{2} = 2.5 \text{ mwb}$$

Rubrics:  $\text{MMF}_{AB} = 375 - \frac{1}{\mu_r \mu_0} = 2.5 \text{ mwb} \Rightarrow$


Comments:

To maintain the same peak flux density throughout the core we keep the central limb C.S.A as double that of rest of the limbs.

12. A DC shunt motor having a field resistance of  $100 \Omega$  and an armature resistance of  $1 \Omega$  is connected to  $200V$  supply and it draws  $10A$  of current from the source. Determine the following:

Marks: 4

Type: IMAGE\_ANSWER\_TYPE

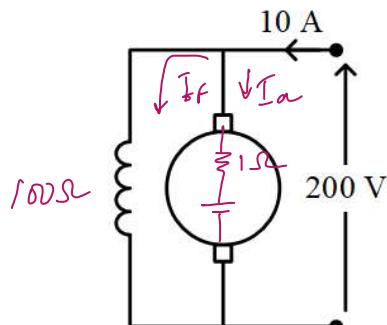

$$I_F = \frac{200}{100} = 2 \text{ A}, \Rightarrow I_a = 10 - 2 = 8 \text{ A}$$

$$I_F^2 \times R_F = 2^2 \times 100 = 400 \text{ W}$$

$$I_a^2 \cdot R_a = 8^2 \times 1 = 64 \text{ W}$$

- Field copper loss in watts. (1 mark)
- Armature copper loss in watts. (1 mark)
- Assume that there are no other losses (except as mentioned in a & b), determine the efficiency of the motor. (2 mark)

$$\eta = \frac{\text{Output}}{\text{Input}} = \frac{\text{Input - losses}}{\text{Input}} = \frac{(200 \times 10) - 464}{200 \times 10} = 0.768 \Rightarrow 76.8\%$$


Rubrics:

Comments:

13. A separately excited generator is supplying a current of 20 A at 200V. The armature resistance is  $0.2 \Omega$

Marks: 3

Type: IMAGE\_ANSWER\_TYPE

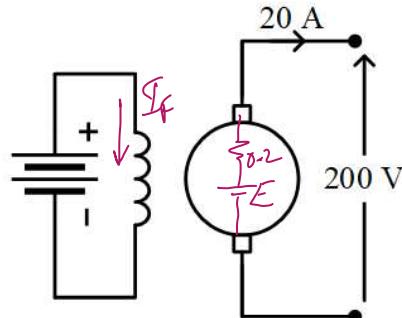

- a. Determine the induced voltage (in volts) in the armature. (1 mark) (204V)

Assume that the same machine is now connected to 100V source (running as motor) and its field current is reduced by 10%. For this operating condition the armature current is 10 A.

- a) Determine its back emf in volts. (1 mark) (98V)  
 b) Ratio of speed of rotation as generator to speed of rotation of motor. (1 mark) (Ans: 1.87)

Rubrics:

Comments:

14. During the lecture You were told that 3 phase induction motor draws 6-8 times the rated current during starting when it is started direct on-line (rated voltage at rated frequency is applied.) State whether this current would either increase or decrease with one-line justification, if it started with

- a) 50% of rated voltage at rated frequency. (1 mark)  
 b) 50% of rated voltage at 50% of rated frequency. (1 mark)

State the effect of increasing the rotor inertia on the duration of this high current and give justification. (1 mark)


NOTE: No credit will be given if the justification is wrong.

Rubrics:

Comments:

$$E = 200 + I_a R_a = 200 + 20 \times 0.2 = 204 \text{ V}$$
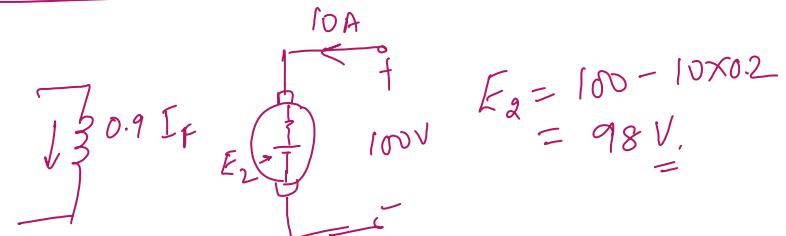
$$E = K \phi_i N_1 \Rightarrow K = \frac{204}{\phi_i N_1} \quad (\text{For this mode})$$



$$\text{Now, } \frac{E_2}{E_1} = \frac{\phi_2 N_2}{\phi_1 N_1} \Rightarrow \frac{N_1}{N_2} = \frac{E_1}{E_2} \times \frac{\phi_2}{\phi_1}$$

$$= \frac{204}{98} \times \frac{0.9 \phi_1}{\phi_1}$$

$$= 1.87$$

Marks: 3

Type: IMAGE\_ANSWER\_TYPE

$$E = 4.44 \cdot \phi_m \cdot N \cdot f$$

decrease because flux intensity is reduced.  
 decrease, although the flux intensity is same, the rate at which the flux cuts the rotor bars is reduced.  $\therefore \frac{d\phi}{dt}$  is small as compared to rated frequency case  
 higher inertia  $\rightarrow$  longer duration.

15. 15. The speed of a 3 phase 400 V, 50Hz induction motor when fed from an inverter is 855 rpm. The corresponding frequency of the stator current is 30 Hz. Therefore

- Number of poles of the motor is 4. (1 mark)
- Speed (in rpm) of the rotor field with respect to stator is 900 rpm. (0.5 mark)
- Speed (in rpm) of the rotor field with respect to rotor is 45 rpm. (0.5 mark)
- Frequency of rotor current is 1.5 (in Hz). (0.5 mark)
- Approximate value of the applied voltage in volts to the stator is 240. (1 mark)
- Percentage slip is 5. (0.5 mark)

Marks: 4

Type: IMAGE\_ANSWER\_TYPE

$$\frac{120 \times 30}{P} \approx 855 \text{ rpm} \Rightarrow P = 4 \text{ poles } (N_s = 900 \text{ rpm})$$

Same as  $N_s = 900 \text{ rpm}$

$$N_s - N = 900 - 855 = 45 \text{ rpm}$$

$$= \frac{8f}{P} = \left( \frac{N_s - N}{N_s} \right) \times 30 = 0.05 \times 30 = 1.5 \text{ Hz}$$

$$V_2 = \frac{V_1 f_2}{f_1} = \frac{400 \times 30}{50} = 240 \text{ V}$$

$$S = \left( \frac{N_s - N}{N_s} \right) = 0.05 \Rightarrow 5\%$$


Rubrics:

Comments:

16. 16. In the circuit shown below  $S_1$  and  $S_2$  are periodically switched ON and OFF.


Marks: 5

Type: IMAGE\_ANSWER\_TYPE

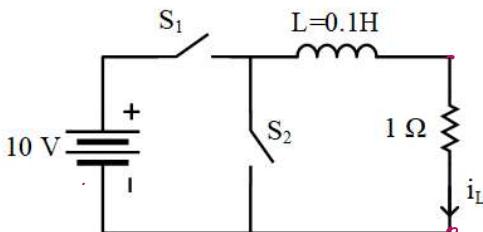

When  $S_1$  is ON,  $S_2$  is OFF, and vice-versa. The period for which  $S_1$  is ON in one cycle is 1 msec while the period for which  $S_2$  is ON is 0.5 msec. Assume that there is always some finite current flowing through L. Determine

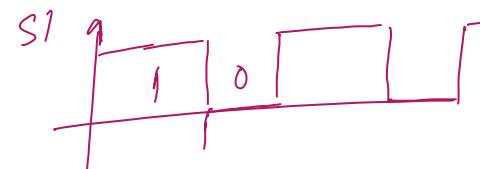- Average value of inductor current. (2 mark)
- Assume that  $S_1$ ,  $S_2$  and L are ideal. Average power (in watts) supplied by the source \_\_\_\_\_. (2 mark)
- Average value of the current supplied by the source \_\_\_\_\_ (in Amp). (1 mark)



$$D = \frac{2}{3}, \therefore V_o = DV_{in} = \frac{20}{3} \text{ V}$$

$$I_{L, \text{average}} = I_{\text{load, average}} = \frac{V_o}{R} = \frac{20}{3} \text{ A}$$

$$P_{\text{loss}} = P_{\text{output}} = I_{\text{load}}^2 \cdot R = \left( \frac{20}{3} \right)^2 \times 1 = \frac{400}{9} \text{ W}$$

$$\text{In, average} \therefore P_{in} = P_{\text{output}} \Rightarrow I_{in} = \frac{P_{\text{output}}}{V_{in}} = \frac{400}{9 \times 10} = \frac{40}{9} \text{ A}$$

Rubrics:

Comments:

17. Figure X shows the DC-DC converter used to operate the DC machine which has negligible  $r_a$ .  $S_1$  and  $S_2$  are controllable switches and they are never turned ON simultaneously. If  $S_1$  is turned ON/OFF ( $S_2$  is permanently OFF) DC-DC converter operates like a buck converter as shown in Figure A. During a particular operating condition back emf of the motor is found to be 8 V and there is always some inductor current flowing. Determine the duty cycle of  $S_1$ . (1 mark)

At this operating condition  $S_1$  is made permanently OFF and  $S_2$  is turned ON/OFF (DC-DC converter now works as boost converter with ' $E_b$ ' as source and 12V as the output as shown in Figure B), Determine the duty cycle of  $S_2$  for this operating condition. (1 mark)

What is the advantage of operating this circuit in this manner? (Explain in one short sentence) (1 mark)

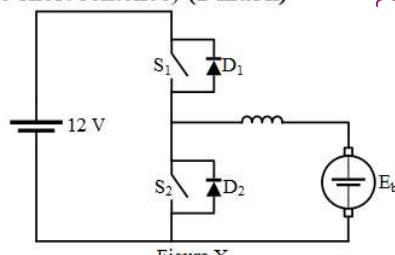


Figure X

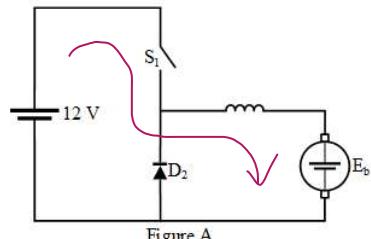


Figure A

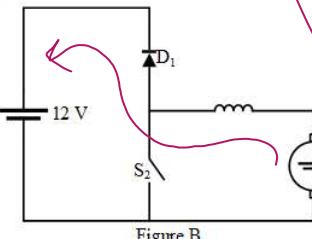


Figure B

Marks: 3

Type: IMAGE\_ANSWER\_TYPE

$$V_{in} = 12V, V_{out} = 8V.$$

$$D = \frac{8}{12} = \frac{2}{3}$$

$E_b = 8V$  (this operating condition only)  
For this mode,  $E_b$  is input and  $V_{in}$  is output voltage

$$\therefore 12 = \frac{8}{(1-D)}$$

$$\Rightarrow 12 - 12D = 8 \Rightarrow D = \frac{4}{12} = \frac{1}{3}$$

The stored energy in the motor inertia  
can be fed back to the source during braking.  
"regenerative braking"

Rubrics:

Comments:

18. Two transformers are designed for same power and voltage ratings.

One is designed for 50Hz and another one is designed for 5000Hz. Comment on the size of these two transformers with justification.

(1 mark)

$E = 4.44 \phi_m \cdot f \cdot T \rightarrow$  as the frequency increases, Number of turns can be reduced! size reduces

$E = 4.44 B_m \cdot A_c \cdot f T \rightarrow$  or core size can be reduced with higher frequency.

50Hz size > 5000Hz Transformer

Marks: 1

Type: IMAGE\_ANSWER\_TYPE

Rubrics:

Comments:

19. The three coils of an induction motor are Coil-A, Coils-B, and Coil-C and these coils are displaced in space by  $120^\circ$ . These three coils are excited by current  $i_a$ ,  $i_b$  &  $i_c$ , respectively. These currents are given by

$$i_a = I_m \sin(\omega_s t), \quad i_b = I_m \sin\left(\omega_s t - \frac{2\pi}{3}\right), \quad \text{and} \quad i_c = I_m \sin\left(\omega_s t - \frac{4\pi}{3}\right),$$

where  $\omega_s = 2\pi f$ . With this, the induction motor rotates in clockwise direction. Suggest a method to change the direction of motor rotation. **(2 marks)**

Rubrics:

Comments:


20. The output of a buck-converter is regulated to 5 V (using some closed-loop control). A fixed resistor of value 4 ohm is connected across the output. The converter is operating at the switching frequency of 50000Hz. Assume that there is some finite current in the inductor all the time and the switches are ideal.

- Sketch and label the waveform of voltage across the inductor when the input voltage is 10 V. **(1 mark)**
- Sketch and label the waveform of voltage across the inductor when the input voltage is 15 V. **(1 mark)**

Rubrics:

Comments:


- 21.

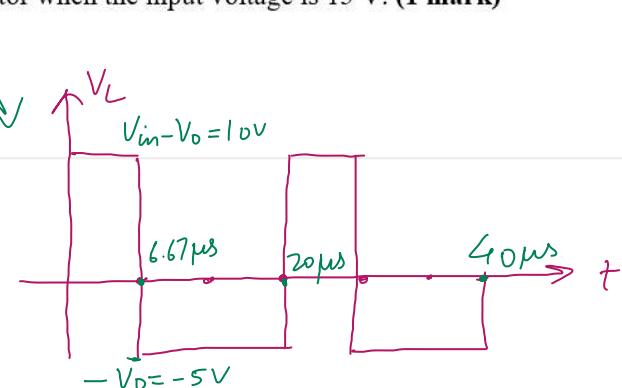

Marks: 2

Type: IMAGE\_ANSWER\_TYPE

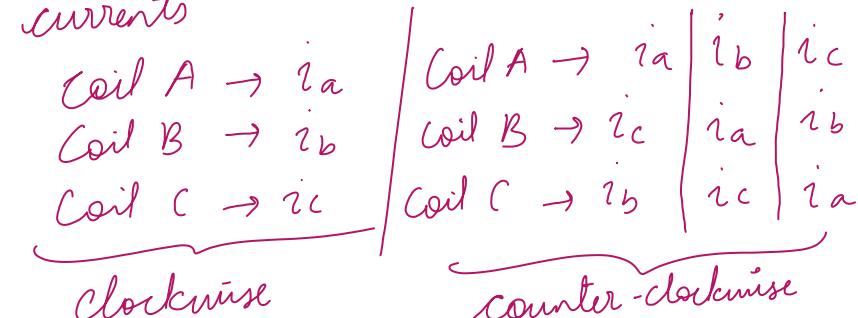We can excite the coils with following currents:




Marks: 2

Type: IMAGE\_ANSWER\_TYPE

$V_o = 5V$  constant (independent of input, as long as input  $> 5V$ )

$$V_{in} = 10V, \quad V_o = 5V \Rightarrow D = 0.5$$
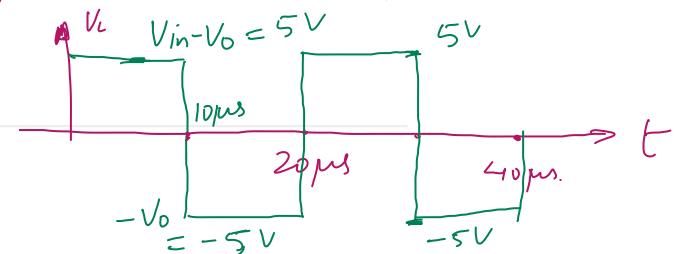
$$f = 50\text{kHz} \rightarrow T = 20\mu\text{s}$$



Consider the system with transfer function

$$G(s) = \frac{3s - 15}{s + 5}.$$

Consider the step response  $y$  for input  $u$  as the unit step input.

The initial value  $y(0+)$  is

Marks: 3

Type: FILL\_IN\_THE\_BLANKS\_TYPE

Ans : 3

22. Consider the system with transfer function

$$G(s) = \frac{2s - 8}{s + 2}.$$

Consider the step response  $y$  for input  $u$  as the unit step input.

The initial value  $y(0+)$  is

Marks: 3

Type: FILL\_IN\_THE\_BLANKS\_TYPE

Ans : 2

23. Consider the system with transfer function

$$G(s) = \frac{s - 18}{s + 2}.$$

Consider the step response  $y$  for input  $u$  as the unit step input.

The final value  $y(\infty)$  equals

Marks: 3

Type: FILL\_IN\_THE\_BLANKS\_TYPE

Ans : -9

24.

Consider the system with transfer function

$$G(s) = \frac{s - 25}{s + 5}.$$

Consider the step response  $y$  for

The final value  $y(\infty)$  equals

Ans : -5


Marks: 3

Type: FILL\_IN\_THE\_BLANKS\_TYPE

25. Consider the graph shown below  
with 4 nodes and 6 edges.

Marks: 5

Type: MULTIPLE\_CHOICE

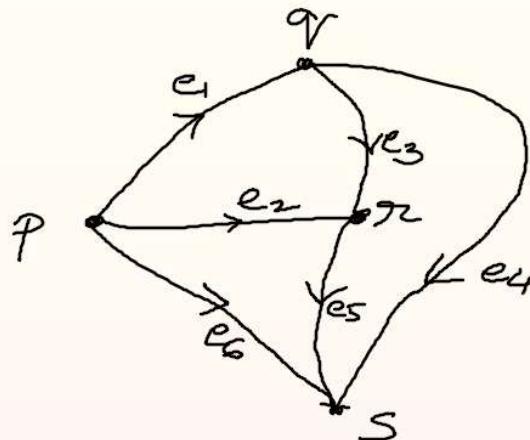

Consider the node-edge incidence matrix  $A$  and  
the loop-edge occurrence matrix  $B$ . No need to explicitly  
construct  $A$  and  $B$ . Let  $v$  be the voltage drops across  
the edges and  $i$  be the currents through the edges.

Pick all the correct statements and only the right ones.  
(No partial marking.)

Options:

- 0) The KCL laws are specified by  $Ai = 0$ .
- 1) The KVL laws are specified by  $Av = 0$ .

2) The KCL laws are specified by  $Bi = 0$ .

3) The KVL laws are specified by  $Bv = 0$ .

4)  $A^T B = 0$

5)  $BA = 0$

26. Consider the inverted pendulum (linearized) model  $\frac{d^2}{dt^2}\theta - \theta = F$ , with  $\theta$  the deviation from the equilibrium point (the upright position)  $P$ , and  $F$  the force used to move the base. Consider a feedback law in which  $F$  is made to depend on  $\theta$  (and/or  $\theta$ 's derivatives) in order to stabilize about  $P$ . Pick all the right statements and only the right ones. (No partial marking.)

Marks: 6

Type: MULTIPLE\_CHOICE

**Options:**

0) The equilibrium position is stable

1) The equilibrium position is unstable

2) A proportional controller can stabilize

3) A proportional+derivative controller can stabilize

4) A proportional controller cannot stabilize

5) A proportional+derivative controller cannot stabilize

The convolution of signals  $3e^{2t}$  and  $5e^{-3t}$   
(for  $t \geq 0$ , and each signal is 0 for  $t < 0$ ) is  
(Show brief intermediate calculations and final answer.)

Marks: 4

Type: IMAGE\_ANSWER\_TYPE

Rubrics:

Comments:

28. The Laplace transform of the unit impulse  $\delta$  equals:  
Pick all the right statements and only the right ones.  
(No partial marking.)

Marks: 2

Type: MULTIPLE\_CHOICE

Options:

0)  1

- 1) the impulse response of the system
- 2) the step response of the system
- 3) undefined
- 4)  $1/s$
- 5)  $s$

29. The convolution of signals  $2e^{3t}$  and  $9e^{-5t}$   
(for  $t \geq 0$ , and each signal is 0 for  $t < 0$ ) is  
(Show brief intermediate calculations and final answer.)

Marks: 4

Type: IMAGE\_ANSWER\_TYPE

Rubrics:

Comments:

27) Convolution of  $3e^{2t}$  &  $5e^{-3t}$   
 $= \mathcal{L}^{-1} \text{ of } \left( \frac{3}{s-2} \times \frac{5}{s+3} \right)$

Solution is similar for  
Q. 2 9 as well.

$$\begin{aligned} \frac{15}{(s-2)(s+3)} &= \frac{3}{s-2} + \frac{-3}{s+3} \\ \mathcal{L}^{-1}(\quad \downarrow \quad) &= 3e^{2t} - 3e^{-3t} \quad \text{for } t \geq 0 \\ &\quad = 0 \quad \text{for } t < 0 \end{aligned}$$

Convolution of  $2e^{3t}$  &  $9e^{-5t}$

$$= \mathcal{L}^{-1} \text{ of } \left( \frac{2}{s-3} \times \frac{9}{s+5} \right)$$

$$\begin{aligned} \frac{18}{(s-3)(s+5)} &= \frac{18/8}{s-3} + \frac{-18/8}{s+5} \\ \mathcal{L}^{-1}(\quad \downarrow \quad) &= \frac{18}{8} e^{3t} - \frac{18}{8} e^{-5t} \quad \text{for } t \geq 0 \\ &\quad = 0 \quad \text{for } t < 0 \end{aligned}$$

No mark deduction for mistake in  
constant. in partial fraction  
expansion


Convolution by brute force (definition) also : no deduction  
of marks.

method :  $\frac{\text{Also}}{50\% \text{ marks}} \rightarrow$  either convolution  
defn  
===== or product of  
laplace transforms.

30. Consider the circuit-graph with 4 nodes and 6 edges

Marks: 2

Type: SINGLE\_CORRECT\_ANSWER

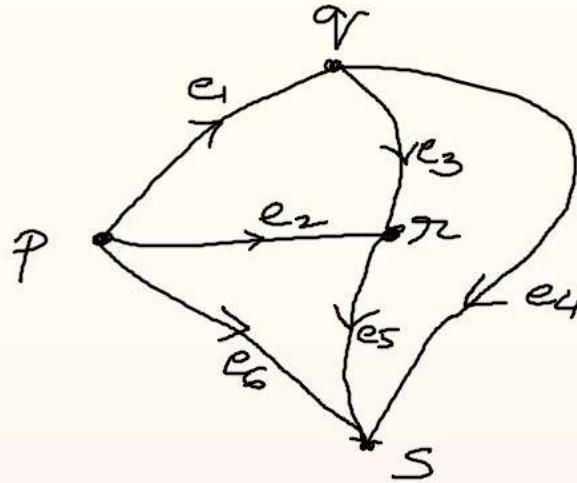

For a link between the Euler formula ( $F - E + V = 2$ )  
with KCL/KVL laws' counts, the polyheron concerned is:

Options:

- 0) Tetrahedron
- 1) Cube
- 2) Triangular prism
- 3) No link with these polyhedra