

Introduction to Electrical Engineering

Course Code: EE 103

Department: Electrical Engineering

Instructor Name: B. G. Fernandes


E-mail id: bgf@ee.iitb.ac.in



Review

Sequential circuits: Output depends on the present set of inputs and also on the past output (Eg: Latches, Flip-flops, Digital Clocks)


S-R Latch

 


Distinct

S	R	output
1	1	No change (Hold)
0	1	$Q = 1$
1	0	$Q = 0$
0	0	invalid

Clocked S-R Flip-Flop:

 


S	R	Clk	Q
0	0	↑	Q(Hold)
1	0	↑	1
0	1	↑	0
1	1	↑	invalid


 


D Flip-Flop: (Data Flip-Flop)

 
One input split into two and used as S and R with a clock.




D	Clk	Q
0	\uparrow	0
1	\uparrow	1

  



J-K Flip-Flop

 

J	K	Clk	Q
0	0		Q _o (Hold)
1	0		1
0	1		0
1	1		toggle

 

Sets each Positive Edge Trigger.

  

- For every second rising edge output will change .
- Frequency of signal at 'Q' is $\frac{1}{2}$ of Clk frequency
 $\Rightarrow \div 2$ Counter



3 bit Asynchronous (Ripple) Counter

(Asynchronous or Ripple)

Why ripple/ Asynchronous?

Q_0 changes at every clock (+ve or -ve rising).
 \Rightarrow J-K in toggle mode.


\Rightarrow Use Q_0 as clock to 2nd Flip-Flop.

Q_1 changes when $Q_0 \downarrow$


\Rightarrow Use Q_1 as clock to 3rd Flip-Flop.

Q_2 changes when $Q_1 \downarrow$

 \Rightarrow Use Q_1 as clock to 3rd Flip-Flop.



*All J and K inputs assumed to be 1.

 

$2^3 =$

8 distinct states \Rightarrow mod-8 counter


$$F = \frac{f_{\text{clock}}}{2^3} \Rightarrow F = \frac{f_0}{2^n} \text{ (General)}$$

Q_2 C	Q_1 B	Q_0 A
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0
1	1	1
0	0	0



3 bit Asynchronous (Ripple) Counter

- ⇒ Only 1st Flip-Flop changes with external clock.
- ⇒ 2nd Flip-Flop waits for 1st Flip-Flop to \downarrow .
- ⇒ This takes a finite delay between external clock \downarrow and output of 1st Flip-Flops to \downarrow (a few ns) known as ⇒ **PROPOGATION DELAY.**
- ⇒ Similarly for 3rd Flip-Flop.
- ⇒ Outputs of all the Flip-Flops do not change simultaneously.
- ⇒ Hence Asynchronous or ripple (Flip-Flops respond one after another).
- ⇒ If clock frequency is high and there are many Flip-Flops (**n-bit counter**) this delay is not acceptable.

 

$\therefore \text{Mod-4} \Rightarrow \text{uses 2 Flip-Flops (00 - 11).}$
 $\text{Mod-16} \Rightarrow \text{uses 4 Flip-Flops (0000 - 1111).}$

How to Design a counter whose number $\neq 2^N$ ($N=1,2,3,\dots$) ?

- \Rightarrow J-K, D, S-R are synchronous Inputs.
- \Rightarrow Their effect on the output is synchronized with its clock input.
- \Rightarrow There are asynchronous inputs also.



PRESET (PRE or $\overline{\text{PRE}}$) \Rightarrow Output= 1

when PRE pin = 1 ($\overline{\text{PRE}}$ = 0); NO MATTER what conditions are present at J, K and Clk.

$\overline{\text{PRE}}$ \Rightarrow is ACTIVE when LOW.

  Similarly CLEAR (CLR or $\overline{\text{CLR}}$) \Rightarrow Output= 0 when CLR pin = 1 ($\overline{\text{CLR}}$ = 0)





PRE ($\overline{\text{PRE}}$)	CLR ($\overline{\text{CLR}}$)	
0(1)	0(1)	Clocked operation
1(0)	0(1)	Q=1
0(1)	1(0)	Q=0




Mod-6 Counter:

Q_2	Q_1	Q_0
C	B	A
0	0	0
0	0	1
0	1	0
0	1	1
1	0	0
1	0	1
1	1	0

6 Stable States

(Temporary)

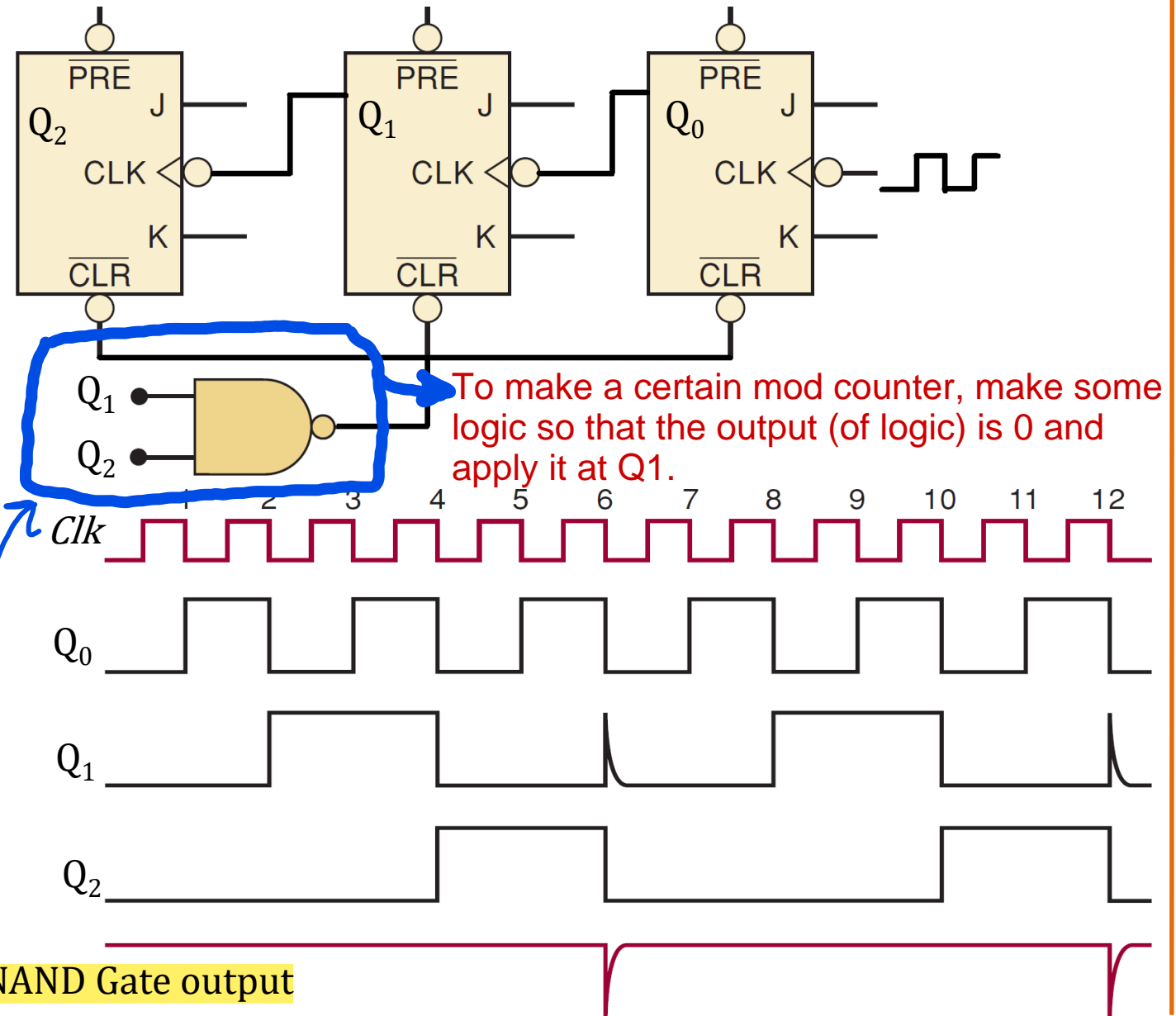Reset all the counts to 000 when this happens.



Asynchronous Down Counter:

They change at alternate edge trigger.

Q_2	Q_1	Q_0
1	1	1
1	1	0
1	0	1
1	0	0
0	1	1
0	1	0
0	0	1
0	0	0
1	1	1


$Q_0 \rightarrow$ changes at every clock pulse (either \uparrow or \downarrow)

$J=K=1$

$Q_1 \rightarrow$ changes when $Q_0 \uparrow$ or $\overline{Q_0} \downarrow$

\therefore Use $\overline{Q_0}$ as clock to 2nd Flip-Flop if it is NGT

 $Q_2 \rightarrow$ changes when $Q_1 \uparrow$ or $\overline{Q_1} \downarrow$



Synchronous Counter (Parallel Counter):

- All Flip-Flops receive clock simultaneously.
- Making $J=K=1$ and apply same clock pulses to all Flip-Flops will not give us the required 'Mod' number or sequence.
- Some means must be used to control when an Flip-Flop should toggle and when it remains unaffected by a clock pulse.



Characteristic Table

J	K	Q_{t+1}
0	0	$Q(\text{Hold})$
1	0	1
0	1	0
1	1	toggle

Learn this to derive

Transition Table

N^{th} state	$(N+1)^{\text{th}}$ state	Inputs Required at	
		J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

this ↗



Design Procedure: Mod-8 Synchronous Counter

Steps to make mod 8 synchronous counter :

1. Determine the desired number of bits (Flip-Flops) and the possible states .

Q_2	Q_1	Q_0				
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				
0	0	0				

Example with 3 bits and corresponding 8 states.



Design Procedure: Mod-8 Synchronous Counter

2. Prepare a table that lists all the present states and their next state.

	Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}			
(0)	0	0	0	0	0	1	(1)		
(1)	0	0	1	0	1	0	(2)		
(2)	0	1	0	0	1	1	(3)		
(3)	0	1	1	1	0	0	(4)		
(4)	1	0	0	1	0	1	(5)		
(5)	1	0	1	1	1	0	(6)		
(6)	1	1	0	1	1	1	(7)		
(7)	1	1	1	0	0	0	(0)		
	0	0	0	0	0	1			

N^{th} state	$(N+1)^{\text{th}}$ state	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



Design Procedure: Mod-8 Synchronous Counter

3. Add two column per Flip-Flop (one for each J and K). There will be six columns for each 'PRESENT' state, indicate the levels requires at each J and K input in order to produce the transition to the 'NEXT' state

Q_2	Q_1	Q_0	Q_{2+}	Q_{1+}	Q_{0+}	J_0	K_0	J_1	K_1	J_2	K_2
0	0	0	0	0	1	1	X	0	X	0	X
0	0	1	0	1	0	X	1	1	X	0	X
0	1	0	0	1	1	1	X	X	0	0	X
0	1	1	1	0	0	X	1	X	1	1	X
1	0	0	1	0	1	1	X	0	X	X	0
1	0	1	1	1	0	X	1	1	X	X	0
1	1	0	1	1	1	1	X	X	0	X	0
1	1	1	0	0	0	X	1	X	1	X	1
0	0	0	0	0	1						

N^{th} state	$(N+1)^{th}$ state	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Now learn this to derive this :(



Design Procedure: Mod-8 Synchronous Counter

4. Design the logic circuit needed to generate the levels required at each J&K input

J_0

Q_2Q_1 Q_0	00	01	11	10
0	1	1	1	1
1	X	X	X	X

$$J_0 = 1 \text{ (or } J_0 = \overline{Q_0} \text{)}$$

J_1

Q_2Q_1 Q_0	00	01	11	10
0	0	X	X	0
1	1	X	X	1

$$J_1 = Q_0$$

J_2

Q_2Q_1 Q_0	00	01	11	10
0	0	0	X	X
1	0	1	X	X

$$J_2 = Q_0Q_1$$

K_0

Q_2Q_1 Q_0	00	01	11	10
0	X	X	X	X
1	1	1	1	1

$$K_0 = 1 \text{ (or } K_0 = Q_0 \text{)}$$

K_1

Q_2Q_1 Q_0	00	01	11	10
0	X	0	0	X
1	X	1	1	X

$$K_1 = Q_0$$


K_2

Q_2Q_1 Q_0	00	01	11	10
0	X	X	0	0
1	X	X	1	0

$$K_2 = Q_0Q_1$$



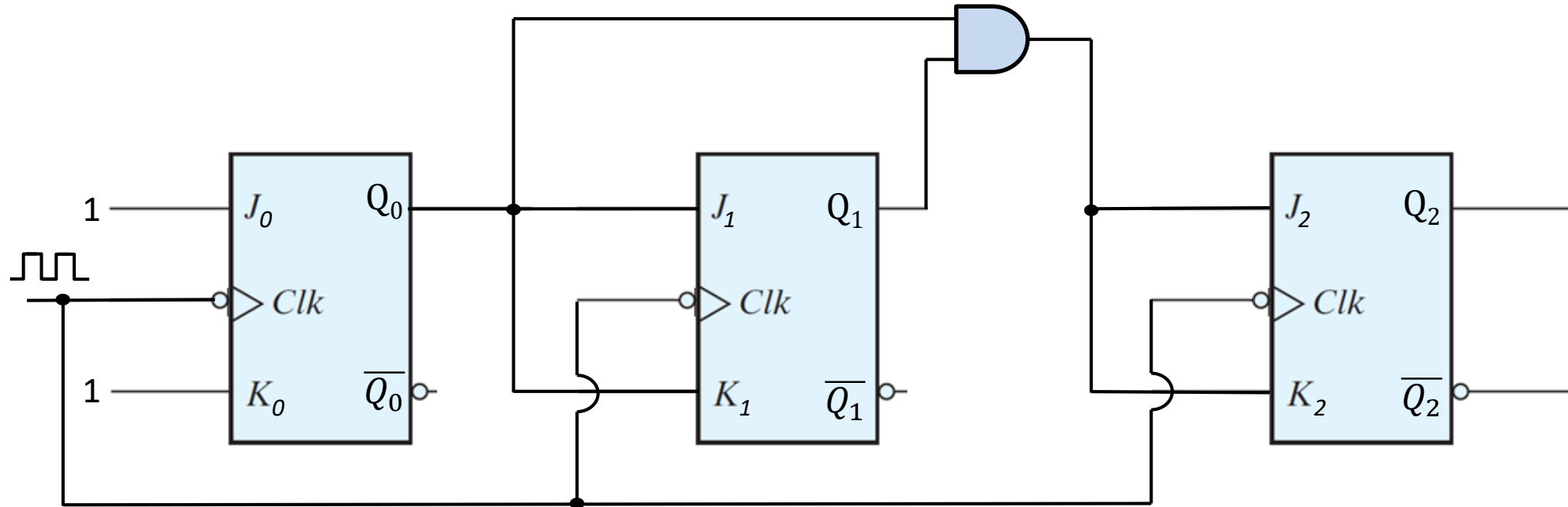Logic Realisation: Mod-8 Synchronous Counter



$$J_0 = 1 \text{ (or } J_0 = \overline{Q_0} \text{)}$$

$$J_1 = Q_0$$

$$J_2 = Q_0 Q_1$$

$$K_0 = 1 \text{ (or } K_0 = Q_0 \text{)}$$

$$K_1 = Q_0$$

$$K_2 = Q_0 Q_1$$

