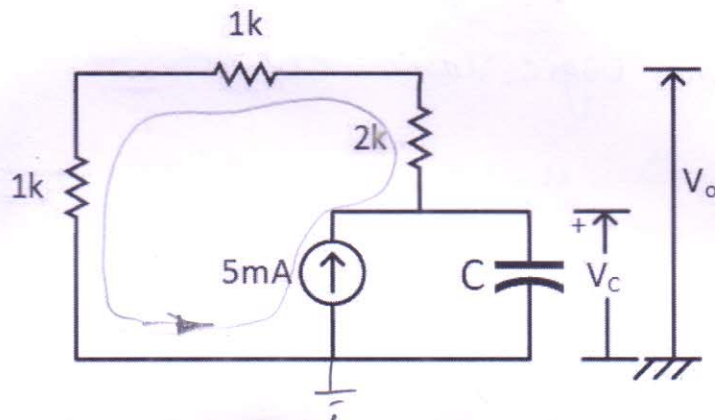


Q.7 For the circuit shown in fig below, determine the steady state voltage across C and V_o .



In steady-state, Capacitor C is fully charged and current of 5mA flows through resistor

$$V_c = (4k \times 5mA) = \underline{20V}$$

$$\begin{aligned} V_o &= V_c - 2 \times 10^3 \times 5 \times 10^{-3} \\ &= 20 - 10 \\ &= \underline{10V} \end{aligned}$$

- ✓ Q.8 A logic design is required for automatic switching ON & OFF of a motor used for pumping water to a water tank. Two micro-switches are fitted on the water tank to indicate water levels. The first one will close when the water level crosses 50% and the second one when it crosses 80%. It is desired to have water level always between these limits. Write a truth table for the above problem and design a simple logic circuit by which the motor can be switched ON/OFF automatically.

P10

Q8. Let S_A & S_B are the microswitches corresponding to the 80% and 50% Levels respectively.

Let us assume that these switches will be closed only when the respective Levels are exceeded.

Let switch closing corresponds to Logic '1'.

A & B are corresponding Logic Variables.

Truth Table

A	B	MOTOR
0	0	1
0	1	1
1	0	X
1	1	0

In 3rd Case, ($A=1, B=0$), Output is don't care, because this condition can never happen


	\bar{A}	A
\bar{B}	1	X
B	1	0

Considering $X \rightarrow 1$


$$\text{Motor} = \bar{A} + \bar{B} \quad \checkmark$$

Considering $X \rightarrow 0$

$$\text{Motor} = \bar{A}$$

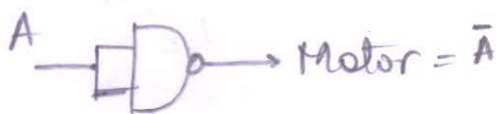

OR

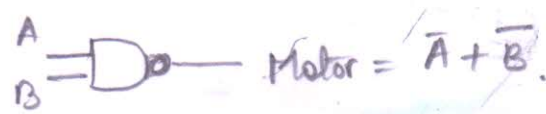

mand greating, Submis. Added in runtime.