

# Lecture 4: Op amp Circuits

EE 103


2023-24/I (Autumn)

Joseph John (j.john@iitb.ac.in, jjohn@ee.iitb.ac.in)


# Problems of BJT based Amplifiers

- Voltage gain depends on the device parameters  
(which in turn depends on temperature and also vary from device to device)
- For example, the gain of a BJT Common-Emitter amplifier is:  
$$-g_m R_C \parallel R_L$$
- Solution:
  - Cascaded amplifiers

# Amplifier Requirements

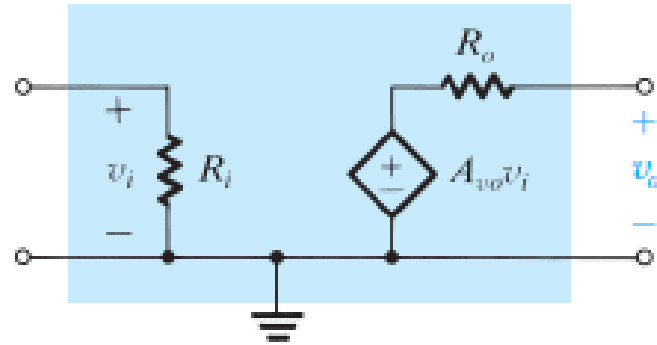


(a)

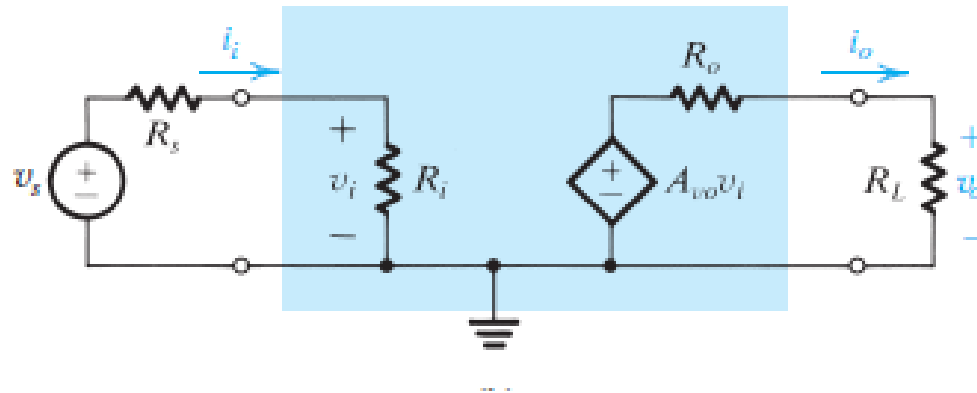

- Input side requirements
  - Input resistance ( $R_i$ ) of the amplifier should be ideally infinite.
- Load requirements
  - Output resistance ( $R_o$ ) of the amplifier should be ideally 0.

# LM 741 Op amp

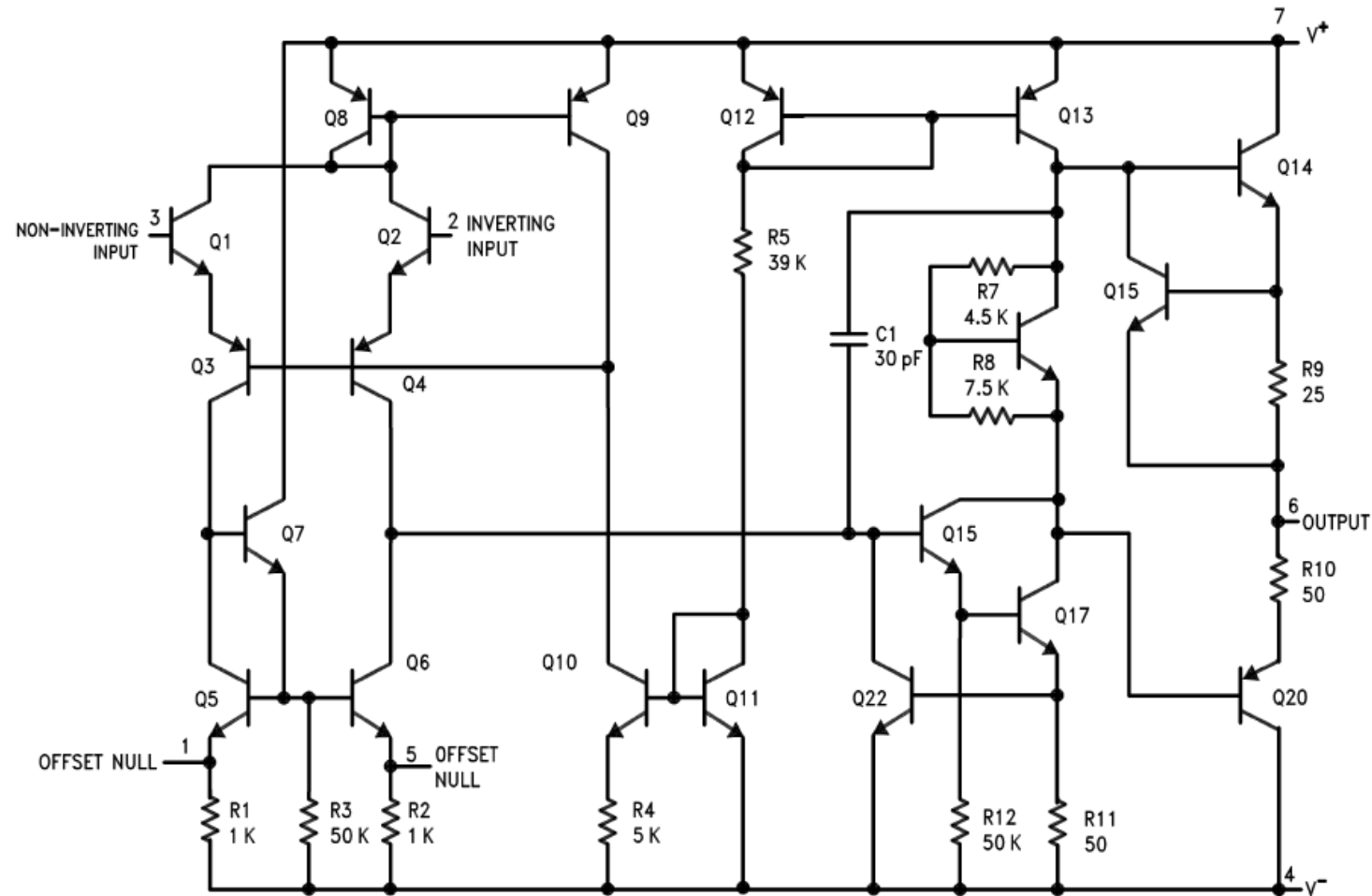

- **Three major blocks:**
  - Input block: gives very high input resistance and also a voltage gain of about 1000.
- A gain clock:
  - gives a voltage gain of about 1000.
- Output stage:
  - Unity voltage gain but very high current gain; also provides short-circuit protection to the output

# 3. Operational Amplifier


## *Operational amplifier (op amp)*

Direct-coupled (dc) high-gain amplifier with differential voltage input & single-ended voltage output.

- Developed for mathematical operations on signal waveforms. It is an electronic circuit with several internal passive & active devices, available as a single-chip device, several op amps on a single chip, or op amps with other circuits on the same chip.
- Main objective: Circuit performance parameters decided by passive components & nearly independent of electronic device parameters.

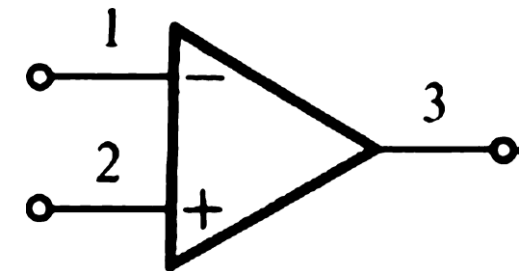
## *Op amp circuit symbol (simplified)*

- Input terminals: 1, 2. Output terminal: 3.
- 3 single-ended ports with the circuit ground (Gnd) as the common terminal (implied, not shown in the symbol).
- Inverting input  $v_{i-}$ : 1-Gnd. Non-inverting input  $v_{i+}$ : 2-Gnd. Output  $v_o$ : 3-Gnd.


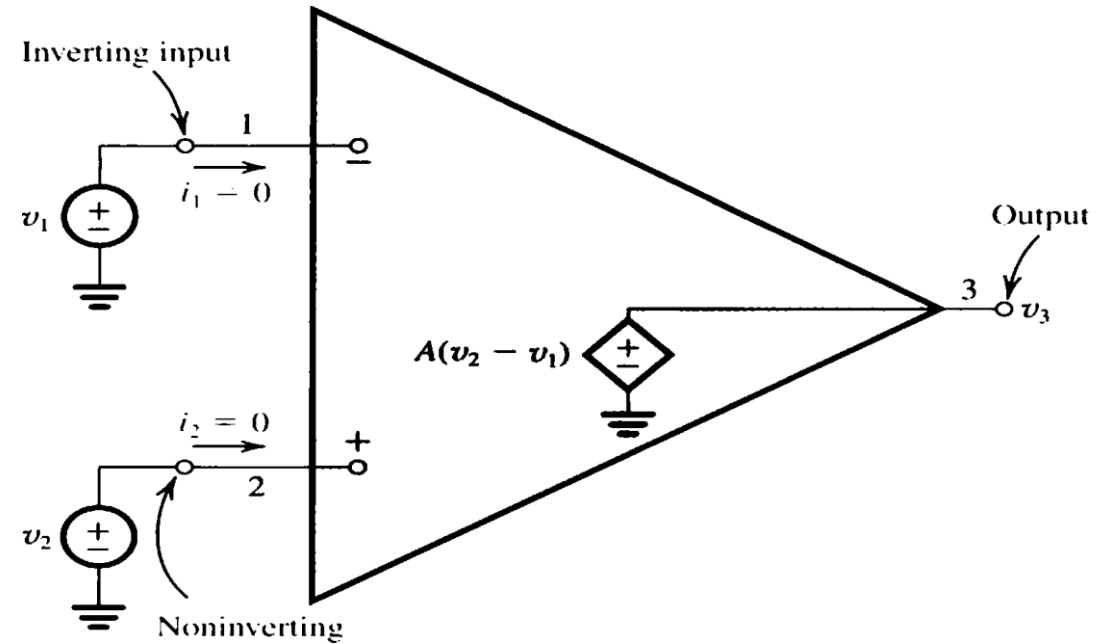
## Input-output relation

- Terminal voltage: voltage between the terminal & Gnd.
- Difference-mode (DM) input  $v_{id} = v_2 - v_1$ .
- Common-mode (CM) input  $v_{ic} = (v_2 + v_1)/2$ .
- Output voltage  $v_3 = A_d v_{id} + A_c v_{ic}$ .
- DM gain:  $A_d$ . CM gain:  $A_c$ .
- Common-mode rejection ratio (CMRR) =  $A_d/A_c$ .



## Ideal op amp

- $A_d \rightarrow \infty$ .  $A_c \rightarrow 0$ .  $v_3 = A_d(v_2 - v_1)$

DM input amplification with no effect of CM input. Finite output voltage obtained with zero DM input.

$$\text{CMRR} = A_d/A_c \rightarrow \infty.$$

- Infinite input resistances for the two inputs (zero input currents) .
- Zero output resistance (output voltage independent of the load current).

## *Op amp in linear operation*


- $v_3 = A_d v_{id}$

For finite output  $v_3$  and  $A_d \rightarrow \infty$ , DM input  $v_{id} = v_3/A_d \rightarrow 0$ .

- Input resistances  $R_{i1}, R_{i2} \rightarrow \infty \Rightarrow$  zero input currents.
- Zero voltage across the input terminals with zero input currents is known as "virtual short" across the input terminals.
- Virtual short condition is very useful in analyzing linear op amp circuits.
- Virtual short is applicable only during linear operation, & the conditions for it have to be satisfied by external circuit & input voltages. Input currents may increase and output may be distorted during nonlinear operation. Input and output voltage limits for linear operation:

CM input:  $V_{CC+} > V_{ICH} > [v_1, v_2] > V_{ICL} > V_{CC-}$ .

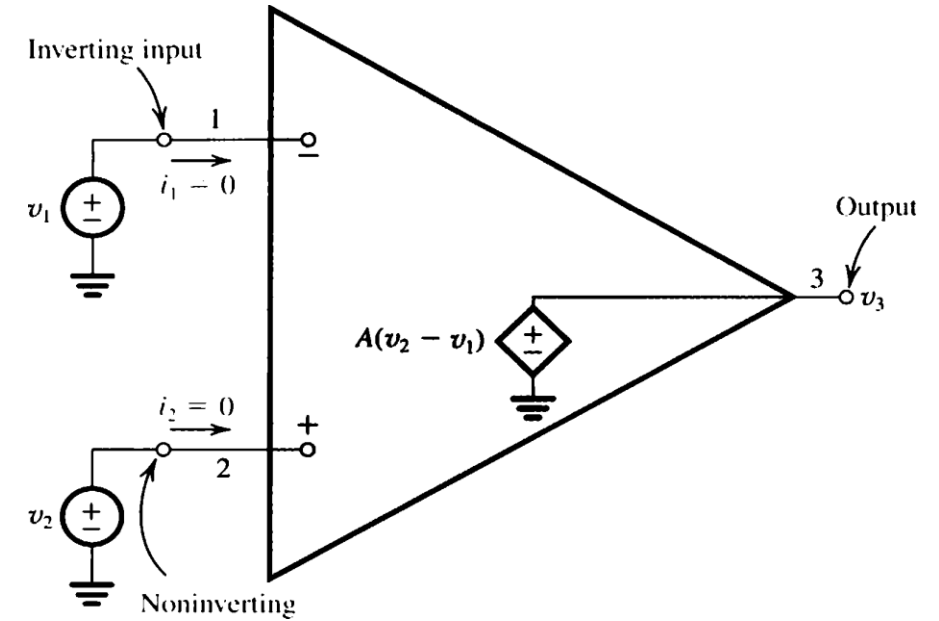Output:  $V_{CC+} > V_{OH} > v_3 > V_{OL} > V_{CC-}$ .



# 4. Linear Circuits

## 4.1. Inverting Amplifier Circuit

$$v_{i+} = 0.$$


Virtual short:  $v_{i-} = v_{i+} = 0$ .  $i_1 = i_2$ .

$$i_2 = i_1 = (v_{in} - v_{i-}) / R_1 = v_{in} / R_1$$

$$v_o = v_{i-} - R_2 i_2 = - (R_2 / R_1) v_{in}$$

Voltage gain:  $A_v = v_o / v_{in} = - R_2 / R_1$ .

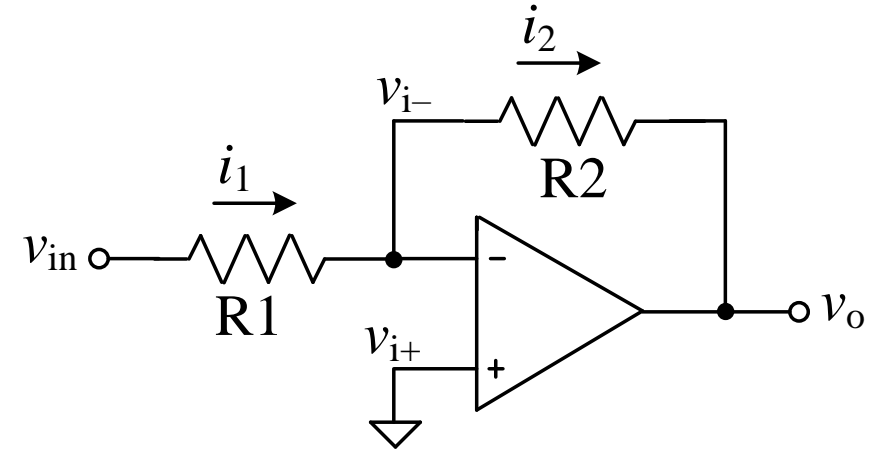Input resistance:  $R_{in} = v_{in} / i_1 = R_1$ .



Circuit operation basis: Negative feedback (visited later), which opposes disturbance. Check the circuit operation with virtual short assumption and a disturbance at the -ve input. If  $v_{i-}$  increases,  $v_o$  decreases,  $i_2$  increases,  $v_{i-}$  decreases, leading to virtual short restoration. If the op-amp input terminals are interchanged, an increase in  $v_{i+}$  will cause further increase leading to virtual short violation.

Current & power gains depend on load resistance (not shown).  $R_{in}$  can be decreased by connecting a resistor between input and ground.

*Application:* Precise inverting gain with low to moderate  $R_{in}$ .

*Example:*  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ .  $R_L = 1 \text{ k}\Omega$ .  $A_v = -10$ ,  $R_{in} = 10 \text{ k}\Omega$ .



## 4.2. Non-inverting Amplifier Circuit

$$V_{i+} = V_{in}$$


Virtual short assumption:  $v_{i-} = v_{i+}$  &  $i_1 = i_2$

$$i_1 = (0 - v_{i-}) / R_1 = -v_{in} / R_1$$

$$v_o = v_{i+} - R_2 i_2 = (1 + R_2 / R_1) v_{in}$$

Voltage gain:  $A_v = v_o / v_{in} = 1 + R_2 / R_1$

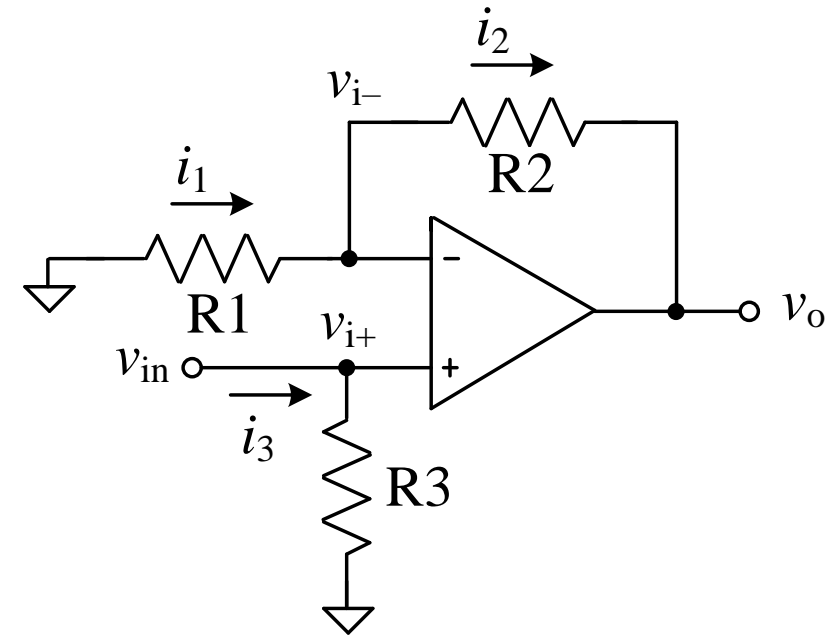Input resistance:  $R_{in} = v_{in} / i_3 = R_3$



$R_3$  is optional & can be selected for the desired  $R_{in}$

Basis for circuit operation: Negative feedback. Check the circuit operation, with virtual short assumption & a disturbance at the -ve input. If  $v_{i-}$  increases,  $v_o$  decreases,  $i_2$  increases,  $v_{i-}$  decreases, leading to virtual short restoration. Next check with the op-amp input terminals interchanged.

*Application:* Precise non-inverting gain with high, moderate, or low  $R_{in}$

Example:  $R_1 = 10 \text{ k}\Omega$ ,  $R_2 = 100 \text{ k}\Omega$ ,  $R_3 = 1 \text{ M}\Omega$ ,  $A_v = 11$ ,  $R_{in} = 1 \text{ M}\Omega$ .


### 4.3. Non-inverting Unity Follower Circuit (Unity Buffer)

It is a special case of non-inverting amplifier with unity voltage gain.

Voltage gain:  $A_v = 1$

Input resistance:  $R_{in} = R_1$

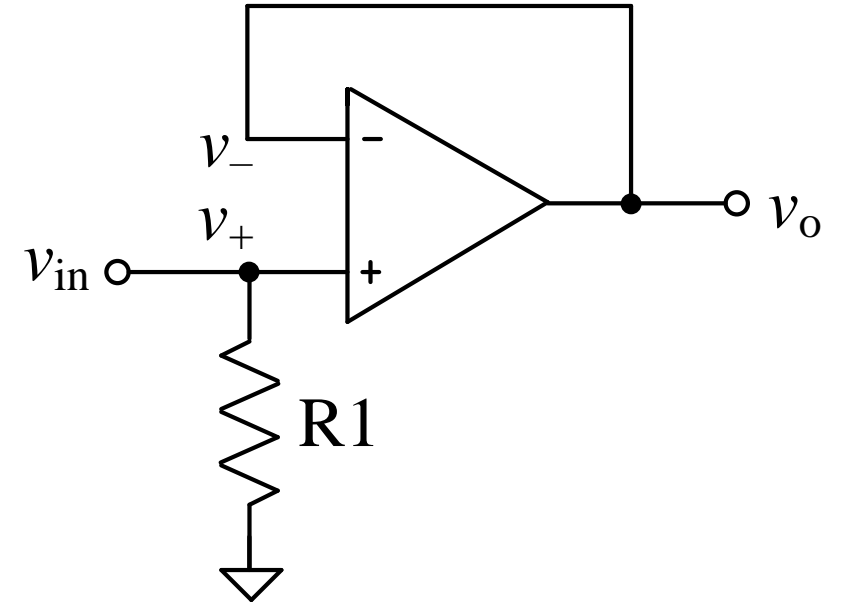*Application:* Buffer amplifier with very high  $R_{in}$  and very low  $R_o$ . It is used for connecting a source with high source resistance to a relatively low value load resistance without causing voltage attenuation. It provides unity voltage gain and large current gain.



## 4.4. Difference Amplifier Circuit

Select  $R_2/R_1 = R_4/R_3 = \alpha$ .

Virtual short assumption:  $i_1 = i_2$  &  $i_3 = i_4$ .

Circuit function: (i) inverting amplifier for  $v_2$ , (ii) attenuator & non-inverting amplifier for  $v_1$ .

$$\begin{aligned} v_o &= v_1 [R_2/(R_1+R_2)] [1+R_4/R_3] - v_2 [R_4/R_3] \\ &= v_1 [\alpha/(1+\alpha)][1+\alpha] - v_2 [\alpha] = \alpha (v_1 - v_2) \end{aligned}$$


DM gain  $A_d = \alpha$ .

CM gain  $A_c = 0$

$$R_{in1} = R_1 + R_2, \quad R_{in2} = R_3.$$


- Precise differential gain. Resistance matching needed. Difficult gain control. Unequal input resistances.
- A voltage (DC bias)  $v_3$  can be added to the output by connecting R2 to this voltage in place of ground.
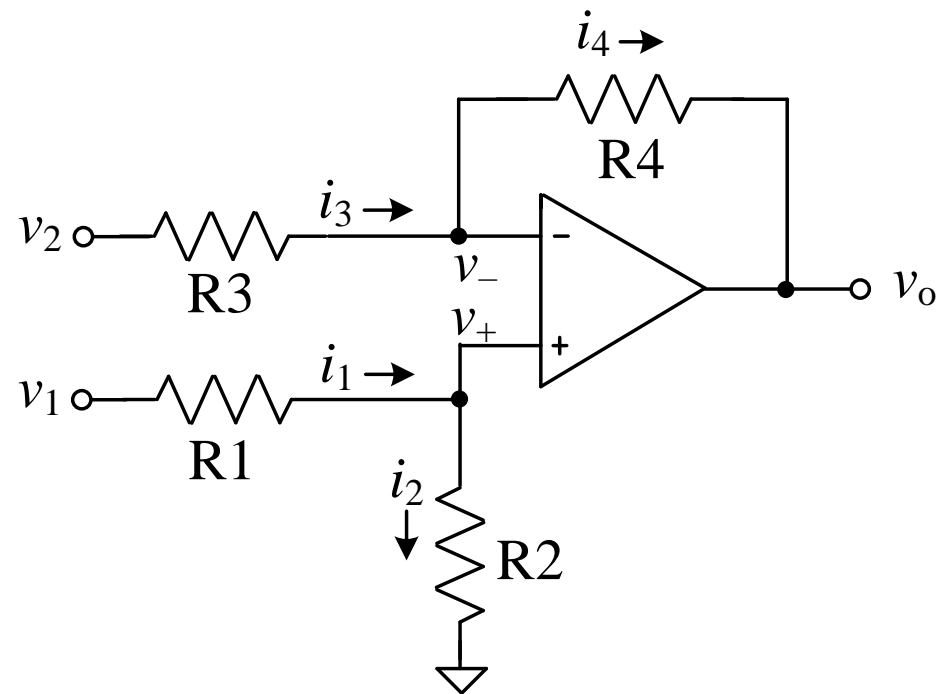
$$v_o = \alpha (v_1 - v_2) + v_3 [1/(1+\alpha)] / (1+\alpha) = \alpha (v_1 - v_2) + v_3$$


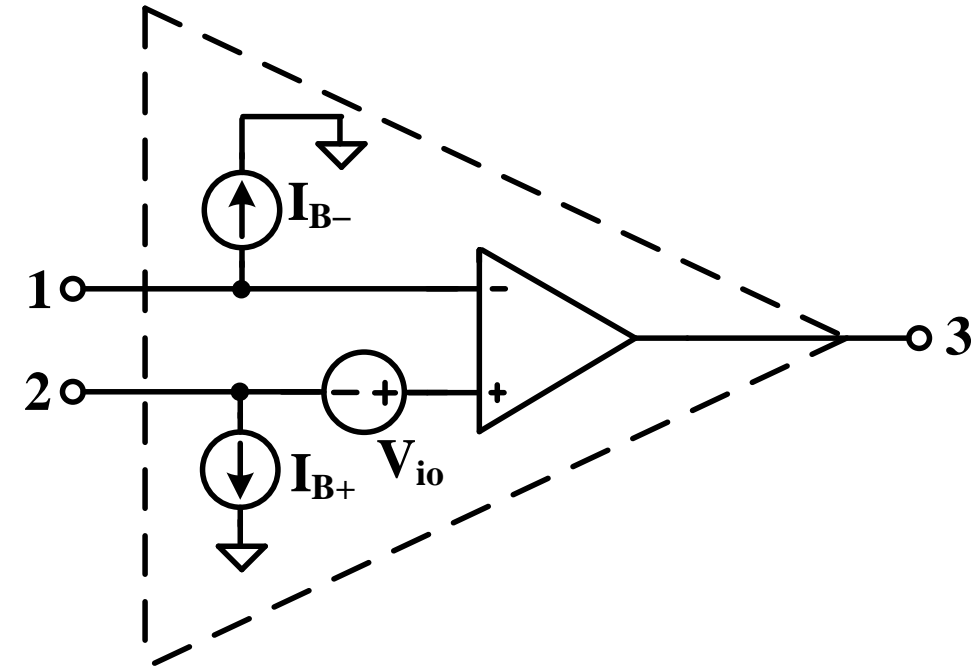
## 4.9. Practical Op Amp

- Op-amp linear operation has limits for CM input voltage, output voltage, & output current (due to DC supplies & internal circuit)
- DC imperfections
  - Input offset voltage (internal error voltage: 1–5 mV) causing output saturation in high-gain circuits.
  - Input bias currents: Small DC input currents (10 pA to 100 nA). These must be permitted by external circuit for proper operation.
- Finite input & output resistances.
- Finite diff. gain (typically  $> 10^5$  at dc, decreasing with frequency), finite CMRR. Another limitation for large amplitude AC signals is “slew rate”, the maximum rate of change of output voltage (typically 1 V/ $\mu$ s).



Op-amp DC error model



## 6. Nonlinear Circuits

### *Voltage Comparator*

Op-amp like device for open-loop operation & precise binary output levels.

$v_p > v_n$ :  $v_o = V_{OH}$  (high-level voltage)

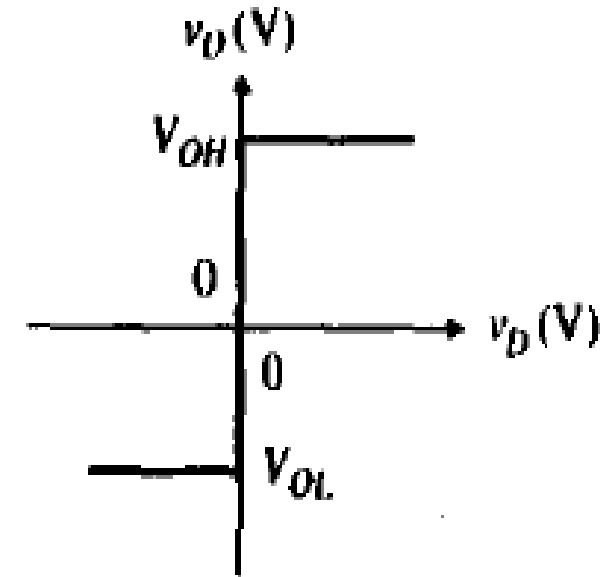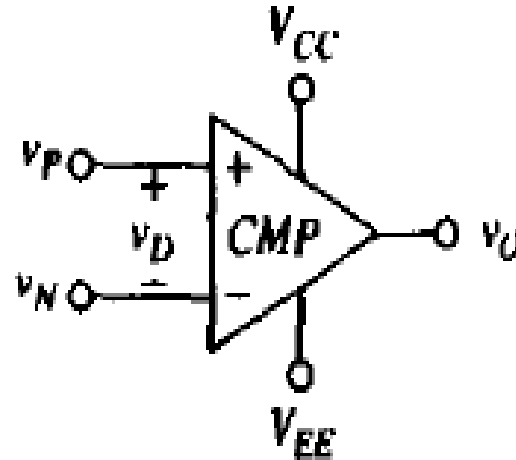$v_p < v_n$ :  $v_o = V_{OL}$  (low-level voltage)





- Circuit symbol: same as op amp, with analog inputs, binary output. Transfer characteristic: Very high gain at  $v_p = v_n$  with sharp transition between the two output levels.
- Input swing and output levels generally dependent on  $V_{CC+}$  and  $V_{EE-}$ .
- A comparator is designed for very low input currents despite large differential input voltage. It has buffers at each input before the differential high-gain. An op amp can also be used as a comparator with due consideration for finite differential input voltage.
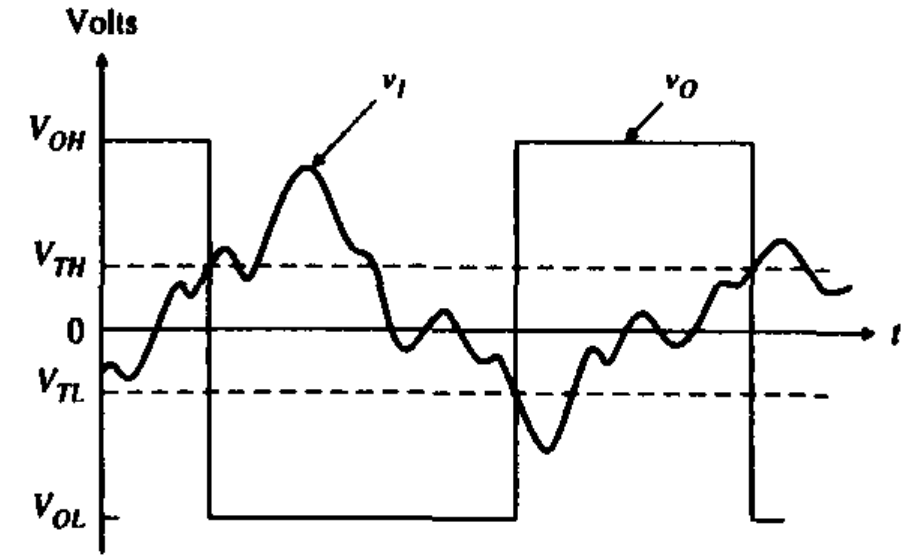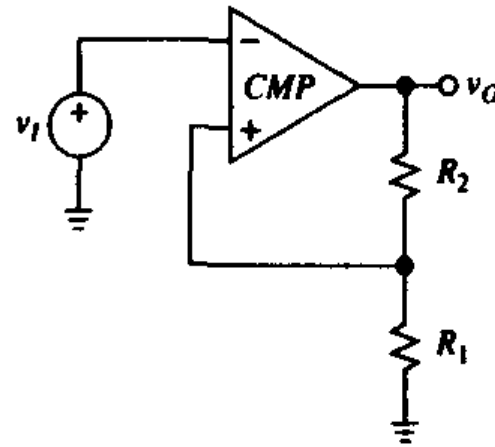
## *Schmitt Trigger*

Comparator with hysteresis: high-gain differential amplifier with +ve feedback. Bistable circuit.

- Inverting Schmitt trigger: clockwise hysteresis.
- Non-inverting Schmitt trigger: counterclockwise hysteresis.



***Applications:*** Chatter elimination, waveform generation, signal processing.