 


EE103 – Digital Lab Demo

2023-24/I Autumn

A) Logic Probe Circuit



'1' : LED ON

'0' : LED OFF

$V_{CC} = 5\text{ V}$ (Pin 14)


GND - Pin 7

JK Flip-flop Function Table

Function Table


Inputs					Outputs	
PR	CLR	CLK	J	K	Q	\overline{Q}
L	H	X	X	X	H	L
H	L	X	X	X	L	H
L	L	X	X	X	H*	H*
H	H	↓	L	L	Q ₀	$\overline{Q_0}$
H	H	↓	H	L	H	L
H	H	↓	L	H	L	H
H	H	↓	H	H	Toggle	
H	H	H	X	X	Q ₀	$\overline{Q_0}$

 - Synchronous inputs: J and K
- Asynchronous inputs: PRE' and CLR'



74S112 JK Flip-flop Pin-out

B) Toggle Flip-flop (using JK Flip-flop)

 

- JK Flip-flop wired as a Toggle Flip-flop (Mod-2 counter)
- $J = K = 1$; $\overline{PRE}' = \overline{CLR}' = 1$
- Q changes at the negative Clock edges
- V_{cc} line corrupted by switching noise
- Should use a de-coupling capacitor (between V_{cc} and GND – typ 0.1 μ F)

C) Mod-6 Ripple UP Counter

- Problem Statement: Design a modulo-6 Ripple UP counter using negative-edge triggered JK flip-flops.
- (Hint: Being an UP counter, use the following sequence of states (CBA): 000, 001, 010, 011, 100, 101, 000, 001,.... – will make design simpler)
- Solution: Connect input Clock to FF-A Clock input; Q_A output to FF-B Clock; Q_B output to FF-C Clock. Outputs $Q_C Q_B Q_A$ (or CBA).

Stable States


(CBA):

000, 001, 010,
011, 100, 101

Unstable (Quasi-stable)
State (CBA):

110 (we will decode
this state and clear the
flip-flop)

Mod-6 Ripple UP Counter

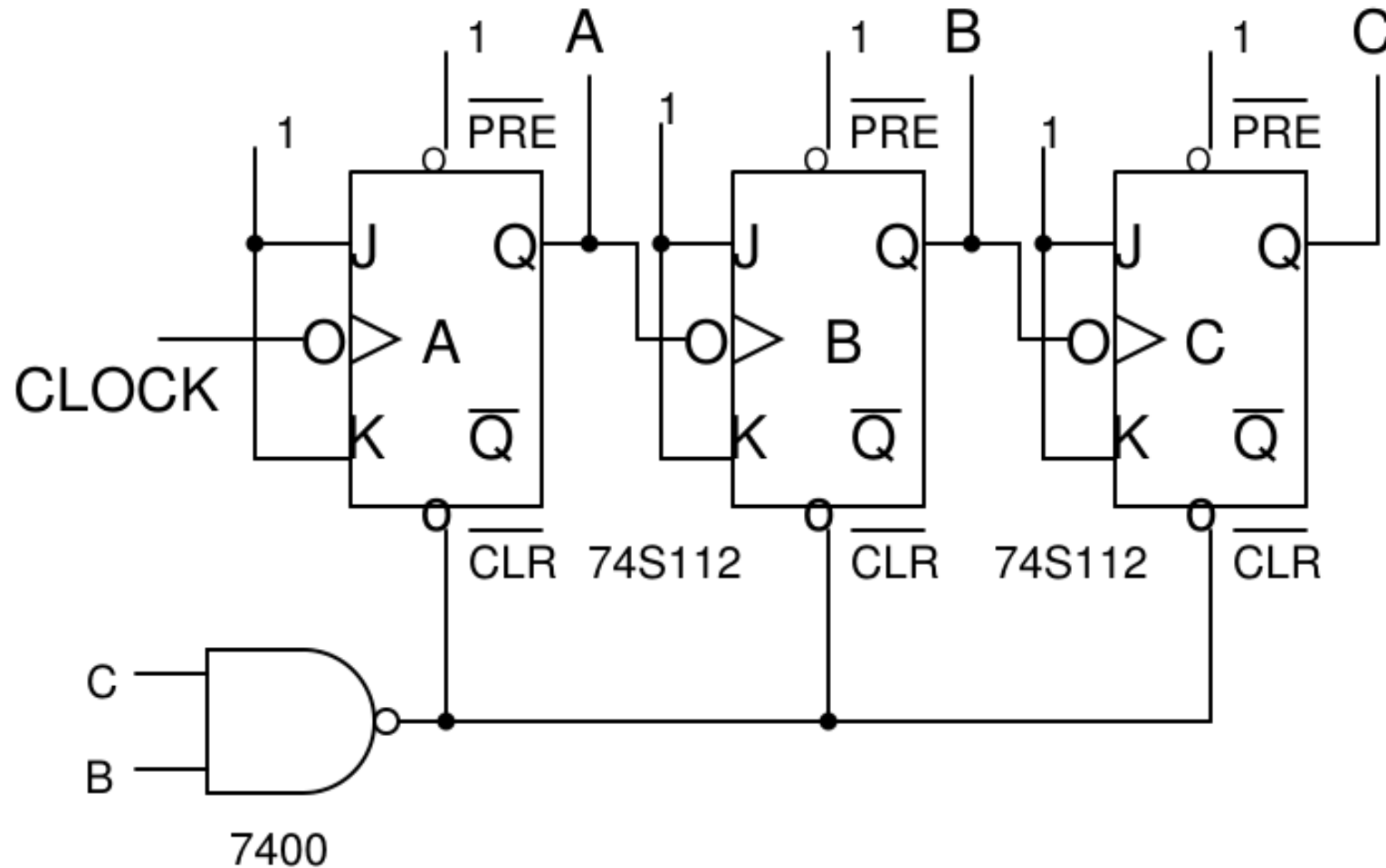

Stable States
(CBA):

000, 001,
010, 011,
100, 101

Unstable State
(CBA):

110

State 111 can
occur only at
Power ON

Ripple Counter Behaviour at Higher Clock Frequencies

- Advantage
 - Easy to design
- Disadvantages
 - Ripple counters used only up to a few MHz
 - Asynchronous outputs
 - The Quasi-stable state can create problems (in time critical applications)

D) Mod-5 Ripple DOWN Counter

- Problem Statement: Design a modulo-5 Ripple DOWN counter using negative-edge triggered JK flip-flops.
- (Hint: Being a DOWN counter, use the following sequence of states (CBA): 111, 110, 101, 100, 011, 111, 110,... – will make design simpler)
- Solution: Connect input Clock to FF-A Clock input; Q_A' output to FF-B Clock; Q_B' output to FF-C Clock. Outputs $Q_C Q_B Q_A$ (or CBA).

Stable States

(CBA):

111, 110, 101,
100, 011

Unstable (Quasi-stable)
State (CBA):

010 (we will decode this
state and clear the flip-
flop). Decode BA'

Mod-5 Ripple DOWN Counter

Stable States
(CBA):

111, 110,
101, 100,
011

Unstable State
(CBA):

010

States 001 and
000 can occur
only at Power ON