

# Introduction to Electrical Engineering

Course Code: EE 103

Department: Electrical Engineering

Instructor Name: B. G. Fernandes


E-mail id: [bgf@ee.iitb.ac.in](mailto:bgf@ee.iitb.ac.in)




# Review:
 
## Asynchronous (Ripple) Counter

Outputs of all the Flip-Flops do not change simultaneously. Hence Asynchronous or ripple (Flip-Flops respond one after another).




\*All J and K inputs assumed to be 1.

 

J	K	Clk	Q
0	0		Q <sub>0</sub> (Hold)
1	0		1
0	1		0
1	1		toggle
 
## Synchronous Counter (Parallel Counter):

- All Flip-Flops receive clock simultaneously.
- Some means must be used to control when an Flip-Flop should toggle and when it remains unaffected by a clock pulse.



# Design Procedure: Mod-8 Synchronous Counter

1. Determine the desired number of bits (Flip-Flops) and the possible states .

$Q_2$	$Q_1$	$Q_0$				
0	0	0				
0	0	1				
0	1	0				
0	1	1				
1	0	0				
1	0	1				
1	1	0				
1	1	1				
0	0	0				



# Design Procedure: Mod-8 Synchronous Counter

2. Prepare a table that lists all the present states and their next state.

$Q_2$	$Q_1$	$Q_0$	$Q_{2+}$	$Q_{1+}$	$Q_{0+}$			
0	0	0	0	0	1			
0	0	1	0	1	0			
0	1	0	0	1	1			
0	1	1	1	0	0			
1	0	0	1	0	1			
1	0	1	1	1	0			
1	1	0	1	1	1			
1	1	1	0	0	0			
0	0	0	0	0	1			

$N^{\text{th}}$ state	$(N+1)^{\text{th}}$ state	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



# Design Procedure: Mod-8 Synchronous Counter

3. Add two column per Flip-Flop (one for each J and K). There will be six columns for each 'PRESENT' state, indicate the levels requires at each J and K input in order to produce the transition to the 'NEXT' state

$Q_2$	$Q_1$	$Q_0$	$Q_{2+}$	$Q_{1+}$	$Q_{0+}$	$J_0$	$K_0$	$J_1$	$K_1$	$J_2$	$K_2$
0	0	0	0	0	1	1	X	0	X	0	X
0	0	1	0	1	0	X	1	1	X	0	X
0	1	0	0	1	1	1	X	X	0	0	X
0	1	1	1	0	0	X	1	X	1	1	X
1	0	0	1	0	1	1	X	0	X	X	0
1	0	1	1	1	0	X	1	1	X	X	0
1	1	0	1	1	1	1	X	X	0	X	0
1	1	1	0	0	0	X	1	X	1	X	1
0	0	0	0	0	1						

$N^{th}$ state	$(N+1)^{th}$ state	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0



# Design Procedure: Mod-8 Synchronous Counter

4. Design the logic circuit needed to generate the levels required at each J&K input

$J_0$

$Q_2Q_1$	00	01	11	10
$Q_0$				
0	1	1	1	1
1	X	X	X	X

$$J_0 = 1 \text{ (or } J_0 = \overline{Q_0} \text{)}$$

$J_1$

$Q_2Q_1$	00	01	11	10
$Q_0$				
0	0	X	X	0
1	1	X	X	1

$$J_1 = Q_0$$

$J_2$

$Q_2Q_1$	00	01	11	10
$Q_0$				
0	0	0	X	X
1	0	1	X	X

$$J_2 = Q_0Q_1$$

$K_0$

$Q_2Q_1$	00	01	11	10
$Q_0$				
0	X	X	X	X
1	1	1	1	1

$$K_0 = 1 \text{ (or } K_0 = Q_0 \text{)}$$

$K_1$

$Q_2Q_1$	00	01	11	10
$Q_0$				
0	X	0	0	X
1	X	1	1	X

$$K_1 = Q_0$$

$K_2$

$Q_2Q_1$	00	01	11	10
$Q_0$				
0	X	X	0	0
1	X	X	1	0

$$K_2 = Q_0Q_1$$




## Problem:

The figure shown is used for generating a magnetic field rotating in steps of  $90^\circ$  by selectively switching the currents in 4 coils by means of switches  $S_1$ ,  $S_2$ ,  $S_3$  &  $S_4$ .

$S_1$  ON &  $S_3$  OFF if  $Q_1 = 0$ .       $S_1$  OFF &  $S_3$  ON if  $Q_1 = 1$ .

 $S_2$  ON &  $S_4$  OFF if  $Q_2 = 0$ .       $S_2$  OFF &  $S_4$  ON if  $Q_2 = 1$ .



The sequence for rotating the field in counter clockwise direction is given below

$Q_2$	$Q_1$	Direction of field
0	0	←
0	1	↓
1	1	→
1	0	↑



## EXCITATION TABLE

$Q_N$	$Q_{N+1}$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

PRESENT STATE		NEXT STATE					
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>2+</sub>	Q <sub>1+</sub>	J <sub>1</sub>	K <sub>1</sub>	J <sub>2</sub>	K <sub>2</sub>
0	0	0	1	1	X	0	X
0	1	1	1	X	0	1	X
1	1	1	0	X	1	X	0
1	0	0	0	0	X	X	1

for J1

$Q_2 \backslash Q_1$	0	1
0	1	0
1	X	X

$$J_1 = \overline{Q_2}$$

for K1

$Q_2 \backslash Q_1$	0	1
0	X	X
1	0	1

$$K_1 = Q_2$$

for J2

$Q_2 \backslash Q_1$	0	1
0	0	X
1	1	X

$$J_2 = Q_1$$

for K2


$Q_2 \backslash Q_1$	0	1
0	X	1
1	X	0

$$K_2 = \overline{Q_1}$$





## Logic Realisation:

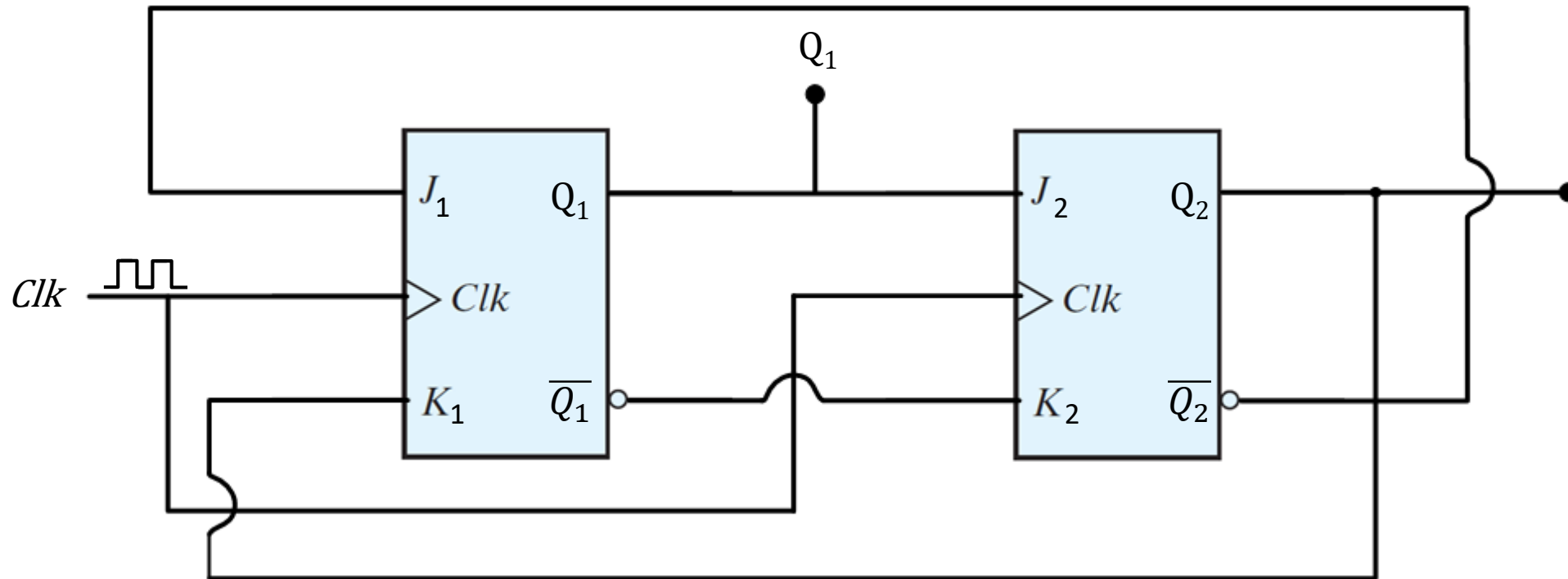

$$J_1 = \overline{Q}_2$$

$$J_2 = Q_1$$

$$K_1 = Q_2$$

$$K_2 = \overline{Q}_1$$



# Interfacing with the Analog World

Most physical variables are analog in nature.

Transducer  $\Rightarrow$  Convert the physical variable to an electrical variable (solar cell, photodiode).

## Analog to Digital Converter

ADC  $\Rightarrow$  Electrical output of transducer is converted to equivalent digital value.

8 bit ADC  $\Rightarrow$  output is digital code of 8 bits.

12 bit ADC  $\Rightarrow$  output is digital code of 12 bits.



# ADCs and DACs


Functions as an interface between computer(digital) and the real(analog) world.

**D/A Conversion :** It is the process of taking a value represented in digital code and converting it to a voltage or current that is proportional to the digital value.

⇒ Input for a voltage reference.  $V_{ref}$

⇒ This is used to determine full scale output or maximum value that D/A can produce.

For each input number ⇒ unique output

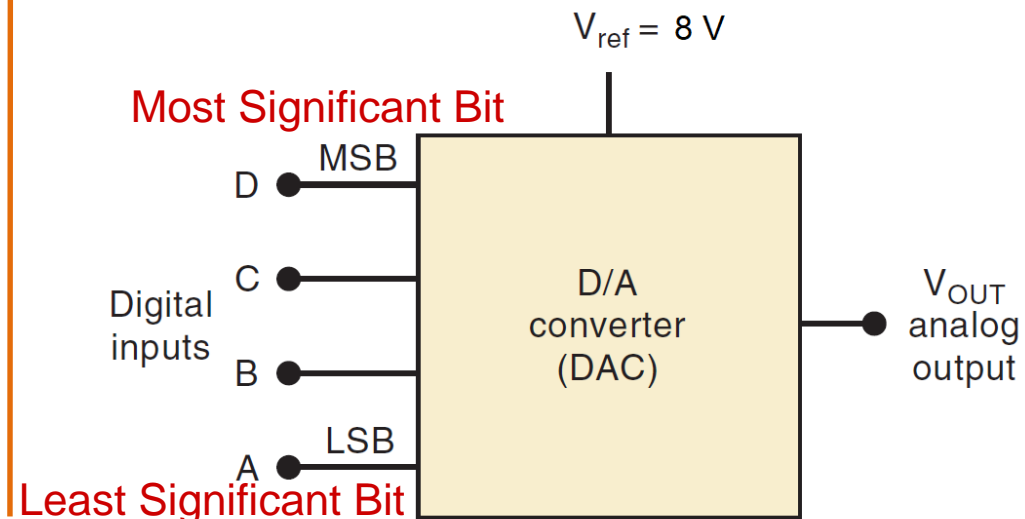

D	C	B	A	$V_{OUT}$
0	0	0	0	0 V
0	0	0	1	0.5 V
.	.	.	.	
.	.	.	.	
.	.	.	.	
1	1	1	1	7.5 V



# D/A Conversion

- $V_{ref} \rightarrow$  used to define full scale reading (FSR)

$0000 \rightarrow 0\text{ V}$   
 $1111 \rightarrow 7.5\text{ V}$  } 16 different binary numbers  $\rightarrow$  16 different analog values  
MAX  $\rightarrow 7.5\text{ V}$

Example:

If  $10100 \rightarrow$  gives output of  $10\text{ mV}$ ,

Then  $11101 \rightarrow$  ???

$10100 \rightarrow (20)_{\text{decimal}} \rightarrow 10\text{ mV}$

$11101 \rightarrow (29)_{\text{decimal}} \rightarrow \frac{29}{20} 10\text{ mV}$   
 $\rightarrow 14.5\text{ mV}$



# D/A Conversion Resolution

- Output changes in steps  $\Rightarrow$  Not strictly analog
- If the no. of bits  $\uparrow$ , step size  $\downarrow$ ,  $\Rightarrow$  Resolution can be improved

**Resolution:** Smallest change that can occur in the analog output for a change in digital input.


For an N-bit DAC  $\Rightarrow$  there are  $2^N$  different levels  
 $\Rightarrow$  No. of steps is  $(2^N - 1)$

$$\text{Resolution} = \frac{FSR}{2^N - 1}$$



# Simple D/A circuit

- Inputs – 0 or 1, 0 or 5 V

 

Input resistors are binary weighted!

For 12 bit DAC: If MSB =  $1\text{k}\Omega$   
 $\Rightarrow$  LSB  $> 2\text{M}\Omega$


$$V_{out} = - \left( V_D + \frac{V_C}{2} + \frac{V_B}{4} + \frac{V_A}{8} \right)$$

What happens if feedback resistor  $R_F$  is reduced?


- Output  $\propto$  weighted sum of the digital inputs
- Resolution of the D/A  $\Rightarrow$  weights of LSB =  $\frac{1}{8} 5\text{ V} = 0.625\text{ V}$




# R-2R Ladder D/A

 

Only MSB = 1

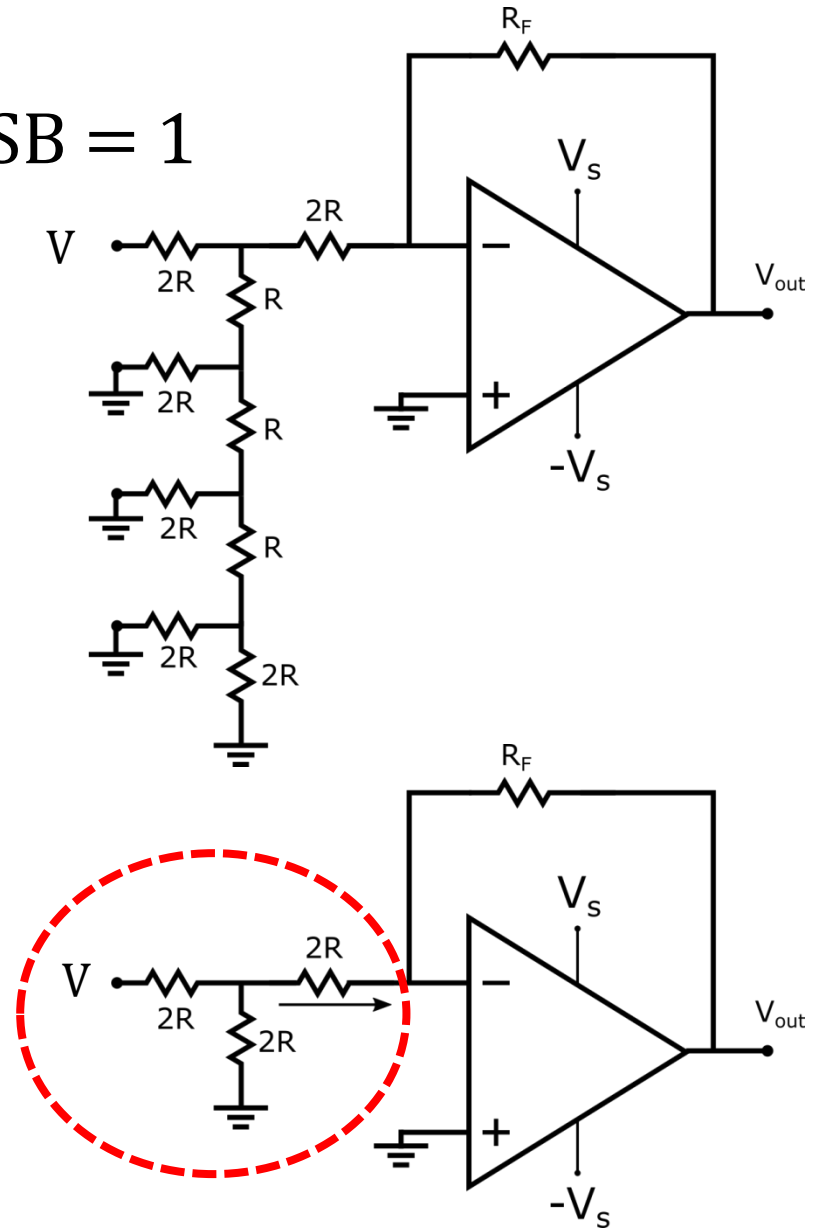

# R-2R Ladder D/A

 



- Current in  $R_F = \frac{I}{2}$ , where  $I = \frac{V}{3R}$
- Current due to  $I^{nd}$  bit =  $\frac{I}{4}$  (See next page for derivation)
- Total current due to all bits
 
$$= \frac{I}{2} + \frac{I}{4} + \frac{I}{8} + \frac{I}{16}$$

$$= \frac{I}{2} \left[ 1 + \frac{1}{2} + \frac{1}{2^2} + \frac{1}{2^3} \right]$$
- Output =  $V_O = \frac{-R_F I}{2} \left[ 1 + \frac{1}{2} + \frac{1}{2^2} + \frac{1}{2^3} \right]$

  Assume all left nodes to be at GND and calculate the current through each of the bits individually using R equivalent and add all of them in the end.








$I_1 \Rightarrow$  current through ' $R_F$ '?





# Simple ADC
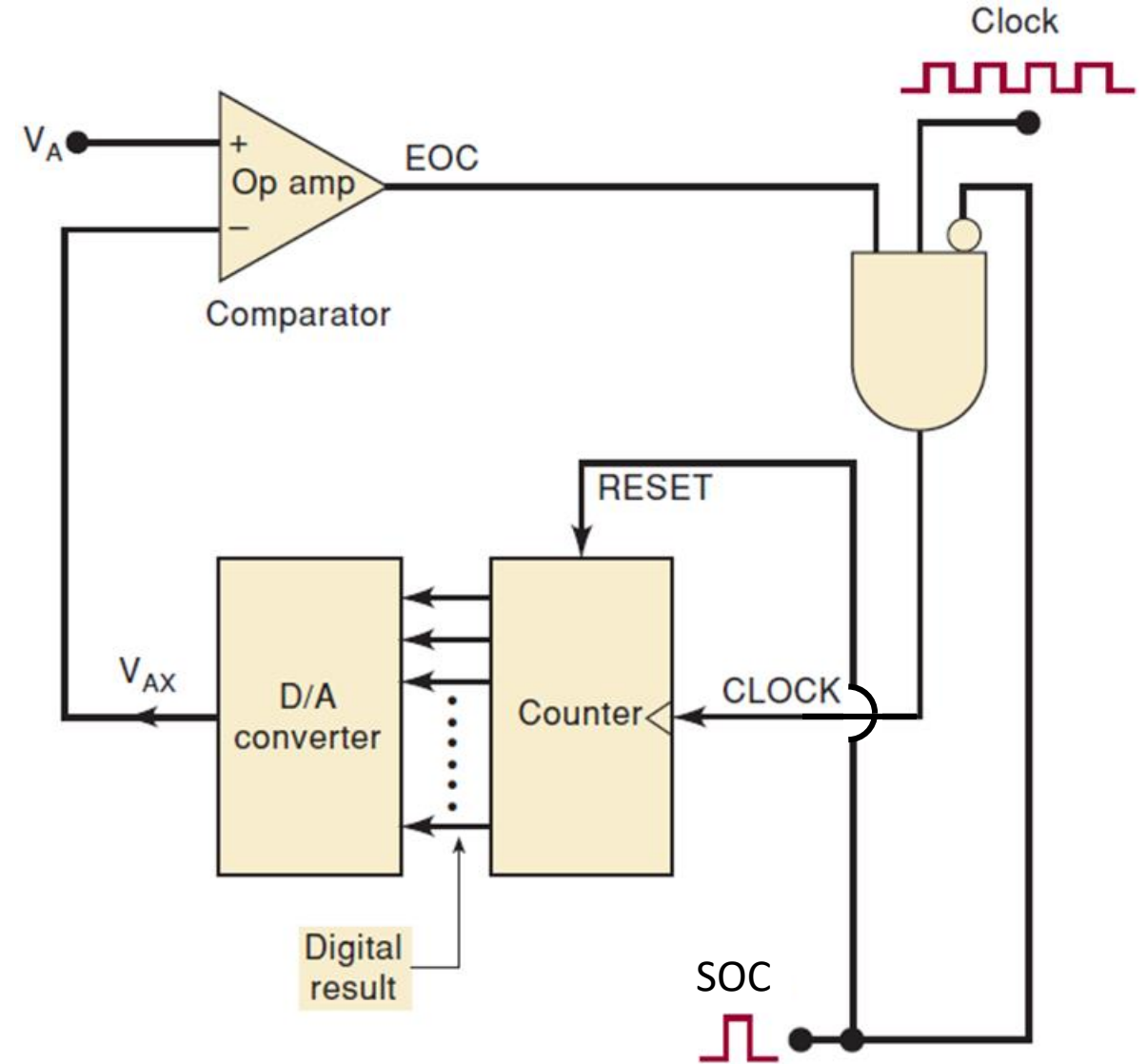
## System on a Chip

- Apply SOC = 1  $\Rightarrow$  Reset the Counter. Also the clock gets disabled for a short duration.
- All Outputs of the converter = 0
- $V_{AX} = 0$
- D/A output connected to  $-ve$  input of comparator  $\Rightarrow$  EOC = 1, till  $V_{AX} < V_A$ .
- Output of 3-input AND is CLOCK signal
- At every CLOCK signal, counter output  $\uparrow$ , 000...0 – 000...1
- D/A output  $\uparrow$  in steps
- If  $V_{AX} < V_A$ , EOC = +ve (1)
- As soon as  $V_{AX} > V_A$ ,  
EOC = -ve (0)





# Simple ADC

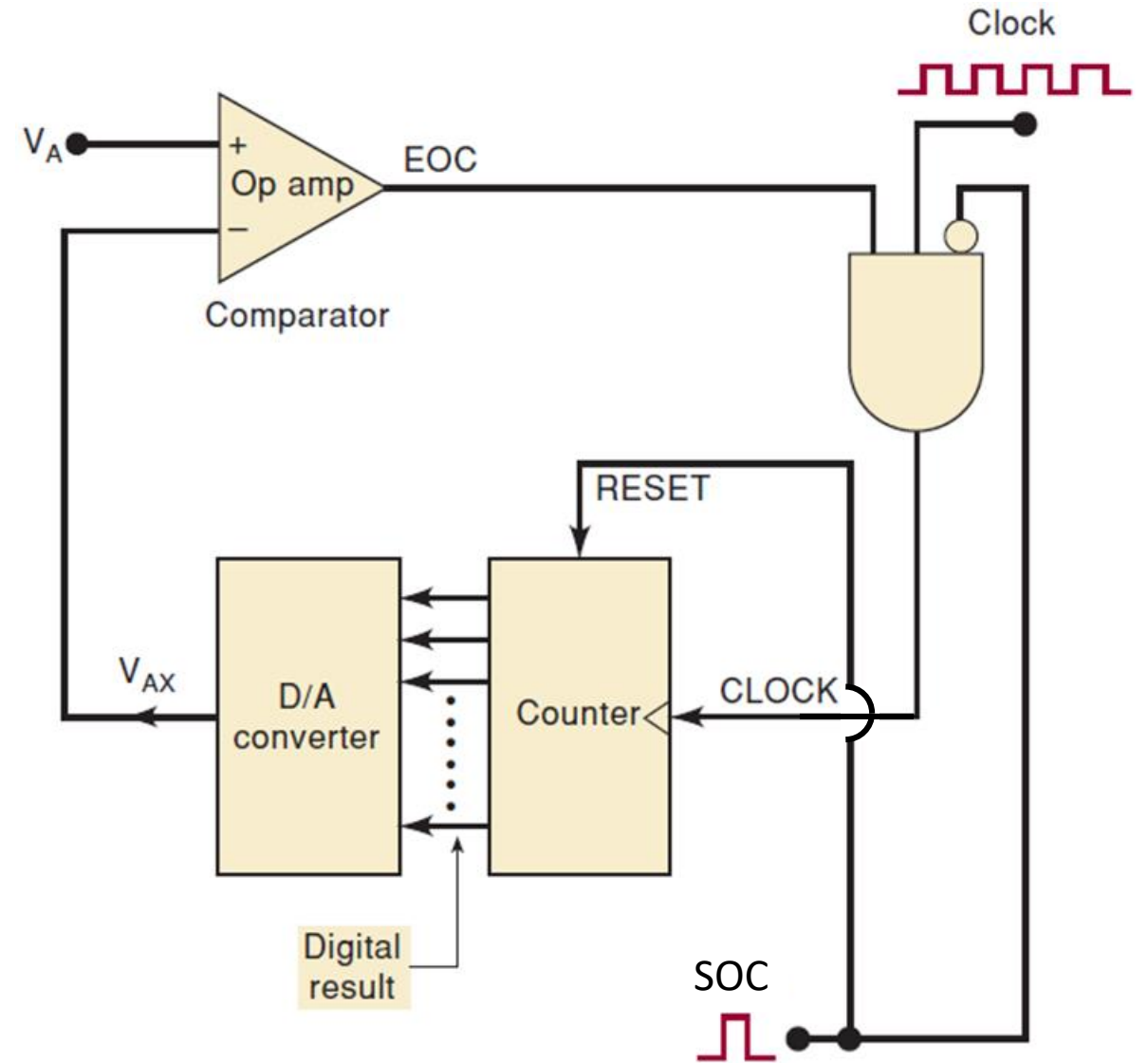 
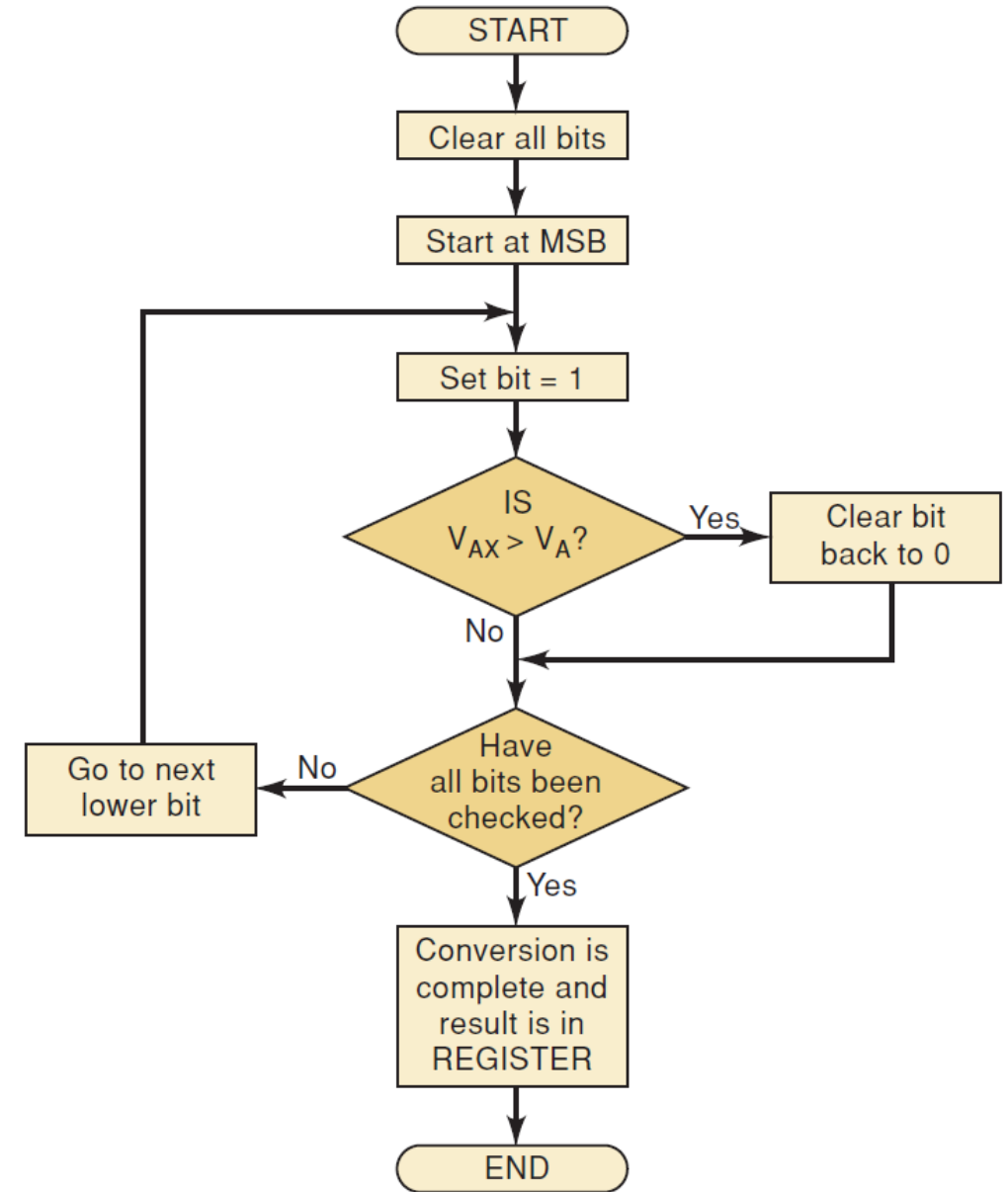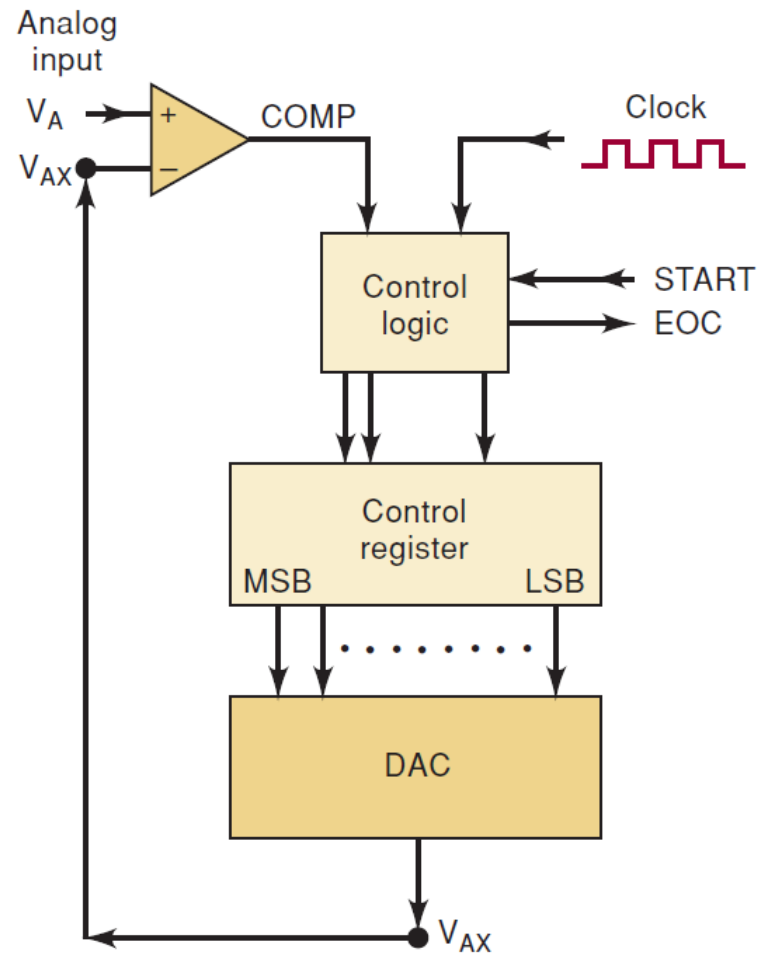
# Successive Approximation ADC

- Most widely used.
- Much shorter conversion time than precision ADC.



# Successive Approximation ADC

