

Lecture 3A: Diode Circuits

EE 103

2023-24/I (Autumn)

Joseph John (j.john@iitb.ac.in, jjohn@ee.iitb.ac.in)

Summary of Topics for Lect 3

- **Lect 3A – Rectifier and Regulator Circuits**

- Part1: Rectifier circuits: Half-wave rectifier, Full-wave rectifier (Bridge rectifier)
- Part 2: Unregulated DC Power Supply
- Part 3: Regulator DC Power Supply (Voltage Regulator: IC based regulated DC Power Supply)

Part 1: Rectifier Circuits

Part 1: Rectifier Circuits

- Half-Wave Rectifier
- Full-wave Rectifier
 - Bridge rectifier circuit

Step Down Transformer (230 V - 12 V RMS)

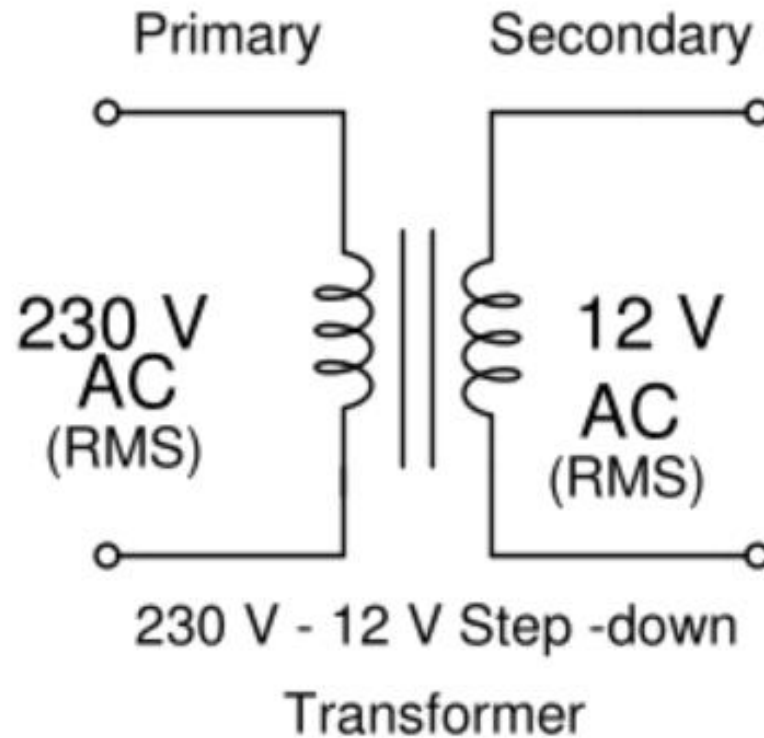


Fig. 1 Step-down Transformer

A) Half-wave Rectifier


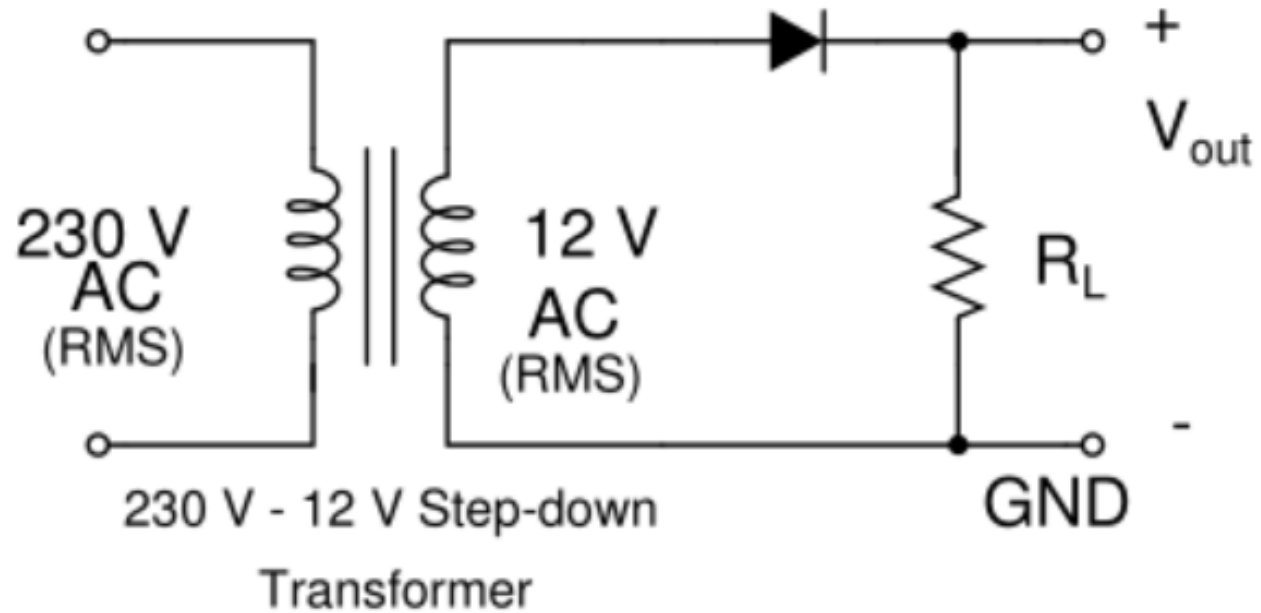


Fig. 2

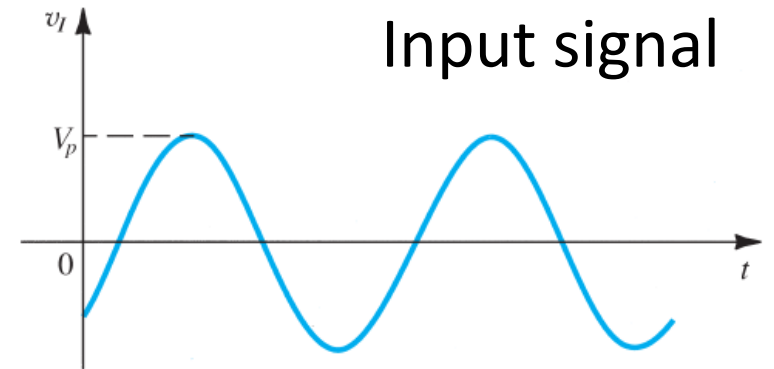

Half-wave Rectifier Output

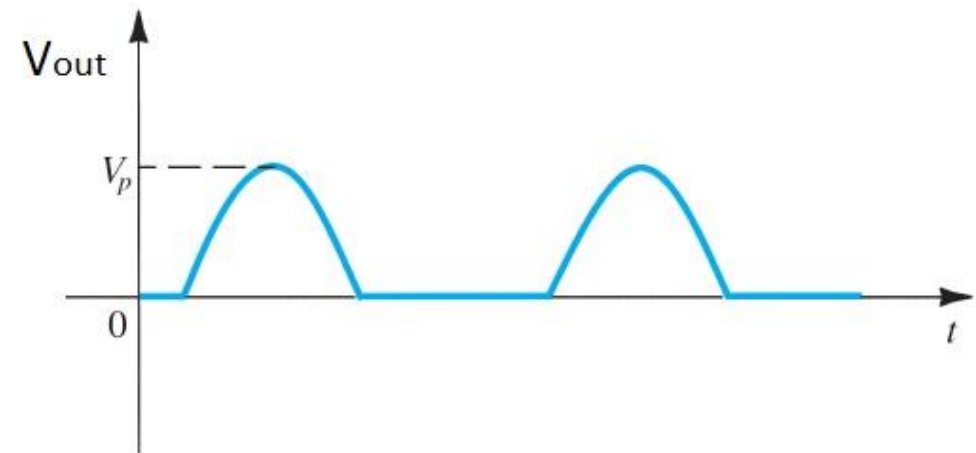


Fig. 3

B) Full-wave (Bridge) Rectifier


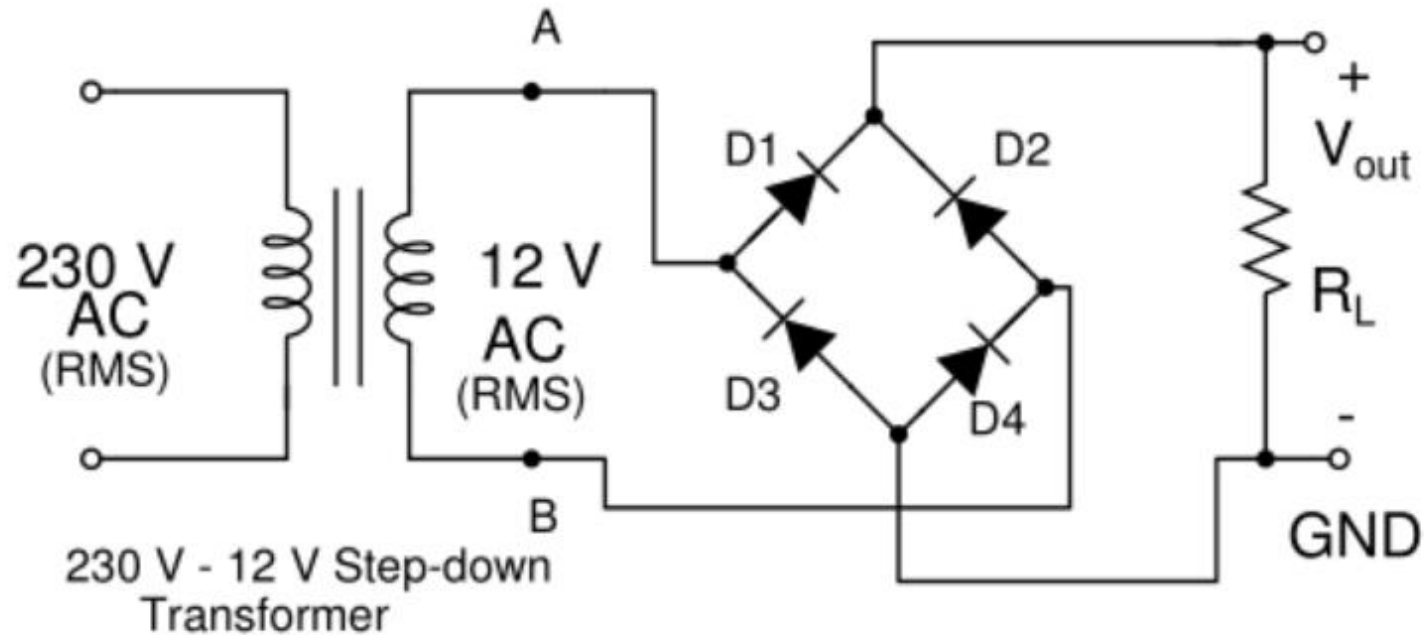


Fig. 4

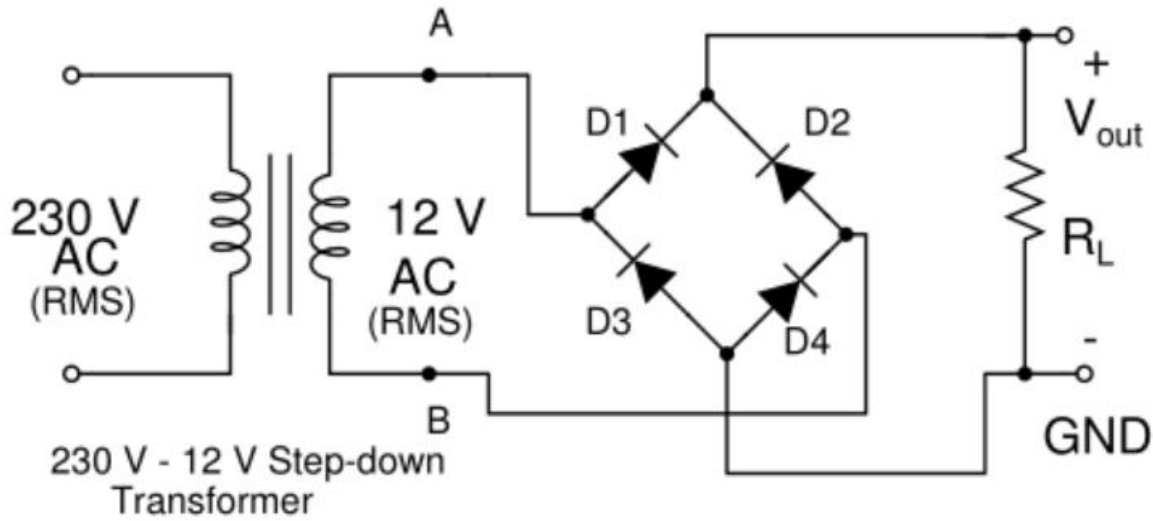- Bridge Rectifier: in every half cycle, two diodes will be in the current path



- 1st half cycle (output A is +ve w.r.t. Output B): current path – from output A \rightarrow D1 \rightarrow R_L \rightarrow D4 \rightarrow B; D2 and D3 will not conduct.
- 2nd half cycle (Output B is +ve w.r.t. output A): current path – from B \rightarrow D2 \rightarrow R_L \rightarrow D3 \rightarrow A; D1 and D4 will not conduct.

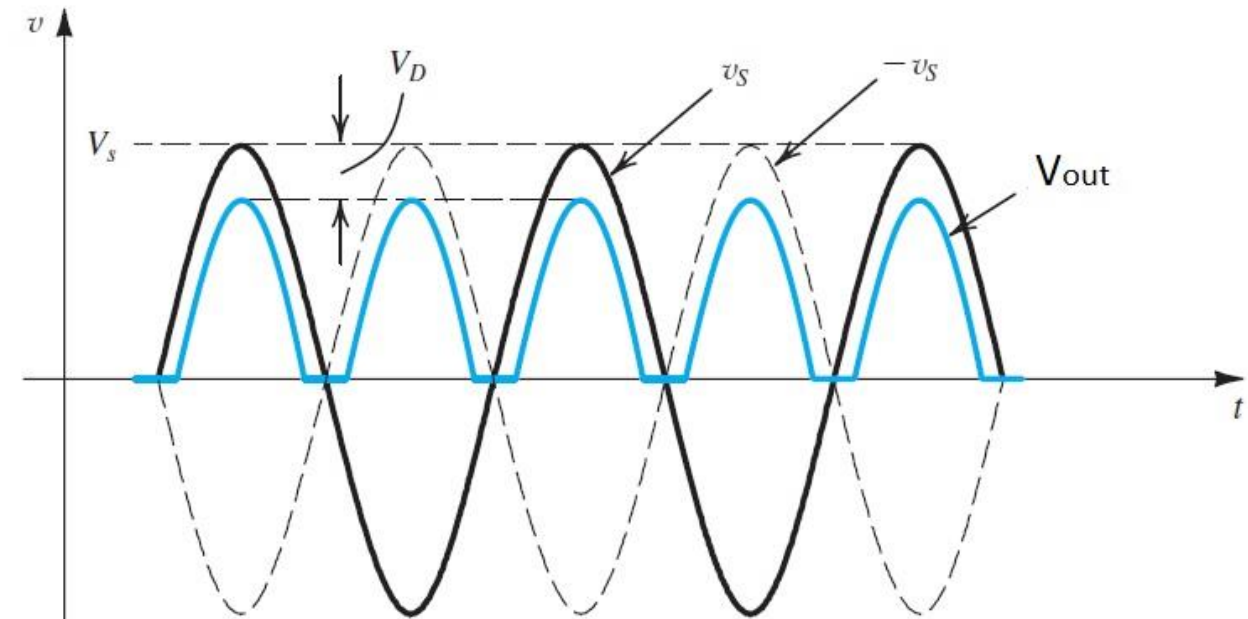


Fig. 5

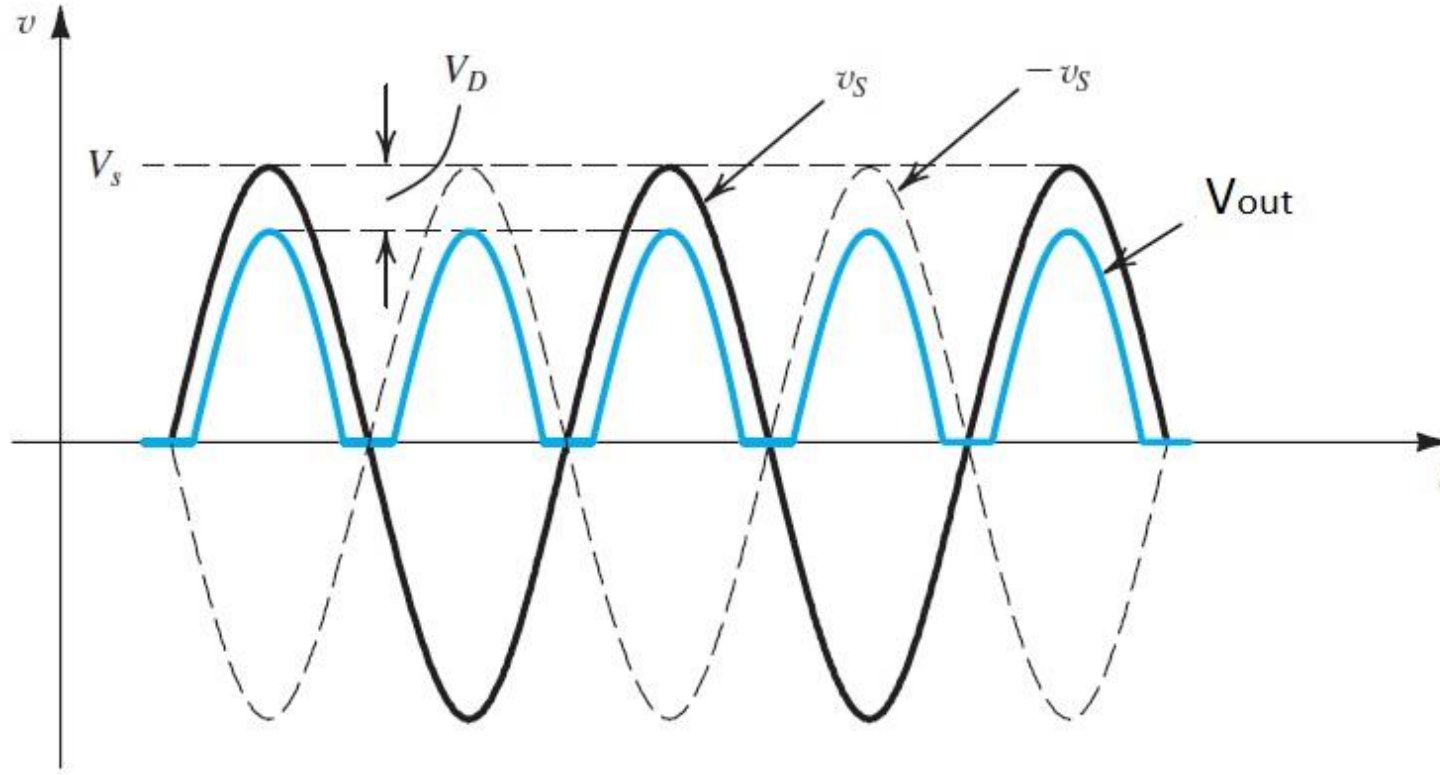


Fig. 6

- Full-wave Rectifier: Input and Output waveforms (considering diode drops)
- Output voltage will have the *two diode drops* lower than the input voltage. Typ. diode drop = 0.6 V

Part 2: Unregulated Power Supply (Capacitive filter)

Unregulated Power Supply

(Using Half-wave Rectifier and a Capacitive filter)


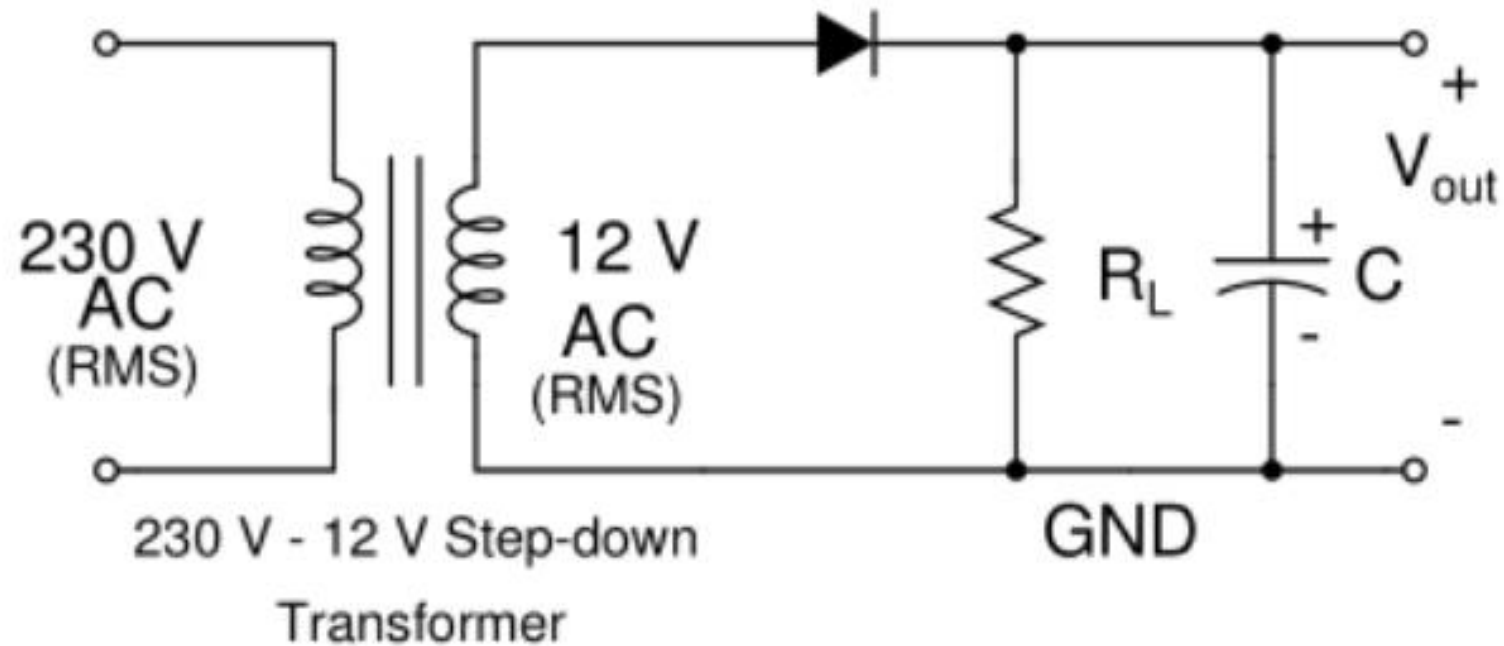


Fig. 7

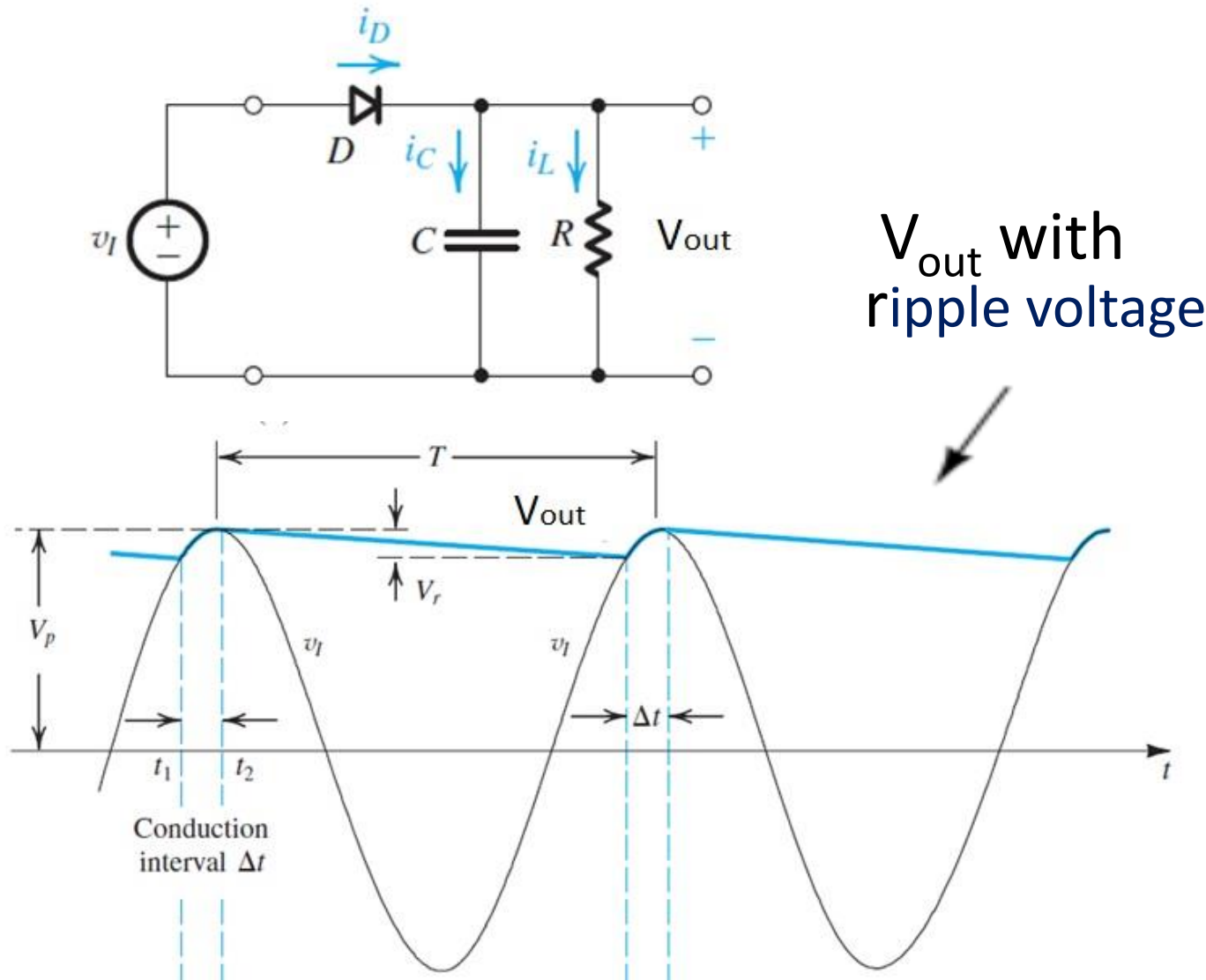

V_{out} with
ripple voltage

- The half-wave rectifier with C is very seldom used due to its higher ripple voltage


Operation with C across R_L

- C charges during Δ_t , and discharges during $(T - \Delta_t)$.
- Ripple voltage, V_r increases with i_L (load current).
- Ripple voltage can be decreased by increasing C (not a good solution).
- For a given i_L , as $C \uparrow$, $\Delta_t \downarrow$ (which will make $i_D \uparrow \uparrow$)

Fig. 9

Operation with C across R_L

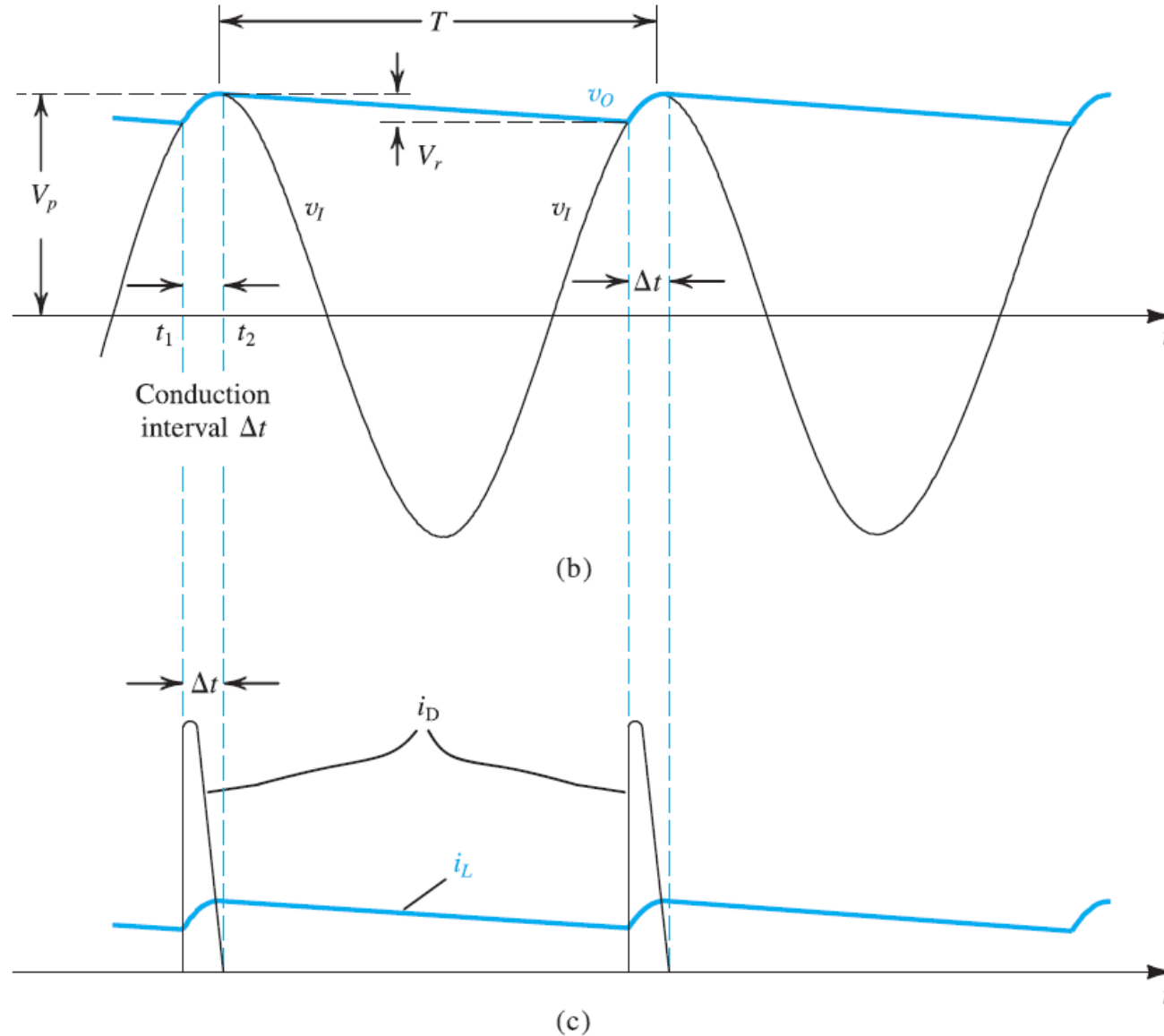- C charges during Δt , and discharges during $(T - \Delta t)$.
- Ripple voltage, V_r increases with i_L (load current).
- Ripple voltage can be decreased by increasing C (not a good solution).
- For a given i_L , as $C \uparrow$, $\Delta t \downarrow$ (which will make $i_D \uparrow \uparrow$)



Unregulated Power Supply

(Using Full-wave Bridge Rectifier and a Capacitive filter)

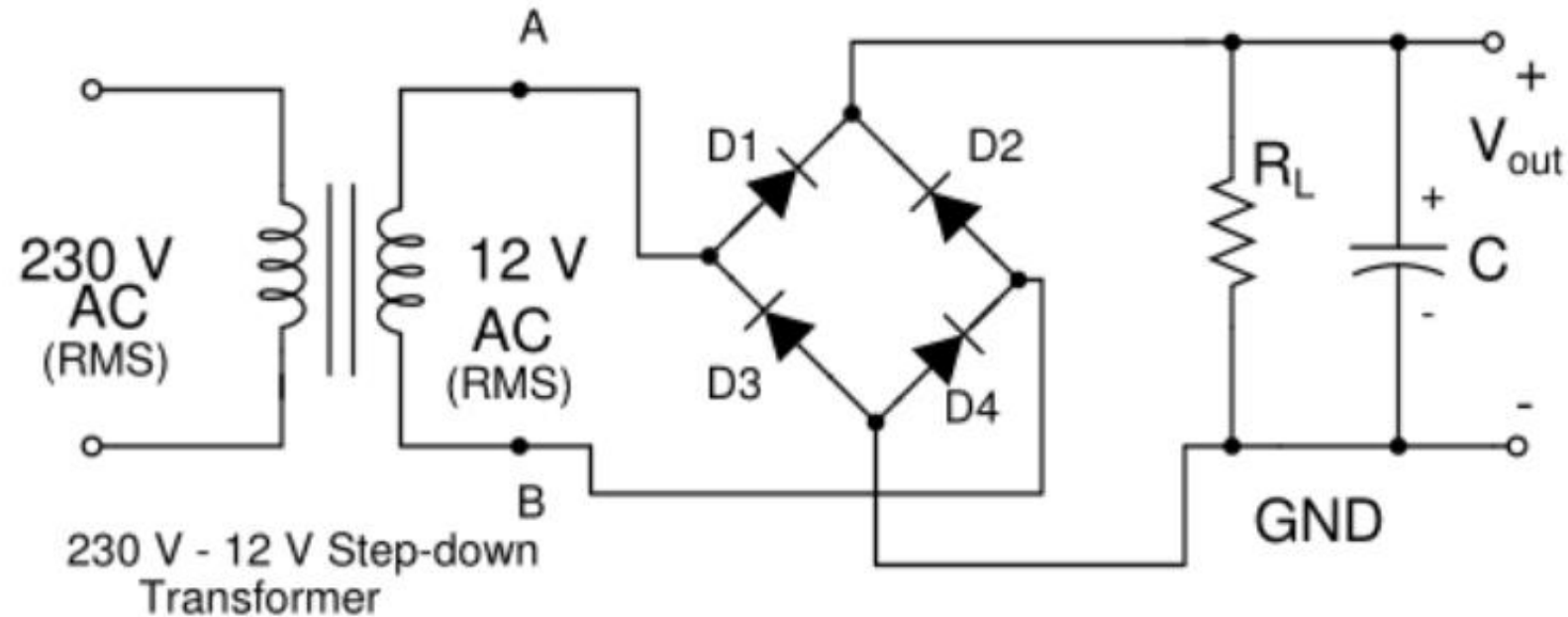


Fig. 10

- Much better than the half-wave (HW) rectifier
 - For the same C and R_L , peak-to-peak ripple voltage gets reduced to half that of HW

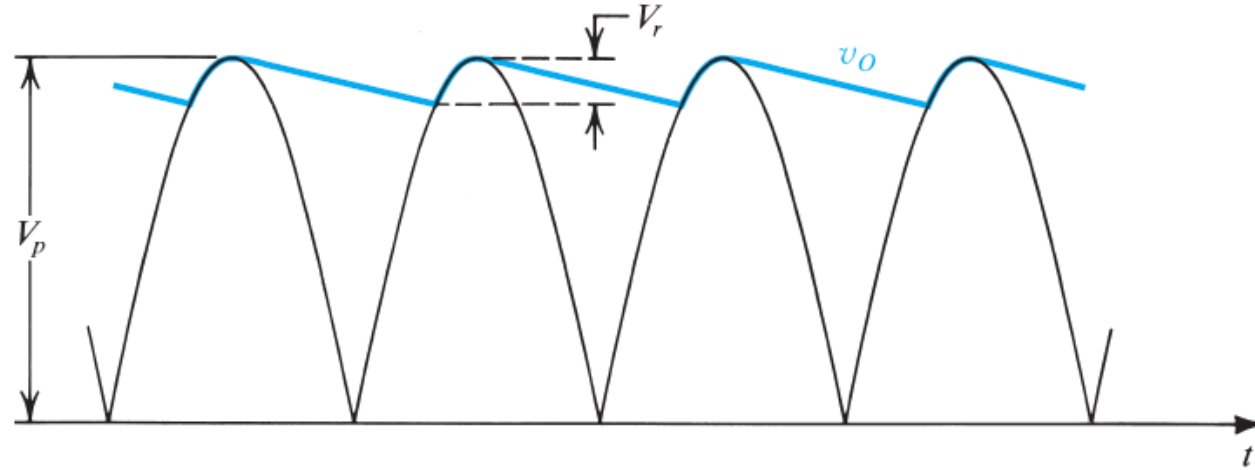
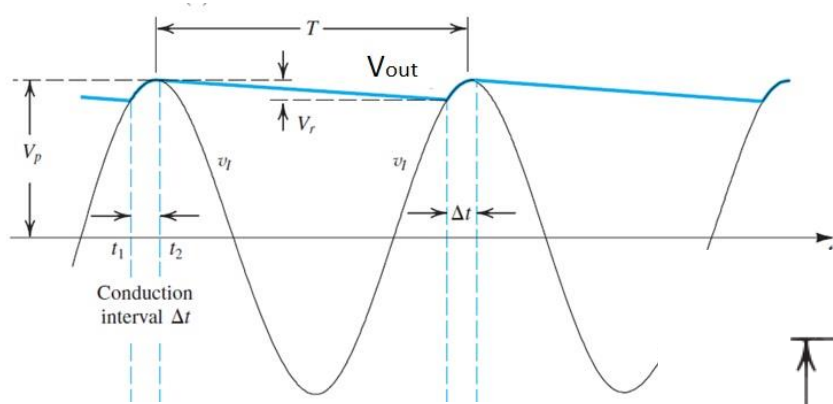


Fig. 11

- Full-wave rectifier output waveform (blue)
- Less Ripple voltage, compared to the Half-wave rectifier circuit
 - Discharge interval for C almost half that of HW case)

Problems of Unregulated Power Supply

- Output voltage fluctuates
 - When ac input voltage fluctuates
 - When load current fluctuates
- Ripple voltage increases with load current
 - Ripple voltage for a given load current (i_L) can be reduced only by increasing C
 - Increasing C beyond a certain value can cause diode damages (as the peak diode current will always be many times the average load current)

Part 3: Regulated DC Power Supply

Regulated Power Supply

- **Problems of the unregulated power supply**
 - Output voltage fluctuates with the input voltage (for a given load current) - Line regulation
 - Output voltage fluctuates for load current (for a given input voltage) - Load regulation
- **Regulated Power Supply**
 - Output voltage stays constant (reasonably well):
 - For varying input voltages
 - For varying load currents

Two solutions

- Solution 1
 - Zener diode regulator circuit
- Solution 2
 - Voltage Regulator IC

Solution 1: Zener Regulator Circuit


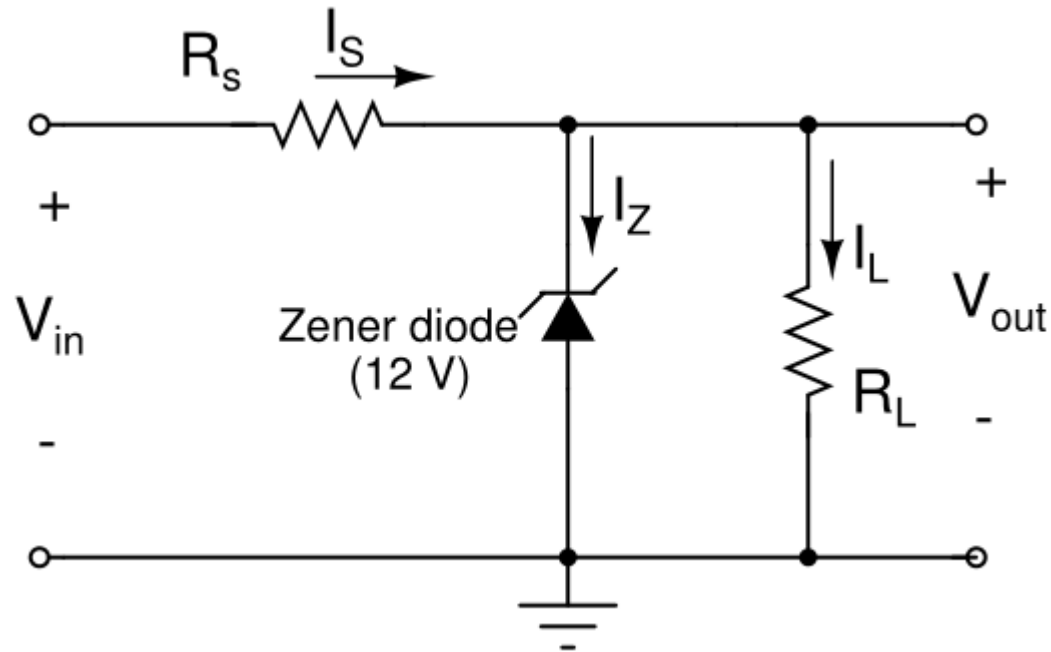
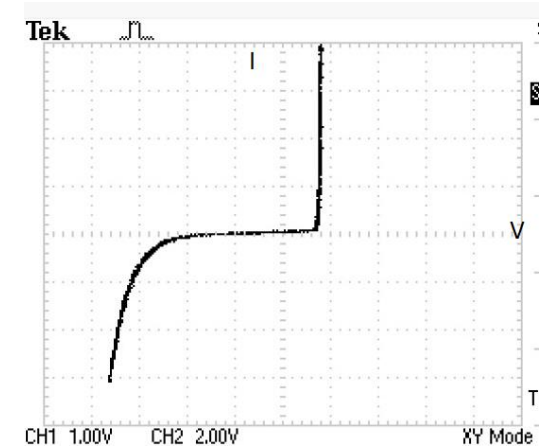
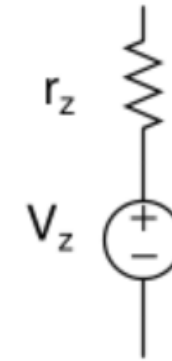


Fig. 18

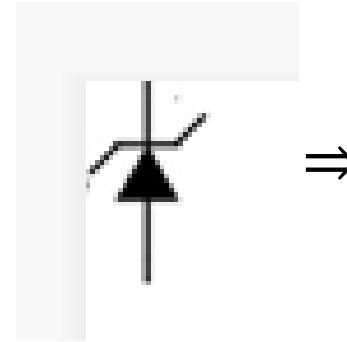Problem statement:


In the Zener regulator circuit shown, $V_{in} = 20\text{ V}$, $R_s = 600\ \Omega$, $R_L = 1\text{ k}\ \Omega$. Find out the regulator output voltage V_{out} and the load current I_L .

Zener parameters: $V_Z = 12\text{ V}$, $r_z = 200\ \Omega$




Solution:

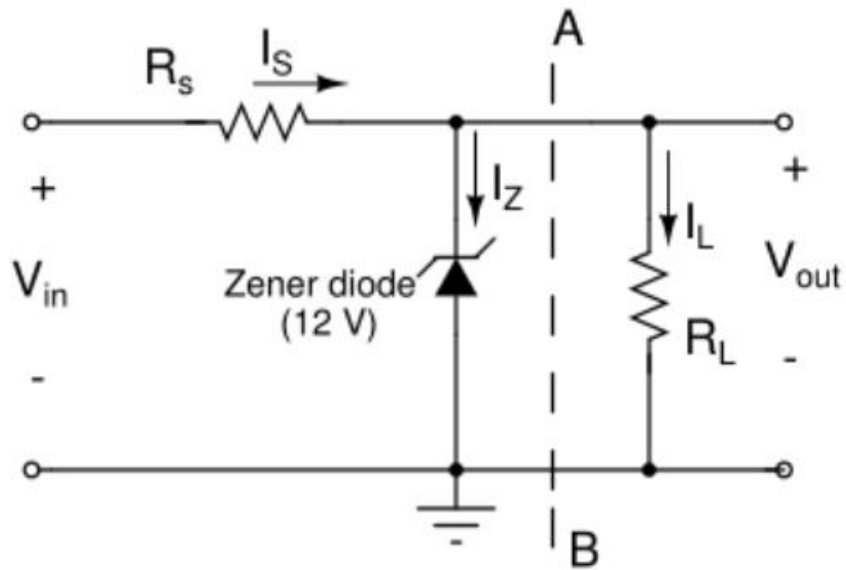- In the circuit, the zener diode is reverse biased and operating as a zener.
- We will use a simple model for the zener diode (zener diode voltage (V_Z) and a series resistor r_z).
- Replace the zener with the equivalent circuit.
- Apply Thevenin's theorem.




\Rightarrow

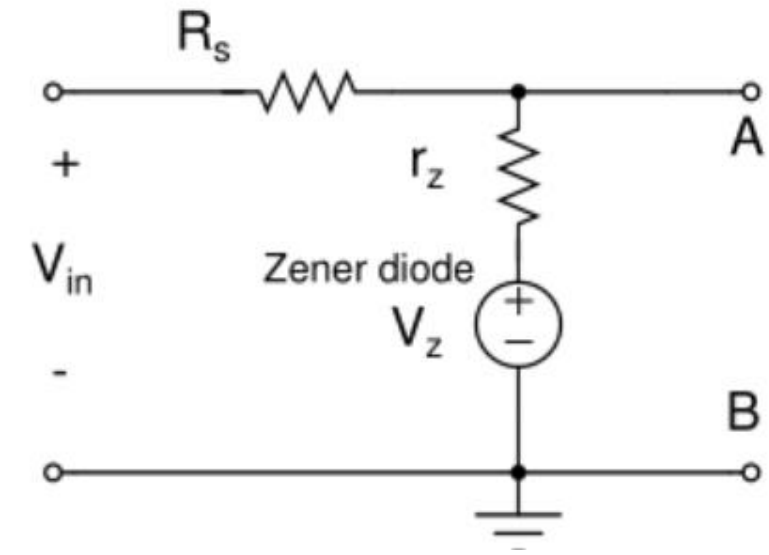

Find V_{Th} and R_{Th} of this circuit across AB

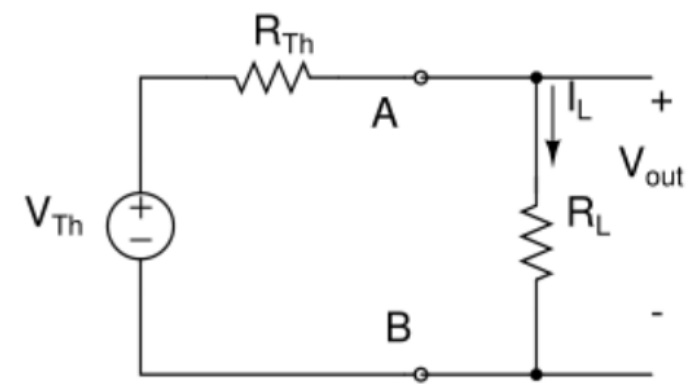Putting $V_{in} = 20\text{ V}$, $R_S = 600\ \Omega$,
 $V_Z = 12\text{ V}$, $r_z = 200\ \Omega$, we get
 $V_{TH} (V_{AB}) = 14\text{ V}$; $R_{TH} (= R_S \parallel r_z) = 150\ \Omega$
 $R_L = 1\text{ k}\Omega$



Substituting
 and evaluating,
 $V_{out} = 12.17\text{ V}$
 $I_L = 12.17\text{ mA}$

3B: 7812 Three-terminal Voltage Regulator

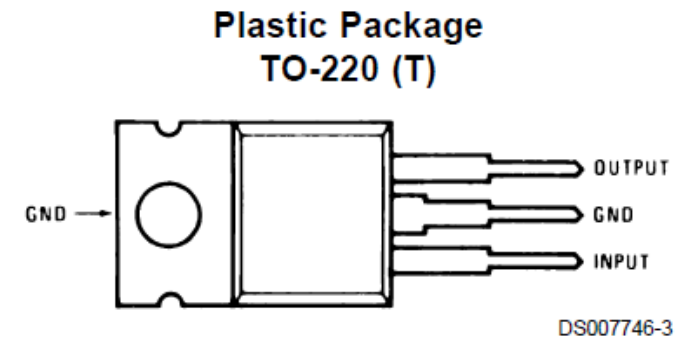
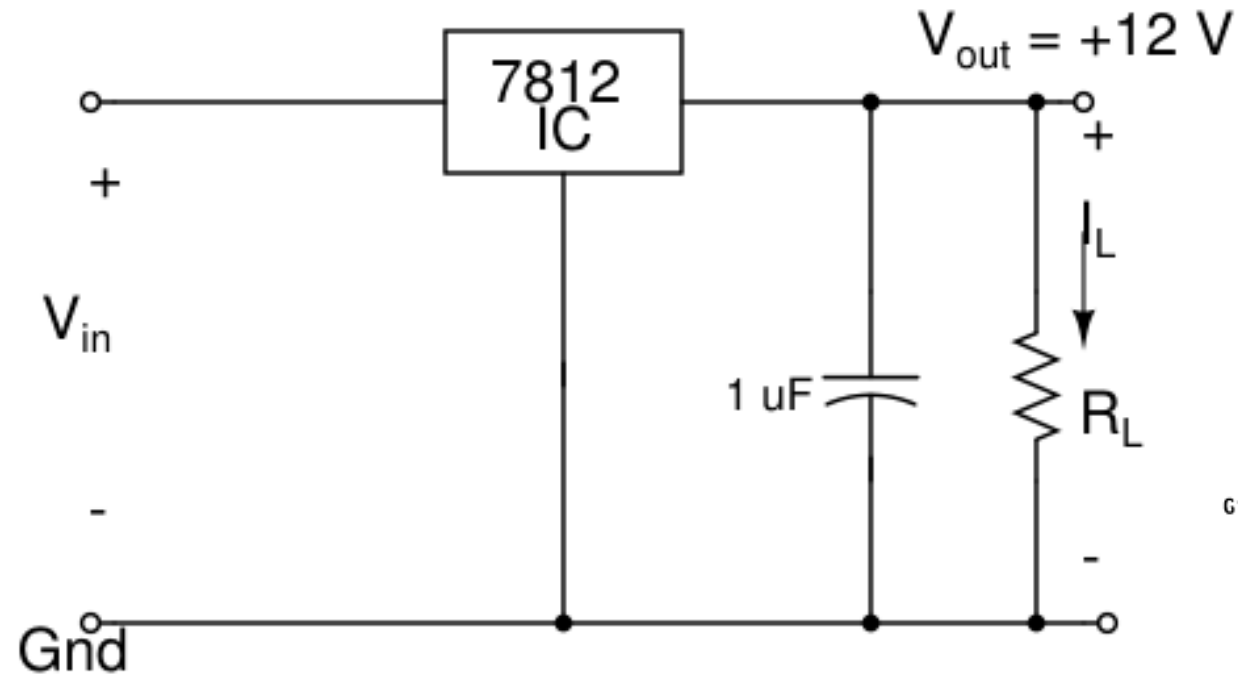


Fig. 12

$V_{in} : +14.5 \text{ to } 30 \text{ V}, V_{out} : 11.5 \text{ to } 12.5 \text{ V}$

$I_L = \text{up to } 1 \text{ A}$

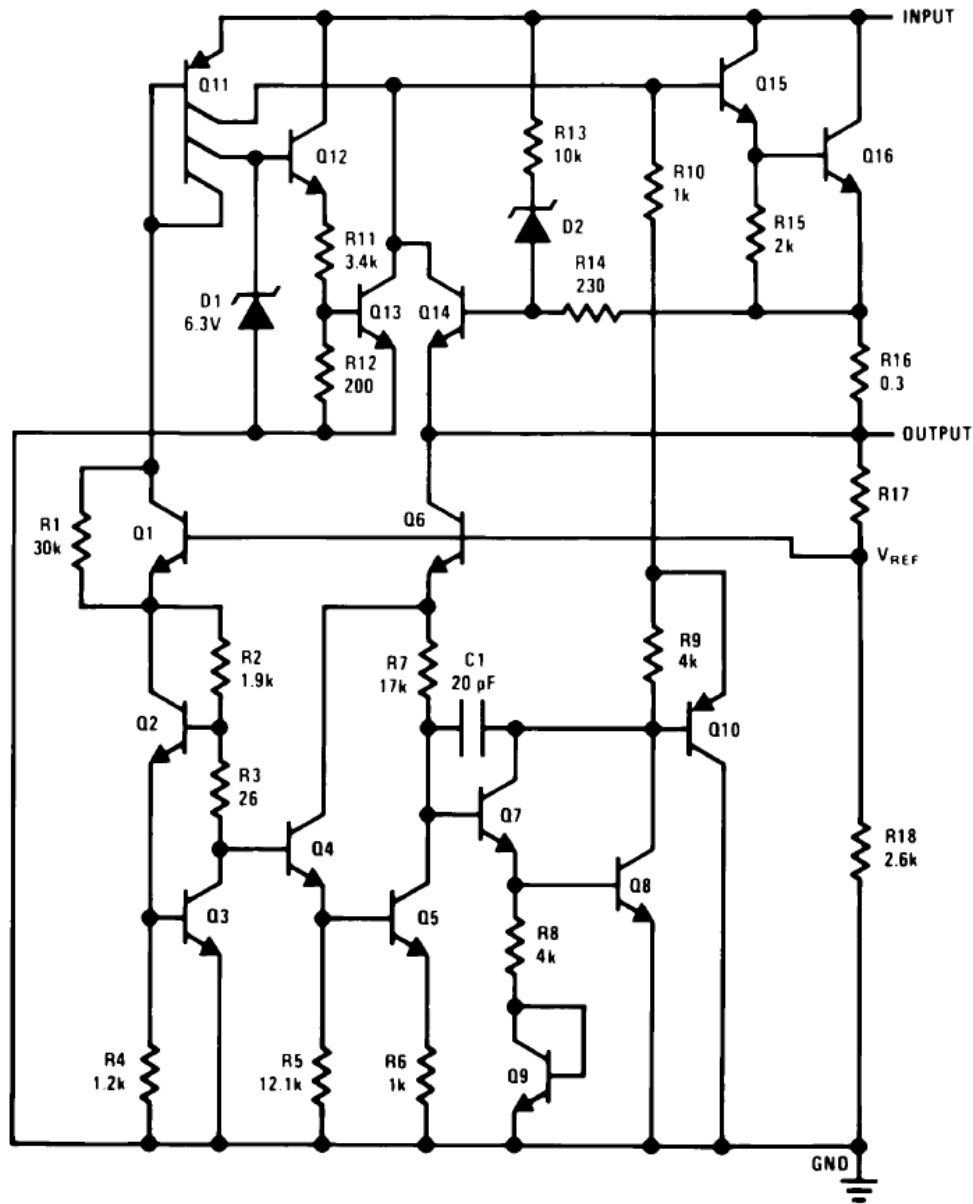


Fig. 13

Major blocks of the 7812 Voltage Regulator IC:

- Series-pass transistor (Q16)
- Stable Zener reference voltage
- Error amplifier
- Short-circuit protection

Source: 7812 Data sheet, National Semiconductor Corp., 2000

Features of an IC Regulator

- V_{out} will be steady for a large range of V_{in} and I_L values
- Minimum V_{in} to the IC regulator: $V_{out} + 2$ or 3 V (typical)
- A small value of capacitor, typically $1\ \mu\text{F}$ is put at the output for stability (i.e. to prevent oscillations)
 - The regulator IC uses a negative feedback error amplifier circuit, which could result in instability.

Other Popular Three-terminal Voltage Regulator ICs

- Positive Voltage Regulator ICs
 1. 7805 : $V_{\text{out}} = 5 \text{ V}$
 2. 7806 : $V_{\text{out}} = 6 \text{ V}$
 3. 7809 : $V_{\text{out}} = 9 \text{ V}$
- Negative Voltage Regulator ICs
 1. 7905 : $V_{\text{out}} = -5 \text{ V}$
 2. 7906 : $V_{\text{out}} = -6 \text{ V}$
 3. 7909 : $V_{\text{out}} = -9 \text{ V}$
 4. 7912 : $V_{\text{out}} = -12 \text{ V}$