
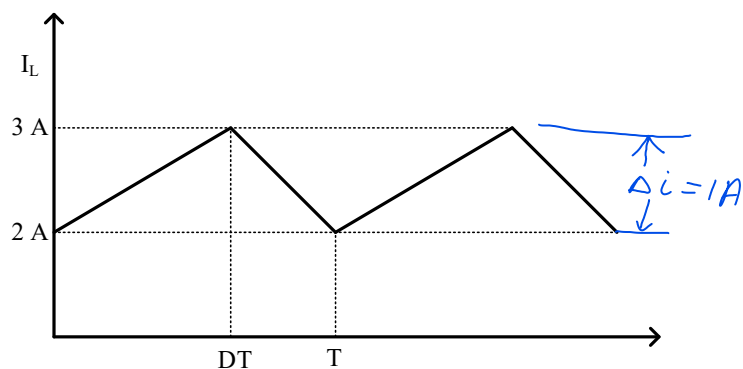


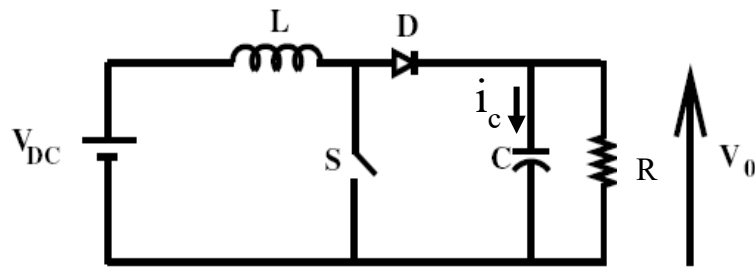1. For the boost converter shown in figure $V_{DC}=30\text{ V}$
 $V_O=60\text{ V}$, switching frequency= 100 kHz . Assume
 that V_O is held constant for a-b.



$$a) V_O = \frac{V_{in}}{1-D}$$

$$\Rightarrow D = \frac{V_O - V_{in}}{V_O} = \underline{0.5}$$

$$b) L \frac{\Delta i}{\Delta t} = V_L$$


$$\Rightarrow V_{in} = L \times \frac{\Delta i}{DT_s}$$

$$L = \frac{V_{in} DT_s}{\Delta i}$$

$$= \frac{30 \times 0.5 \times 10^{-5}}{1\text{ A}}$$

$$= \underline{150 \mu\text{H}}$$

- Duty Cycle. **(0.5-mark)**
- Value of L in μH . **(0.5-mark)**
- Sketch the labelled waveform of current flowing through the capacitor assuming that charging current is +ve. (Credit will be given only if the waveform is correct. No partial credit). **(1-mark)**
- Sketch the variation of V_O assuming that current through RL remains constant. Note that nature of variation may not be important. (No partial credit). **(1-mark)**

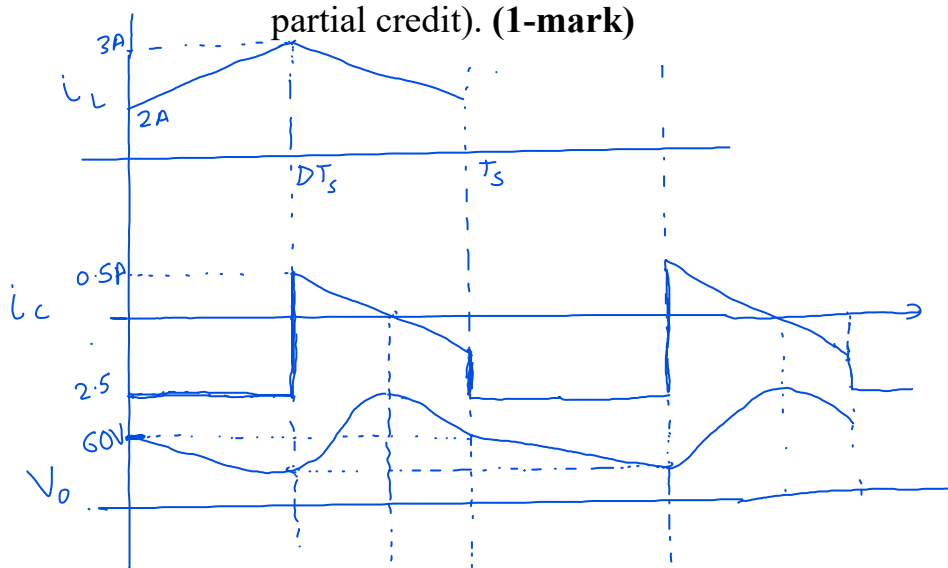

2. A single phase full bridge VSI is feeding a purely inductive load as shown. Where T_1 - T_4 are transistors and D_1 - D_4 are feedback diodes. Also note that having turned on each pair of devices is maintained in that state for π radians. The frequency of the voltage applied to the load is 50 Hz.

$$f_s = 50 \text{ Hz}$$



$$\therefore T_s = \frac{1}{50} = 20 \text{ msec}$$

2π rad in one T_s .

$$\therefore \pi \text{ rad is } \frac{T_s}{2} = 10 \text{ msec}$$

$$\therefore x = 10 \text{ msec}$$

$$y = 20 \text{ msec}$$

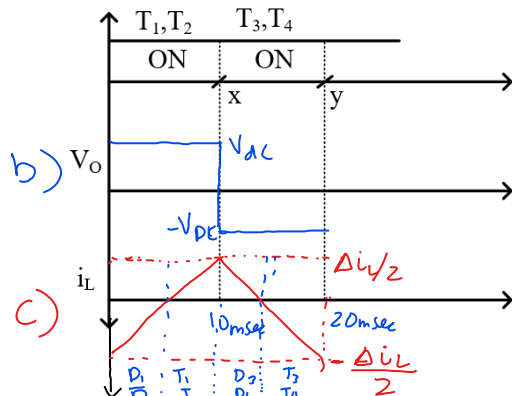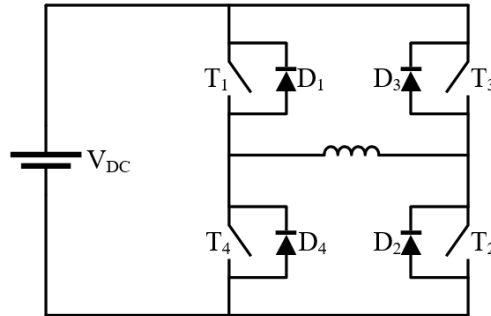

$$\Delta i_L = \frac{V_{DC} \times \Delta t}{L} = \frac{V_{DC} \times 10 \times 10^{-3}}{L}$$

- Determine x and y in m sec. **(0.5-mark)**
- Draw the labelled waveform of voltage applied to the load. **(0.5-mark)**
- Draw the labelled load current waveform, assuming that steady state is achieved and average value of load current is zero. **(1-mark)**
- Determine the time duration (in m sec) of conduction of transistor T_1 and diode D_1 . **(1-mark)**

both T_1 & D_1 will be conducting for 5 msec

$$V_o = \frac{50}{1-0.5} = 100 \text{ V} \neq 150 \text{ V}$$

\therefore converter is operating in DCM

$$a) V_{in} = L \frac{\Delta i}{\Delta t} = V_L$$

$$= L \frac{\Delta i}{D T_s}$$

$$50 = 10 \times 10^{-6} \frac{\Delta i}{0.5 \times 10^{-5}}$$

$$\Rightarrow \Delta i = \underline{\underline{25 \text{ A}}}$$

Also

$$V_o - V_{in} = V_L = L \frac{\Delta i}{\Delta t}$$

$$150 - 50 = 10 \times 10^{-6} \times 25 \frac{1}{(\beta - D) T_s}$$



$$100 = \frac{10^{-5} \times 25}{(\beta - 0.5) 10^{-5}}$$

$$(\beta - 0.5) = 0.25$$

$$\therefore \underline{\underline{\beta = 0.75}}$$

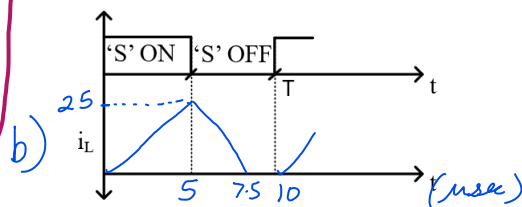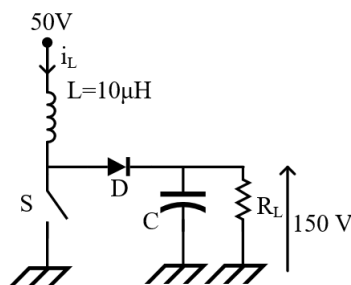3. The boost converter shown in figure operates with a duty cycle of 0.5 and switching frequency = 100 kHz. Determine:

- The time in μsec for which diode D is conducting. **(1-mark)**
- Draw the labelled inductor current waveform. **(1-mark)**



4. Suggest a circuit for buck-boost converter which can transfer power in both the directions, i.e. power can flow from low-voltage side to high-voltage side, as well as from high-voltage side to low-voltage side. **(1-mark)**

5. In one case, a regulated 5-volt supply is obtained using a linear regulator (e.g. LM7805 IC). In other case, a switching regulator is used to obtain regulated 5-volt supply. For both the cases, qualitatively plot the efficiency curve as a function of input voltage. **(1-mark)**


\therefore Diode will be conducting for $(\beta - D) T_s$ duration

$$= 0.25 \times 10^{-5}$$

$$= \underline{\underline{2.5 \mu\text{sec}}}$$

4. Suggest a circuit for buck-boost converter which can transfer power in both the directions, i.e. power can flow from low-voltage side to high-voltage side, as well as from high-voltage side to low-voltage side.

(1-mark)

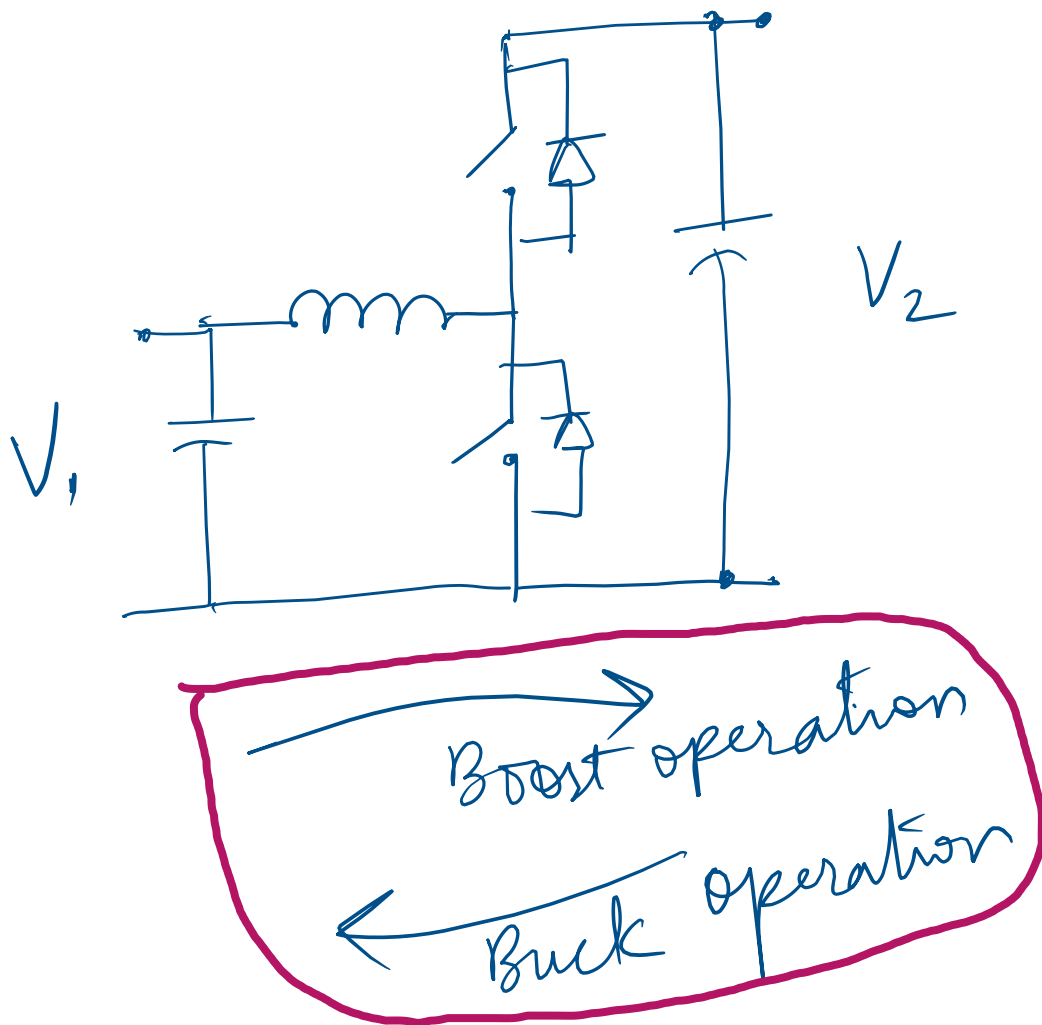

5. In one case, a regulated 5-volt supply is obtained using a linear regulator (e.g. LM7805 IC). In other case, a switching regulator is used to obtain regulated 5-volt supply. For both the cases, qualitatively plot the efficiency curve as a function of input voltage.

(1-mark)

