
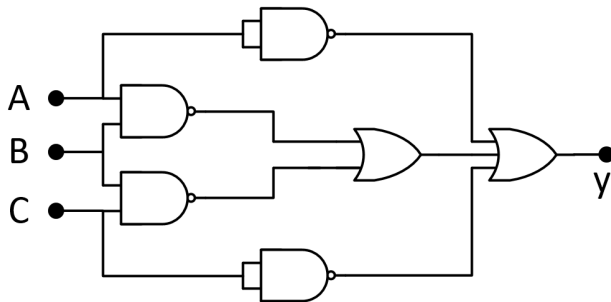


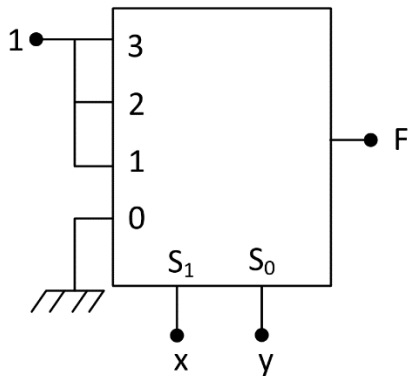1. For the logic circuit shown, the simplified expression for output y is _____




2. The output F in terms of x & y for the 4-1 MUX shown in figure is _____



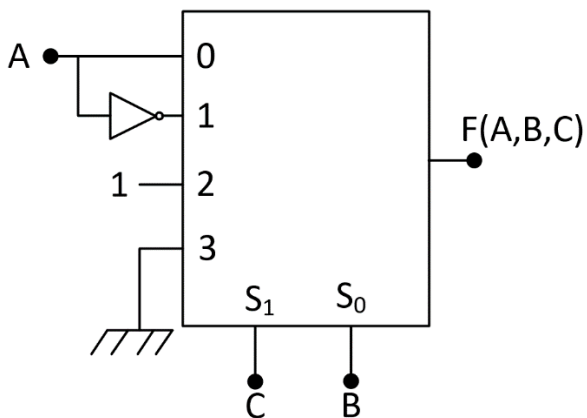3. 4-1 MUX is used to implement a 3 input Boolean function as shown in figure. The Boolean function $F(A,B,C)$ implemented is _____

{Write in terms of $F(A,B,C)=\Sigma(x, x, x, \dots, x)$ }



4. A 3-bit code converter is required which would cyclically add 3 to input code. i.e. 000 should be converted to 011, ... , 111 to 010. Assume that input and output codes to be 'CBA' and 'RQP' respectively.

<u>Inputs</u>			<u>Outputs</u>		
C	B	A	R	Q	P
0	0	0	0	1	1
⋮	⋮	⋮	⋮	⋮	⋮
1	1	1	0	1	0

- Write the truth table for input and output conditions
- Obtain the minimized function using K-Map
(Hint: for 3 K-Maps function output R, Q & P)