

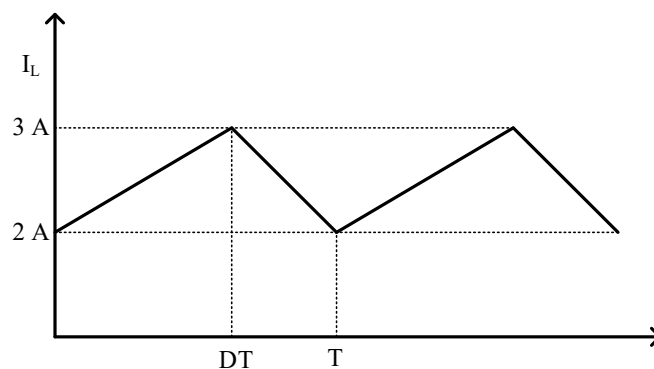


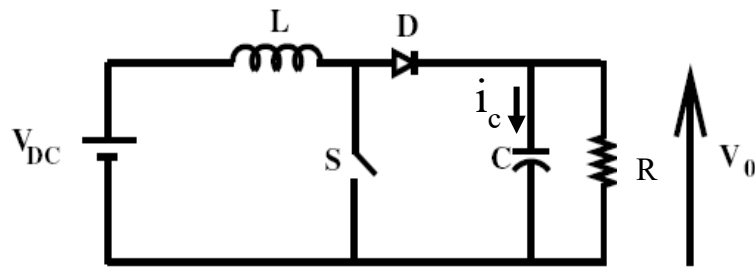1. For the boost converter shown in figure $V_{DC}=30\text{ V}$
 $V_O=60\text{ V}$, switching frequency= 100 kHz . Assume
 that V_O is held constant for a-b.



- Duty Cycle. **(0.5-mark)**
- Value of L in μH . **(0.5-mark)**
- Sketch the labelled waveform of current flowing through the capacitor assuming that charging current is +ve. (Credit will be given only if the waveform is correct. No partial credit). **(1-mark)**
- Sketch the variation of V_O assuming that current through RL remains constant. Note that nature of variation may not be important. (No partial credit). **(1-mark)**

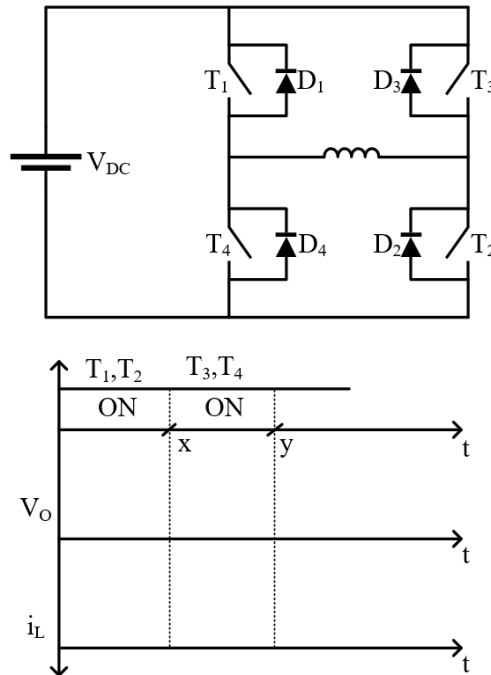2. A single phase full bridge VSI is feeding a purely inductive load as shown. Where T_1 - T_4 are transistors and D_1 - D_4 are feedback diodes. Also note that having turned on each pair of devices is maintained in that state for π radians. The frequency of the voltage applied to the load is 50 Hz.




- Determine x and y in m sec. **(0.5-mark)**
- Draw the labelled waveform of voltage applied to the load. **(0.5-mark)**
- Draw the labelled load current waveform, assuming that steady state is achieved and average value of load current is zero. **(1-mark)**
- Determine the time duration (in m sec) of conduction of transistor T_1 and diode D_1 . **(1-mark)**

Check whether the i_L is getting 0 before the cycle or not.



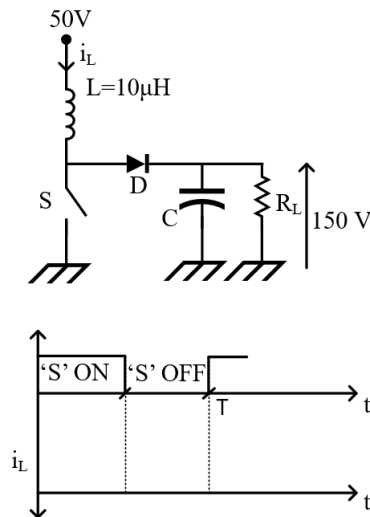3. The boost converter shown in figure operates with a duty cycle of 0.5 and switching frequency = 100 kHz. Determine:

- The time in μsec for which diode D is conducting. **(1-mark)**
- Draw the labelled inductor current waveform. **(1-mark)**



4. Suggest a circuit for buck-boost converter which can transfer power in both the directions, i.e. power can flow from low-voltage side to high-voltage side, as well as from high-voltage side to low-voltage side. **(1-mark)**



5. In one case, a regulated 5-volt supply is obtained using a linear regulator (e.g. LM7805 IC). In other case, a switching regulator is used to obtain regulated 5-volt supply. For both the cases, qualitatively plot the efficiency curve as a function of input voltage. **(1-mark)**