

Name: _____

Roll No.: _____

Signature: _____

EE103: 2022-2023/I (Autumn)

Quiz-2 Digital Electronics *SOLUTION*

December 05, 2022. (Monday)

Marks: 10

Time: 5:30 PM- 6:00 PM

1. The output expression for the K map shown in figure is _____.

(1 Mark)

RS PQ	00	01	11	10
00		1	1	
01	1	1	1	1
11	1	1	1	1
10			1	1

$$F = S + Q\bar{R} + PR$$

2. In the circuit shown below
- $\beta = 99$
- and
- $V_{CE} = 9$
- V. Determine the ratio
- $\frac{R_b}{R_c}$
- .

(1 Mark)


$$I_c = I - I_B = \beta I_B$$

$$I = (\beta + 1) I_B \quad \text{--- (5)}$$

substitute (3) & (4) in (5)

$$\frac{1}{R_c} = \frac{(99+1) \times 8.3}{R_B}$$
 
$$\frac{R_b}{R_c} = \underline{\underline{830}} \quad \leftarrow 0.5$$



$$I = I_c + I_B \quad \text{--- (1)}$$

$$I_c = \beta I_B \quad \text{--- (2)}$$



$$10 - R_c I = 9 \Rightarrow I = \frac{1}{R_c} \quad \text{--- (3)}$$

$$9 - R_b I_B - 0.7 = 0 \Rightarrow I_B = \frac{8.3}{R_B} \quad \text{--- (4)}$$

3. Assume that all the outputs are cleared prior to occurrence of first rising edge of the clock determine the ratio of
- F_{out}/F_{clk}
- .

Where F_{out} is the frequency of output and F_{clk} is the frequency of the clock.

(1 Mark)

  

This is a MOD 5 counter

$$\therefore \frac{F_{out}}{F_{clk}} = \frac{1}{5} \quad \leftarrow 0.5$$

4. The OPAMP shown in the figure are ideal and they are suitably biased. Determine the following

A. V_{out1} . B. V_{out} .

(2 Marks)

$$V_{i+} = 1V \Rightarrow V_{i-} = 1V$$

$$\therefore \frac{V_{out1} - 1}{1k} = \frac{1 - (-2)}{1k}$$


$$V_{out1} = 4V$$

OPAMP 2 is non inverting Amp

$$\therefore V_{out} = \left(1 + \frac{1k}{1k}\right) V_{out1}$$

$$= 2 \times 4V$$


$$\underline{\underline{V_{out} = 8V}}$$

 

5. In a sequential circuit, the initial state (before the 1st clock pulse) of the circuit is $Q_1Q_0 = 00$. Write down the truth table for the first five clock pulses and therefore what would be the state (Q_1Q_0) at the end of 33rd clock pulse. Note that $J_0 = \overline{Q_1}$, $K_0 = Q_1$, $J_1 = Q_0$, $K_1 = \overline{Q_0}$. (3.5 Marks)

J_0^n	K_0^n	Q_0^n	J_1^n	K_1^n	Q_1^n	Q_0^{n+1}	Q_1^{n+1}
1	0	0	0	1	0	1	0
1	0	1	1	0	0	1	1
0	1	1	1	0	1	0	1
0	1	0	0	1	1	0	0
1	0	0	0	1	0	1	0

MOD 4 counter

 

at the end of 33rd clock pulse it would be at $\text{MOD}(\frac{33}{4}) = 1^{\text{st}}$ state
 $\therefore Q_1, Q_0 = 01$

3

6. The digital circuit shown in figure generates a modified clock pulse at the output 'y'. Draw the output waveform on the graph provided to you below. Assume initial $Q=1$. (1.5 Marks)

