

Introduction to Electrical Engineering

Course Code: EE 103

Department: Electrical Engineering

Instructor Name: B. G. Fernandes

E-mail id: bgf@ee.iitb.ac.in



Review : K- MAP

- In K-Map, squares are labelled so that horizontally adjacent squares differ only in one variable.

Eg: Upper left-hand square in the 4 – variable map is $\bar{A} \bar{B} \bar{C} \bar{D}$, while the square immediately to its right is $\bar{A} \bar{B} \bar{C} D$.

Similarly vertically adjacent squares differ only in one variable. Square directly below $\bar{A} \bar{B} \bar{C} \bar{D}$ is $\bar{A} B \bar{C} \bar{D}$.

- Note that each square in the top row is considered to be adjacent to a corresponding square in the bottom row.

Eg: $\bar{A} \bar{B} C D$ square in the top row is adjacent to $A \bar{B} C D$ square in the bottom row.

Therefore In order for vertically and horizontally adjacent squares to differ in only one variable it must be

$\bar{A} \bar{B} \quad \bar{A} B \quad A B \quad A \bar{B}$ and $\bar{C} \bar{D} \quad \bar{C} D \quad C D \quad C \bar{D}$


CD \ AB	00	01	11	10
00				
01				
11				
10				

	$\bar{C} \bar{D}$	$\bar{C} D$	$C D$	$C \bar{D}$
$\bar{A} \bar{B}$				
$\bar{A} B$				
$A B$				
$A \bar{B}$				




Review : MULTIPLEXER

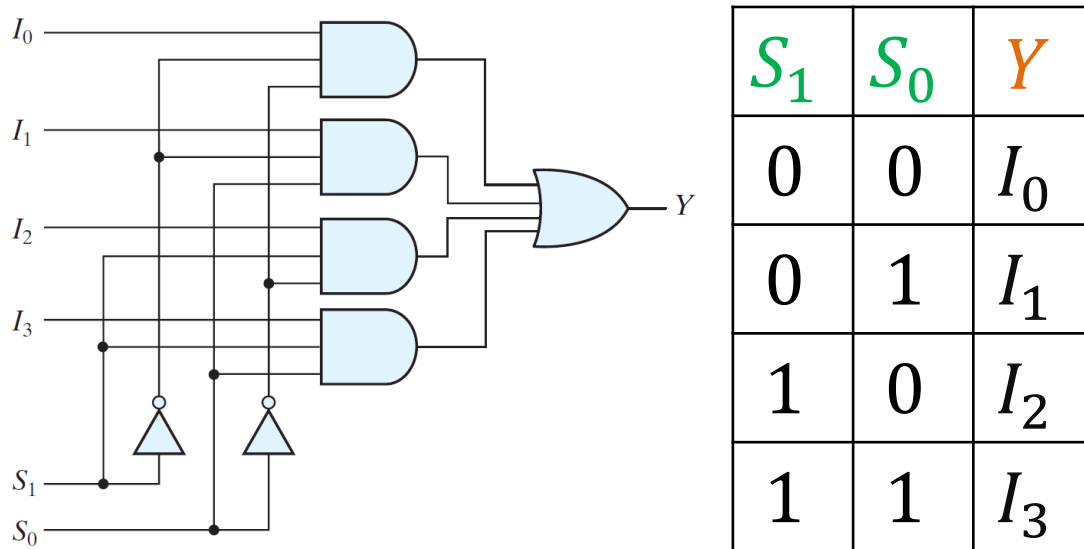- Logic circuit accepts several data inputs. But allows only one of them at a time to get through the o/p.
- Routing of the desired input to the o/p is done by 'select' inputs or 'address' inputs.



Four-to-one-line multiplexer

 

Implementation of Boolean expressions using Multiplexers (MUX)

- In a practical circuit, the number of ICs should be minimized; K-map solution requires a combination of gates, with differing number of inputs - which in most cases will not result in the minimum number of ICs.

Another Solution:

- A 4-to-1 MUX can directly implement the Truth Table of a TWO variable function using its TWO selection inputs and Input lines.
- Similarly, an 8-to-1 MUX can directly implement the Truth Table of a THREE variable function using its THREE selection inputs;
- A 16-to-1 MUX can implement the Truth table of a FOUR variable function using its FOUR selection inputs.
- It is more efficient to implement a Boolean function of n variables using a MUX that has $(n-1)$ selection inputs.



Multiplexer: Example 1

There are 3 input variables and we are using two of them to get a output regardless of the value of third variable.

Implement using 4-to-1 multiplexer: $F(x, y, z) = \sum(1, 2, 6, 7)$


Address lines			F	
x	y	z		
0	0	0	0	$F = z$
0	0	1	1	
0	1	0	1	$F = \bar{z}$
0	1	1	0	
1	0	0	0	$F = 0$
1	0	1	0	
1	1	0	1	$F = 1$
1	1	1	1	

Truth table

Logic :

If $xy = 0$, $F = z$
 If $xy = 1$, $F = \bar{z}$
 If $xy = 2$, $F = 0$
 If $xy = 3$, $F = 1$

 Might have to remember the output corresponding to particular decimal number.




Multiplexer implementation



Multiplexer: Example 2

Implement using 8-to-1 multiplexer: $F(A, B, C, D) = \sum(1, 3, 4, 11, 12, 13, 14, 15)$



Address lines					
<i>A</i>	<i>B</i>	<i>C</i>	<i>D</i>		<i>F</i>
0	0	0	0	0	$F = D$
0	0	0	1	1	
0	0	1	0	0	$F = D$
0	0	1	1	1	
0	1	0	0	1	$F = \bar{D}$
0	1	0	1	0	
0	1	1	0	0	$F = 0$
0	1	1	1	0	
1	0	0	0	0	$F = 0$
1	0	0	1	0	
1	0	1	0	0	$F = D$
1	0	1	1	1	
1	1	0	0	1	$F = 1$
1	1	0	1	1	
1	1	1	0	1	$F = 1$
1	1	1	1	1	

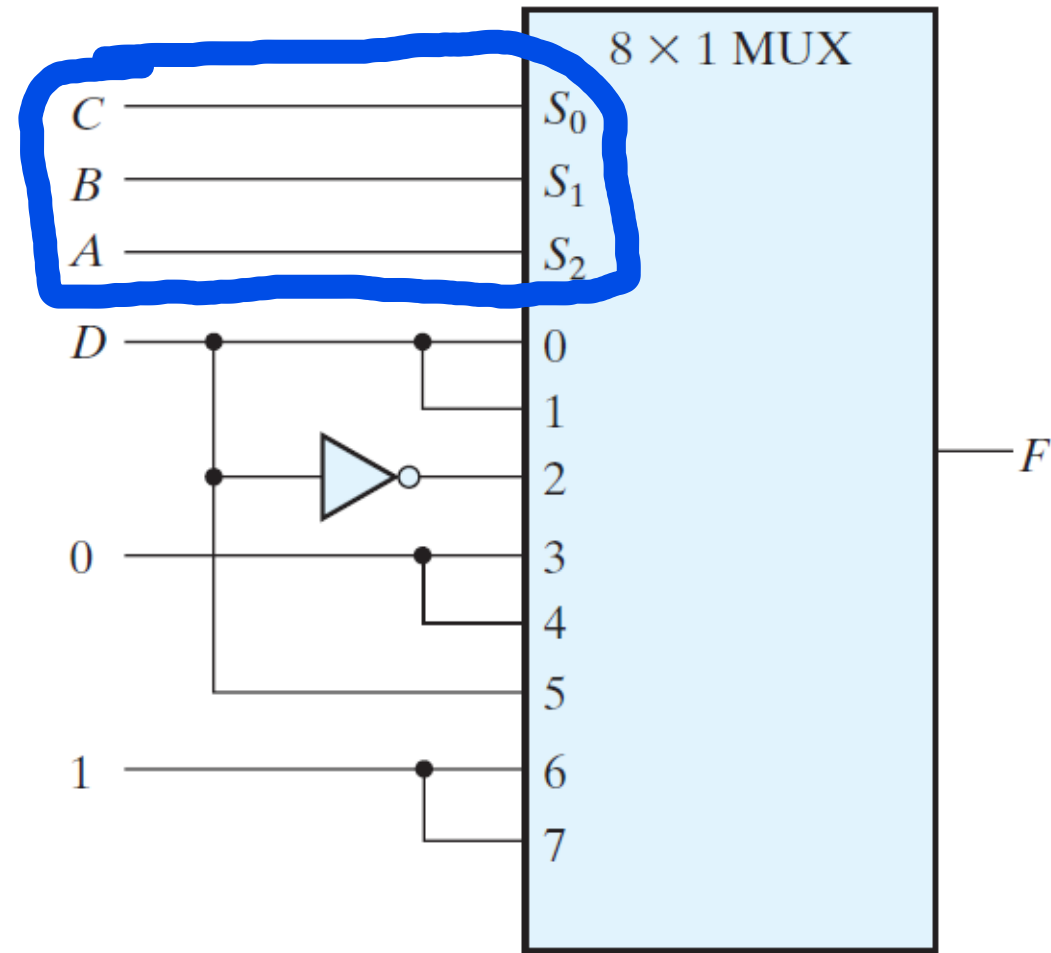

Multiplexer vs Demultiplexer


Multiplexer: takes several inputs and transmits one of them to the output.

  Demultiplexer (DeMUX): takes single input and distributes it over several outputs.




Decoder

 A logic circuit that converts an N-bit binary input code into M output lines
Each output line is activated for only one of the possible combinations of Inputs



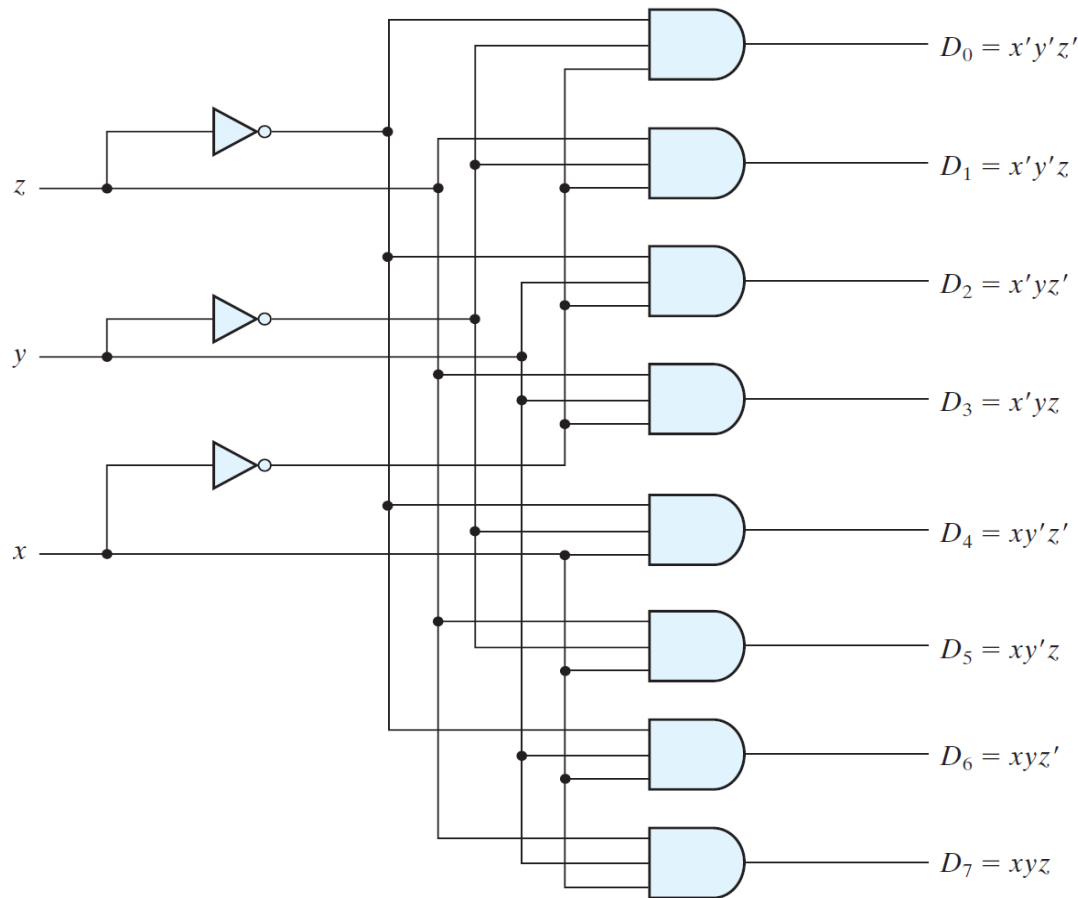3 to 8 line Decoder → 3 input and 8 output lines or
 1-of-8 Decoder → Only 1 of the 8 outputs is activated



Inputs			Outputs							
x	y	z	D_0	D_1	D_2	D_3	D_4	D_5	D_6	D_7
0	0	0	1							
0	0	1		1						
0	1	0			1					
0	1	1				1				
1	0	0					1			
1	0	1						1		
1	1	0							1	
1	1	1								1

IC - 74LS138 is a popular 3-to8 decoder






BCD to 7 Segment Decoder

Binary Coded Decimal

4 bit BCD input.

  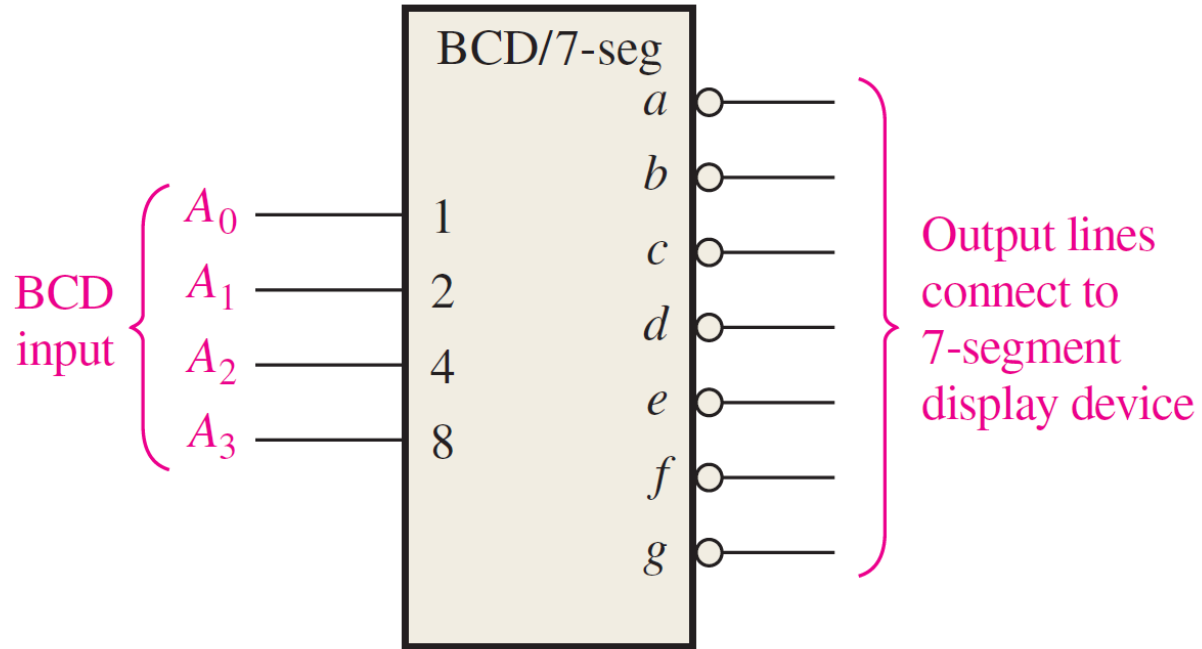According to the input it provides the output that pass current through the appropriate segments




Sequential Circuits

- Combinatorial circuits: Output at any instant of time are dependent on the input levels present at that time.
(Eg: Gates, MUX, Decoder)
Prior input conditions have no effect on the present output
⇒ No memory
- Sequential circuits: Output depends on the present set of inputs and also on the past output (Eg: Latches, Flip-flops, Digital Clocks)




S-R Latch

 
An electronic device that changes its output immediately on the basis of the applied input.
One can use it to store either 0 or 1 at a specified time



 Normal operation $S=R=1$; Assume $Q = 0 \therefore \bar{Q} = 1$
($Q = 1 ; \bar{Q} = 0$ is also possible)



 If $Q = 1 ; \bar{Q} = 0$, No change in output



Instead if $Q = 1 , \bar{Q} = 0$
 Q Becomes 0 and $\bar{Q} = 1$

Making $S=R=0$ is not allowed
 $\Rightarrow Q = \bar{Q} = 1$




Truth table of S-R Latch:


S	R	output
1	1	No change (Hold)
0	1	$Q = 1$
1	0	$Q = 0$
0	0	invalid

The output remains the same as of the previous one.

 The output changes only when the value of one of the variables changes from 1 to 0.



 Instead of NAND latch we can have NOR latch also.
Replace NAND gate by NOR gate



Truth table of NOR latch

S	R	output
0	0	No change (Hold)
1	0	$Q = 1$
0	1	$Q = 0$
1	1	invalid

Flip-Flop:

- ⇒ Made up of an assembly of logic gates.
- ⇒ Logic gates have no storage capacity.
- ⇒ Can be connected together in ways that permit information to be stored.
- ⇒ Bistable multivibrator latch

Digital systems can operate either asynchronously or synchronously.

Asynchronous ⇒ Output can change any time. No common clock; output of previous flip flop is used as new clock; slower; more errors; aka Serial counter; easy to use.
⇒ Difficult to troubleshoot.


Synchronous Same clock is applied to each flip flop; faster; less errors; aka Parallel counter; hard to use.

The exact time at which output can change is determined by a signal “clock”

PET ⇒ Positive Edge Trigger




symbol

 

NET ⇒ Negative Edge Trigger




symbol

 

Clocked S-R Flip-Flop


S - R Latch with a clock.

 

Truth table

= That of NOR Latch



S	R	Clk	Q
0	0	↑	Q(Hold)
1	0	↑	1
0	1	↑	0
1	1	↑	invalid

 

Depending upon the inputs,
output will change only at the ↑ of the clock



Clocked S-R Flip-Flop

  

Instead of PET (\rightarrow), if NET was used (\rightarrow) output changes at \downarrow

