

Introduction to Electrical Engineering

Course Code: EE 103

Department: Electrical Engineering

Instructor Name: B. G. Fernandes



E-mail id: bgf@ee.iitb.ac.in



Review:

DC machines:
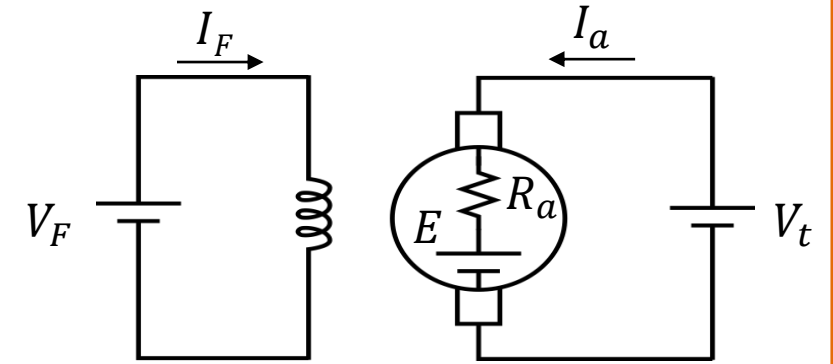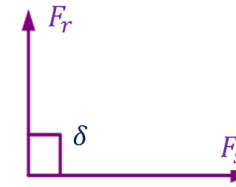
$$EI_a = V_t I_a - I_a^2 R_a$$
$$T = \frac{EI_a}{\omega} = \frac{(K\phi\omega)I_a}{\omega} = K\phi I_a$$



- In DC machine → Stator field is 'time-invariant'
→ Stator winding is concentrated and connected to a DC supply

Induction(Asynchronous) machines:

- The result of displacing 3 windings by 120° in **space** and displacing the winding 'I' by 120° in **time phase** is a **single revolving field of constant magnitude**
- For a given winding arrangement, **speed of rotation** is determined by **supply frequency** of the input alone
- This speed of rotation of field is called '**synchronous speed**' and it is denoted by N_s
- N_r can not be = N_s because at $N_r = N_s$, relative speed between rotor (conductor) and stator field is zero
→ no emf, and therefore, no 'I' and no force or torque
- $N_s - N_r$ → slip speed


$$N_s = \frac{120f}{P}$$

$$\text{Slip: } S = \frac{N_s - N_r}{N_s}$$



Review (cont.):

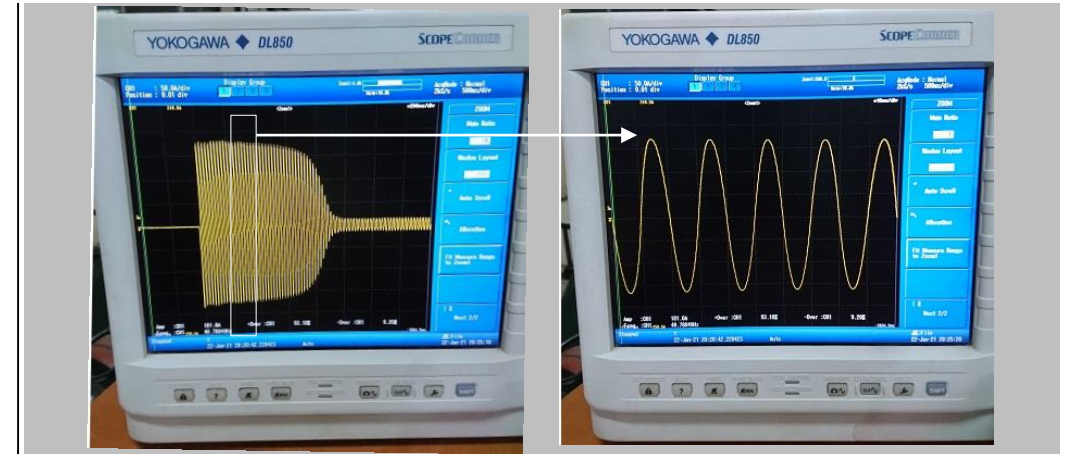- At starting, relative speed between field and conductor (rotor) is maximum,
→ induced emf, and therefore, rotor ' I ' is maximum.
- Now, for any current in rotor there is an equivalent ' I ' in stator
∴ if an IM is started at rated ' V ' & ' f ', a high ' I ' will be drawn from the source



Induction motor started at rated ' V ' & ' f '

→ This high ' I ' could be $\cong (6 - 7)$ times the rated current of motor

- At steady state, $T_e = T_L$ (neglecting friction)
- N_s can be changed by changing the supply frequency.
- To reduce the speed, ' f ' ↓ Recall that: $V = 4.44f\phi_m N_{\text{turns}}$
- If the ' V ' is kept constant and ' f ' is reduced, ϕ_m tries to ↑ → this should not be done
- Instead, ϕ_m is kept constant. This can be done by keeping $\frac{V}{f} = \text{constant} \Rightarrow$ both, ' V ' and ' f ' are changed




DC – DC conversion




DC-DC Conversion

How to convert dc input of 30 V to 5 V output?

→ Use potential divider

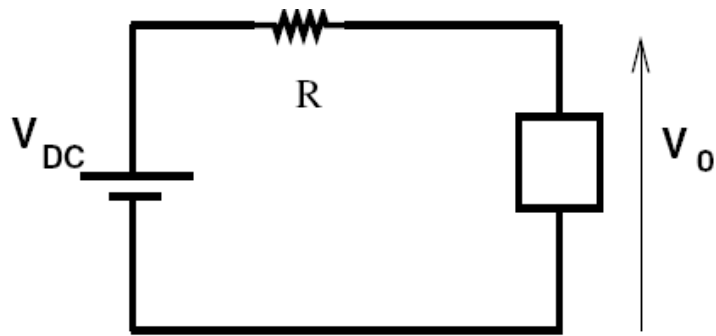

→ Use a linear voltage regulator '7805'

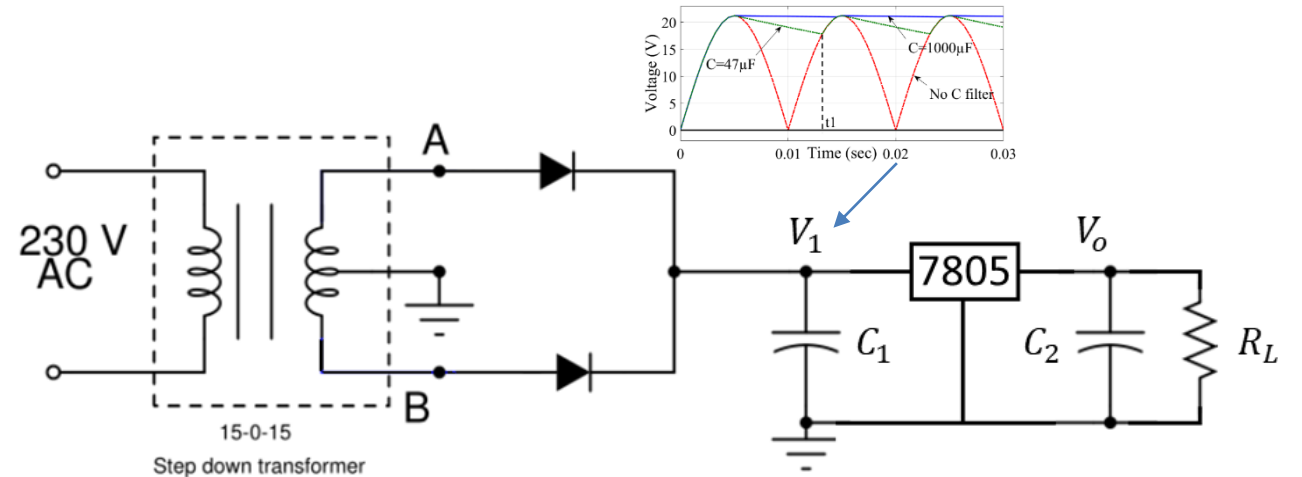


V_1 can range from 7 to 35 V

But, unnecessary power losses in R and in the '7805' IC
Can this be avoided?

DC-DC Conversion

How can a circuit change the voltage level, yet dissipate low power?

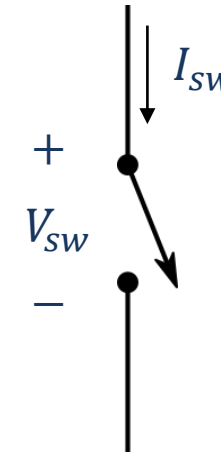- Circuit elements $\rightarrow R, L, C \rightarrow$ Passive
- L & $C \rightarrow$ do not consume power
- Power loss in a switch' $= V_{SW} \times I_{SW}$
 - When switch is open, $I_{SW} = 0$
 - When switch is closed, $V_{SW} \rightarrow$ Very low
 - Power loss ≈ 0



- Resistor results in power dissipation
- For high efficiency, a power switch with low on-state voltage drop must be used
- In addition, use only L & C elements



DC-DC Conversion



How can a circuit change the voltage level, yet dissipate low power?

Operate the switch as follows


- Close to position '1' for some time and then transfer it to position '2'

$$V_O = V_{DC} \frac{T_1}{T_1 + T_2} = V_{DC} D$$

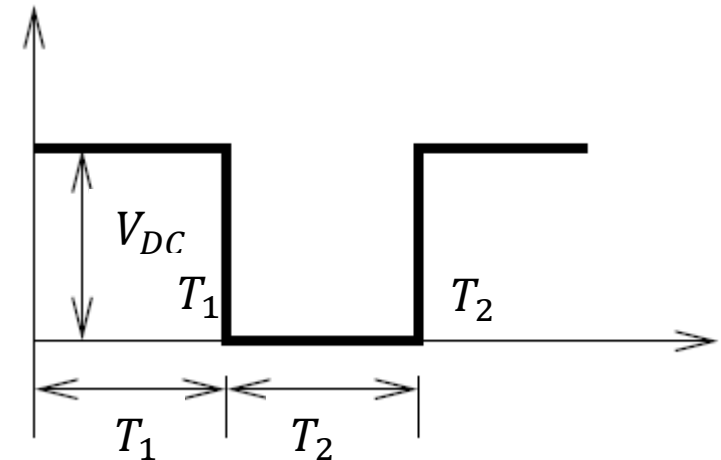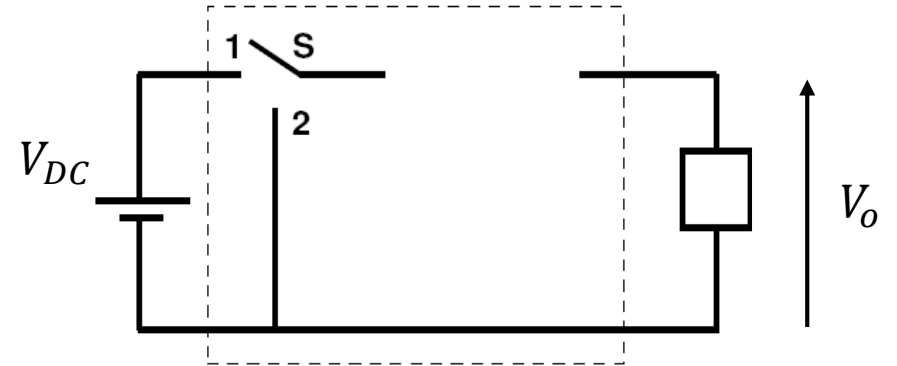- D is the duty cycle of the switch
- Power loss ≈ 0
 \therefore voltage drop across the device during ON period ≈ 0



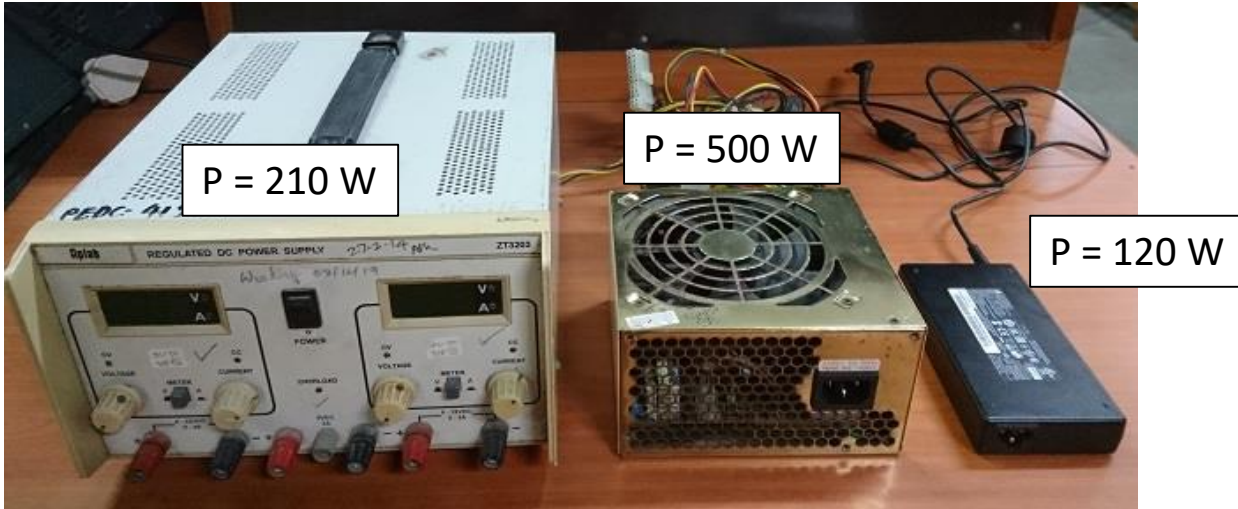DC-DC Conversion: Linear vs. switching power supply



DC-DC Conversion: Buck Converter

Following circuit is a buck converter

$L \rightarrow$ filter inductor


$C \rightarrow$ filter capacitor

' V_o ' is assumed to remain constant


Switch ' S ' is switched at a **very high** frequency

- S is ON for DT second
- S is OFF for $(1 - D)T$ second
- T is switching period, given by
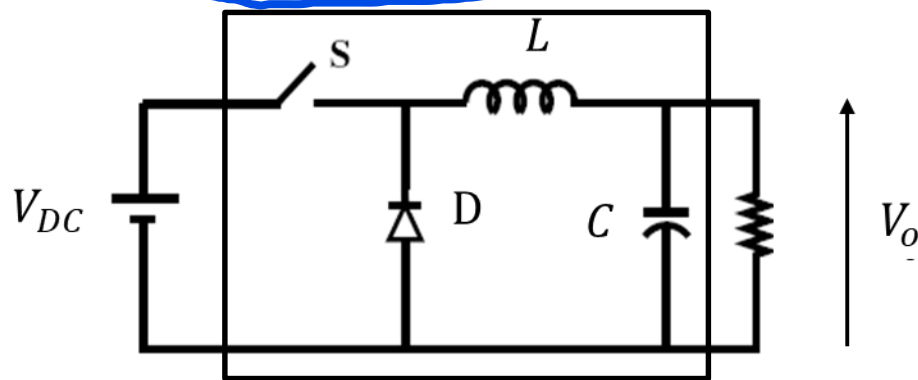
$$T = \frac{1}{f_{sw}}, \quad f_{sw}: \text{switching frequency}$$


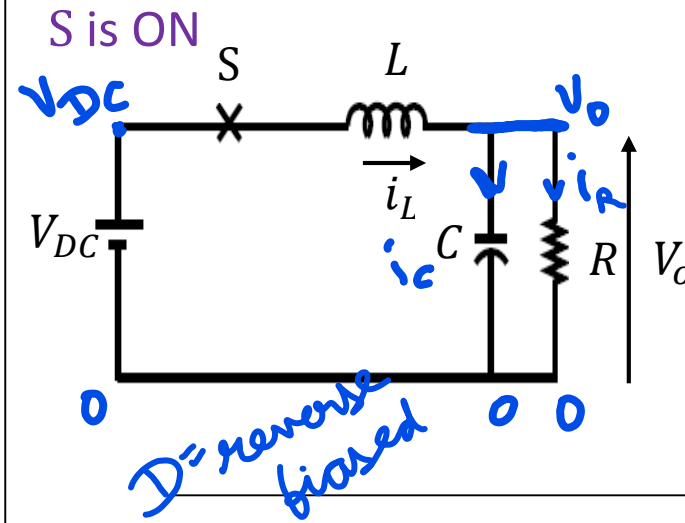
$$q_c = C V_o \Rightarrow I_c = C \frac{dV_o}{dt}$$



For, $0 < t < DT$

$$V_L = V_{DC} - V_o = \text{constant}$$


$\rightarrow i_L$ increases linearly

$$\rightarrow i_L = i_C + i_R \text{ (KCL)}$$

$$\rightarrow i_L = C \frac{dv_o}{dt} + \frac{v_o}{R}$$

$$\rightarrow V_D = -V_{DC}$$

$$V_S = 0$$

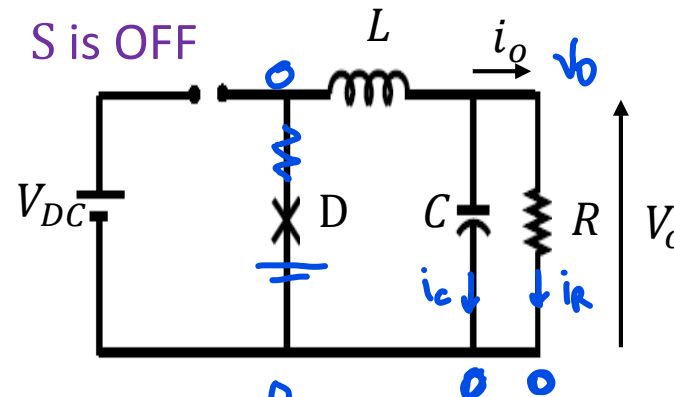

For, $DT < t < T$

$$V_L = -V_o = \text{constant}$$

$\rightarrow i_L$ decreases linearly


$$\rightarrow i_L = C \frac{dv_o}{dt} + \frac{v_o}{R}$$

$$\rightarrow V_S = V_{DC}$$

$$V_L = -V_o = L \frac{di_L}{dt} \Rightarrow \frac{di_L}{dt} = -\frac{V_o}{L} = c \quad V_S = 0$$



DC-DC Conversion: Buck Converter

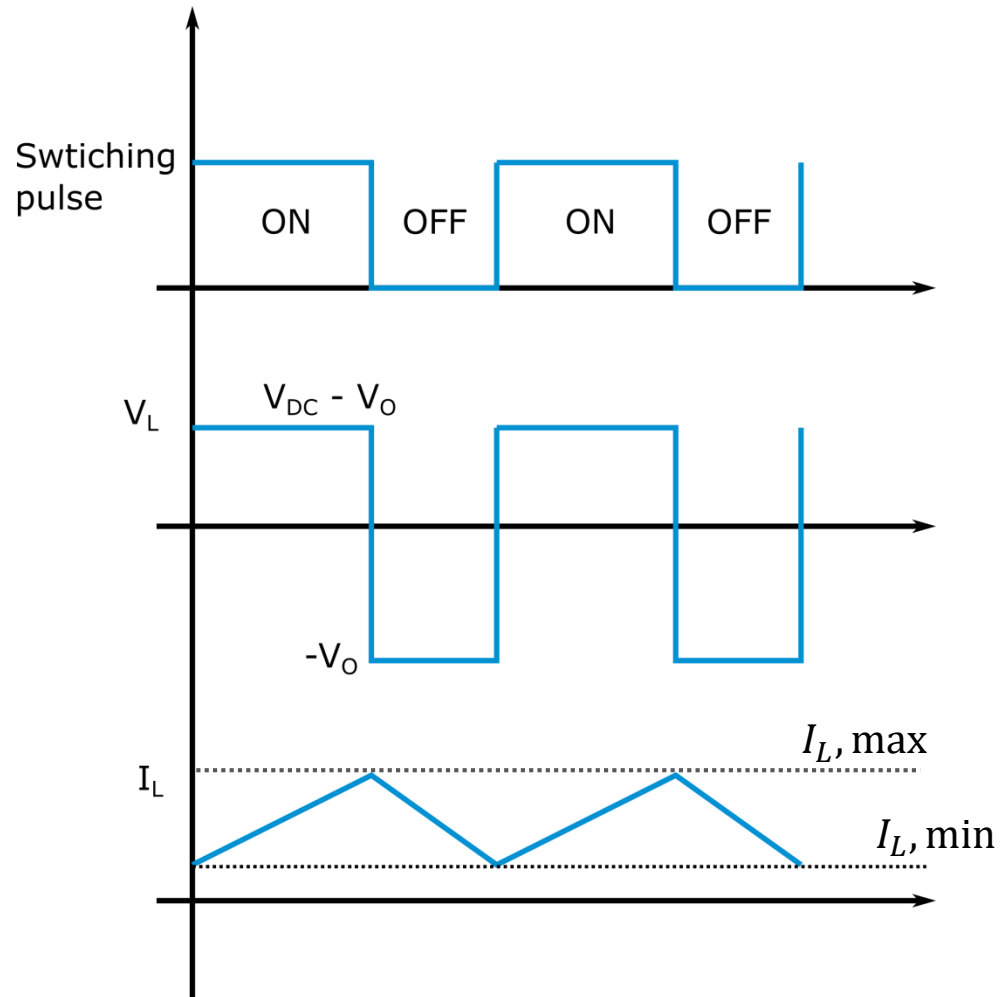

Assume i_L is continuous and **steady-state** is assumed

Average voltage across $L = 0$

$$\therefore (V_{DC} - V_O)DT = V_O(1 - D)T$$

$$V_O = DV_{DC}$$

➔ Buck Converter, **Output < Input**


not $I_L = \text{constant}$
but same cycle





DC-DC Conversion: Buck Converter output when 'D' changes

$V_{DC} = 30\text{ V}$,
 $L = 47\text{ }\mu\text{H}$,
 $C = 22\text{ }\mu\text{F}$,
 $R_L = 10\text{ }\Omega$

Why a jump?

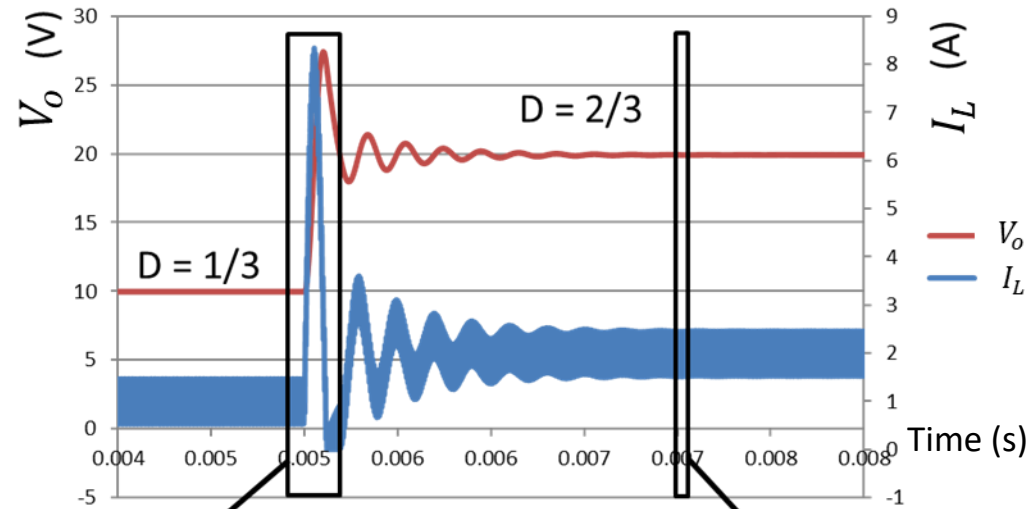

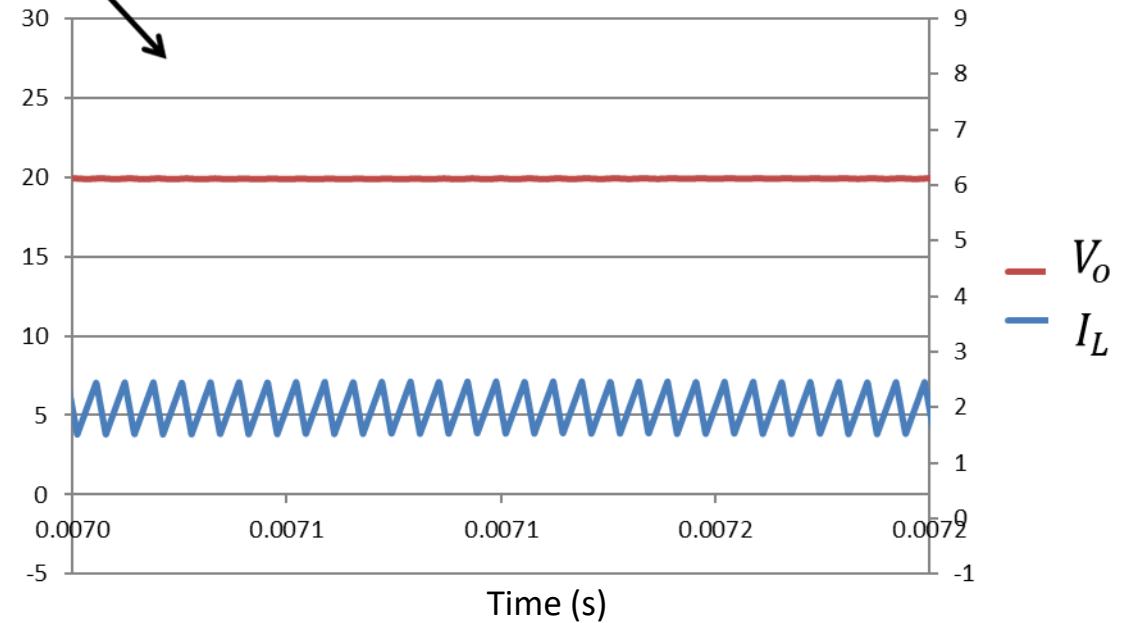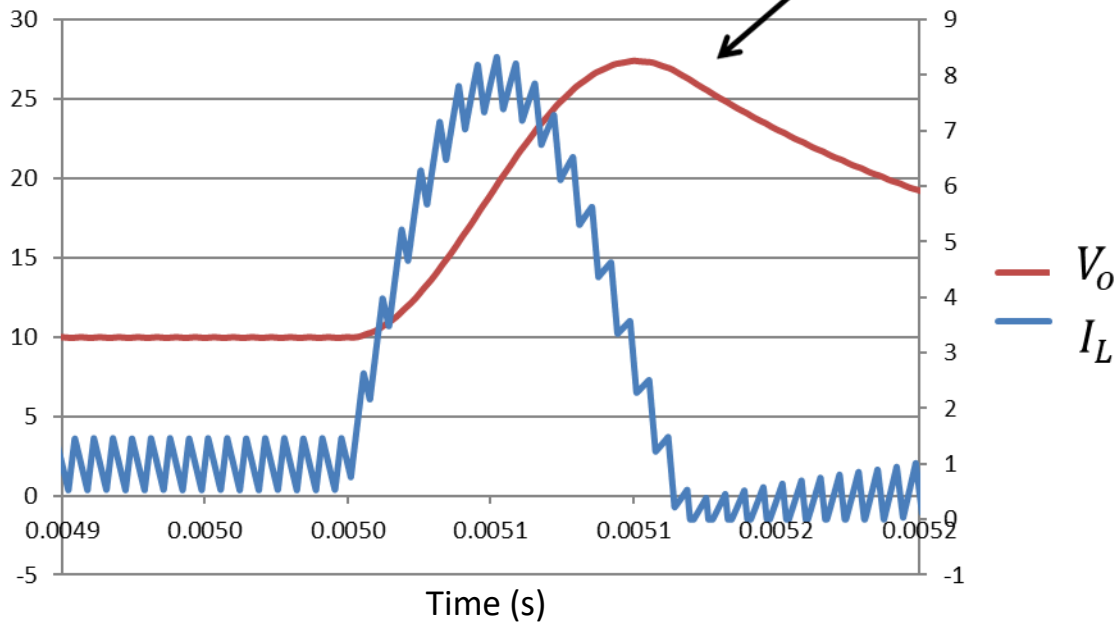- The relation: $V_o = DV_{DC}$ is valid during steady state only
- Notice the rise time in both the plots



DC-DC Conversion: Boost Converter

Following circuit is a boost converter

$L \rightarrow$ filter inductor

$C \rightarrow$ filter capacitor

' V_o ' is constant and ripple free

Switch 'S' is switched at a very high frequency

- S is ON for DT time
- S is OFF for $(1 - D)T$ time
- T is switching period,

$$T = \frac{1}{f_{sw}}, \quad f_{sw}: \text{switching frequency}$$

