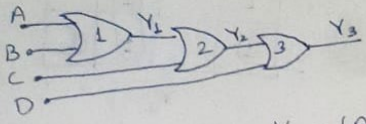



1. Implement a four-input OR gate using two-input OR gates only?

Ans 1 → Fig (a) is showing one possible arrangement of 2-input OR gate
A, B, C, D are the logic inputs & Y_3 is the output



The o/p of OR gate 1 is $Y_1 = (A+B)$
The o/p of OR gate 2 is $Y_2 = (Y_1 + C) = (A+B+C)$
The o/p of OR gate 3 is $Y_3 = (Y_2 + D) = (A+B+C+D)$

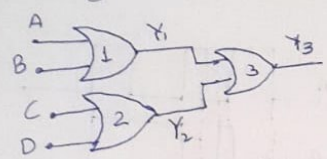→ Fig (b) showing another arrangement possible with 4-input



The o/p of OR gate 1 is, $Y_1 = (A+B)$
The o/p of OR gate 2 is, $Y_2 = (C+D)$
The o/p of OR gate 3 is, $Y_3 = Y_1 + Y_2 = (A+B+C+D)$

2. Simplify the following

- a) $(A \cdot B + C \cdot D) \cdot [(\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D})]$
b) $(1 + L \cdot M + L \cdot \bar{M} + \bar{L} \cdot M) \cdot [(L + \bar{M}) \cdot (\bar{L} \cdot M) + (\bar{L} \cdot \bar{M}) \cdot (L + M)]$

Ans 2 → a) $(A \cdot B + C \cdot D) \cdot [(\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D})]$
→ let $(A \cdot B + C \cdot D) = X$
Then $(\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) = \bar{X}$
The given expression reduced to $X \cdot \bar{X}$
∴ $(A \cdot B + C \cdot D) \cdot [(\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D})] = 0$


b) $(1 + L \cdot M + L \cdot \bar{M} + \bar{L} \cdot M) \cdot [(L + \bar{M}) \cdot (\bar{L} \cdot M) + (\bar{L} \cdot \bar{M}) \cdot (L + M)]$

- $(1 + \text{Boolean Expression}) = 1$
- $(\bar{L} \cdot M)$ is complement of $(L + \bar{M})$ & $(\bar{L} \cdot \bar{M})$ is complement of $(L + M)$
- The given expression is $1 \cdot (0 + 0) = 0$

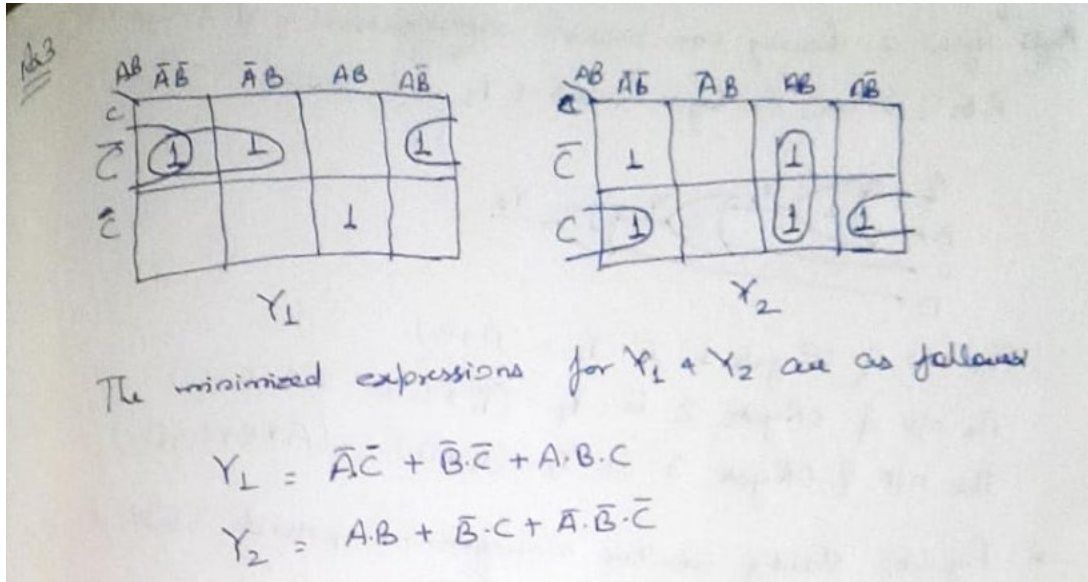3. Using Karnaugh maps, write the minimized Boolean expressions for the output functions of a two-output logic system whose outputs Y1 and Y2 are given by the following Boolean functions:

$$Y_1 = \bar{A}.B.\bar{C} + A.\bar{B}.\bar{C} + A.B.C + \bar{A}.\bar{B}.\bar{C}$$

$$Y_2 = \bar{A}.\bar{B}.C + A.B.\bar{C} + A.\bar{B}.C + A.B.C$$



4. For the half-adder circuit of Fig. 4(a), the inputs applied at A and B are as shown in Fig.4(b). Plot the corresponding SUM and CARRY outputs on the same scale.

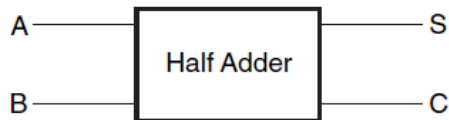


Fig. 4(a)


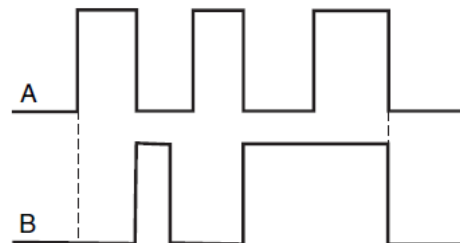


Fig. 4(b)

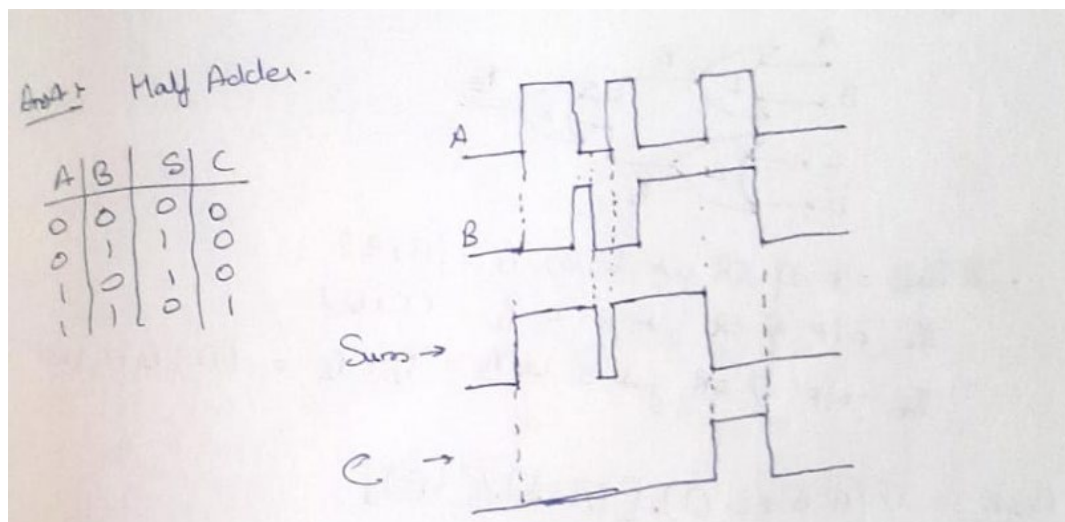

5. Write the simplified Boolean expressions for **DIFFERENCE** and **BORROW** outputs for the Fig. 5. (HA- Half adder; HS- Half Subtractor)

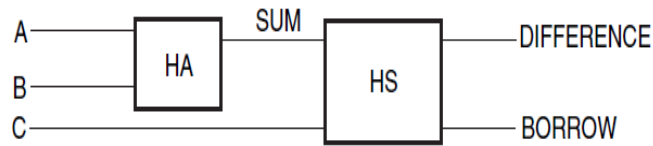


Fig.5

Let us assume that the two inputs to the half-subtractor circuit are X and Y , with X equal to the SUM output of the half-adder and Y equal to C . DIFFERENCE and BORROW outputs can then be expressed as follows:

$$\text{DIFFERENCE output} = X \oplus Y = \bar{X}.Y + X.\bar{Y} \quad \text{and} \quad \text{BORROW output} = \bar{X}.Y$$

Also, $X = \bar{A}.B + A.\bar{B}$ and $Y = C$.

Substituting the values of X and Y , we obtain

$$\begin{aligned} \text{DIFFERENCE output} &= (\bar{A}.B + A.\bar{B}).C + (\bar{A}.B + A.\bar{B}).\bar{C} = (A.B + \bar{A}.\bar{B}).C + (\bar{A}.B + A.\bar{B}).\bar{C} \\ &= A.B.C + \bar{A}.\bar{B}.C + \bar{A}.B.\bar{C} + A.\bar{B}.\bar{C} \end{aligned}$$

$$\text{BORROW output} = \bar{X}.Y = (\bar{A}.B + A.\bar{B}).C = (A.B + \bar{A}.\bar{B}).C = A.B.C + \bar{A}.\bar{B}.C$$

6. a) Make a truth table for the Boolean function $F = \bar{x}.\bar{y}.\bar{z} + \bar{x}.y.\bar{z} + x.y.\bar{z}$
 b) Simplify the above function to a minimum number of literals.
 c) Now use Karnaugh map to simplify F .
 d) Show implementation of F using NOT, OR and AND gates. What is the total count of gates?

6

x	y	z	f
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

$F = \bar{x}.\bar{z} + y.\bar{z}$

7. a) Minimize the following function using K-Map and write the minimized function in sum-of products form
 $F(A, B, C, D) = \sum(1, 2, 4, 5, 6, 9, 10, 14, 15)$
 b) Using K-map simplify the above function and expression it in product-of-sums form.

7a)

$F = ABC + \bar{A}\bar{B}\bar{C} + \bar{B}\bar{C}D + C\bar{D}$

b)

$\bar{F} = \bar{B}CD + \bar{A}CD + \bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}$

$F = (\bar{B}CD + \bar{A}CD + \bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C})$


$F = [(B + \bar{C} + \bar{D}) \cdot (A + \bar{C} + \bar{D}) \cdot (B + C + D) \cdot (\bar{A} + \bar{B} + C)]$

8. Minimize the following function using K-Map and write the minimized function in sum-of products form
 $F(A, B, C, D) = \sum(1, 3, 5, 9, 13) + d(0, 7, 10)$

$F = \bar{A}D + \bar{C}D$

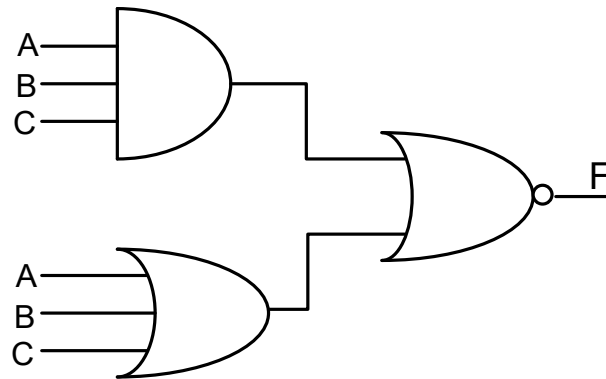
9. The logic diagram of the Boolean function is given below.

- Analyze the diagram and write its truth table
- Analyze the diagram and write the Boolean function in sum-of-product form.
- Implement the function using 4-to-1 line multiplexer.



$$\begin{aligned}
 i) \quad F &= \overline{(A \cdot B \cdot C) + (A + B + C)} = (\overline{A \cdot B \cdot C}) \cdot (\overline{A + B + C}) \\
 &= (\overline{A} + \overline{B} + \overline{C}) \cdot (\overline{A} \cdot \overline{B} \cdot \overline{C}) \\
 &= \overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot \overline{C} + \overline{A} \cdot \overline{B} \cdot \overline{C} \\
 &= \overline{A} \cdot \overline{B} \cdot \overline{C}
 \end{aligned}$$

A	B	C	F
0	0	0	1
0	0	1	0
0	1	0	0
0	1	1	0
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	0

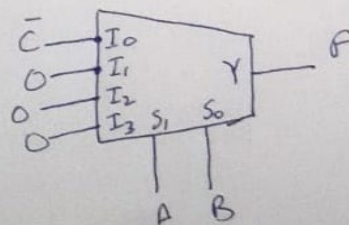



10. Design an X-NOR gate (i.e. $F(x, y) = \bar{x}\bar{y} + xy$) using only 2-input NOR gates. You are given only x and y inputs. You are allowed to use only a maximum of FIVE 2-input NOR gates. Draw a clear circuit diagram.

