

Introduction to Electrical Engineering

Course Code: EE 103

Department: Electrical Engineering

Instructor Name: B. G. Fernandes

E-mail id: bgf@ee.iitb.ac.in



Review:

DC-DC Conversion: Buck Converter

$L \rightarrow$ filter inductor

$C \rightarrow$ filter capacitor

' V_o ' is assumed to remain constant

Switch 'S' is switched at a **very high** frequency


- S is ON for DT second
- S is OFF for $(1 - D)T$ second

Average voltage across $L = 0$

$$\therefore (V_{DC} - V_o)DT = V_o(1 - D)T$$

$$\Rightarrow V_o = DV_{DC}$$

→ Buck Converter, Output < Input

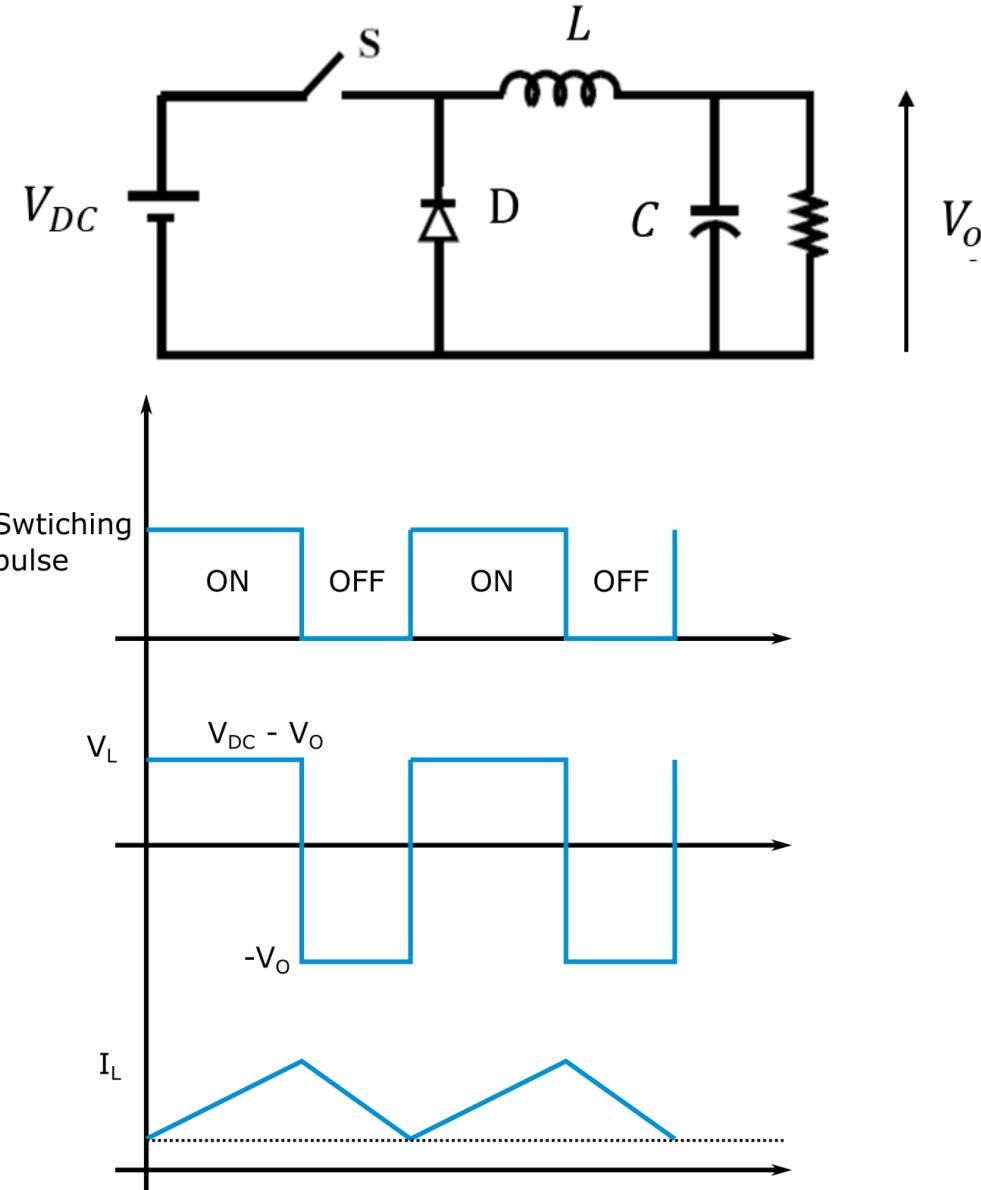

DC-DC Conversion: Boost Converter

Following circuit is a boost converter




$L \rightarrow$ filter inductor

$C \rightarrow$ filter capacitor


' V_o ' is constant and ripple free

Switch 'S' is switched at a very high frequency

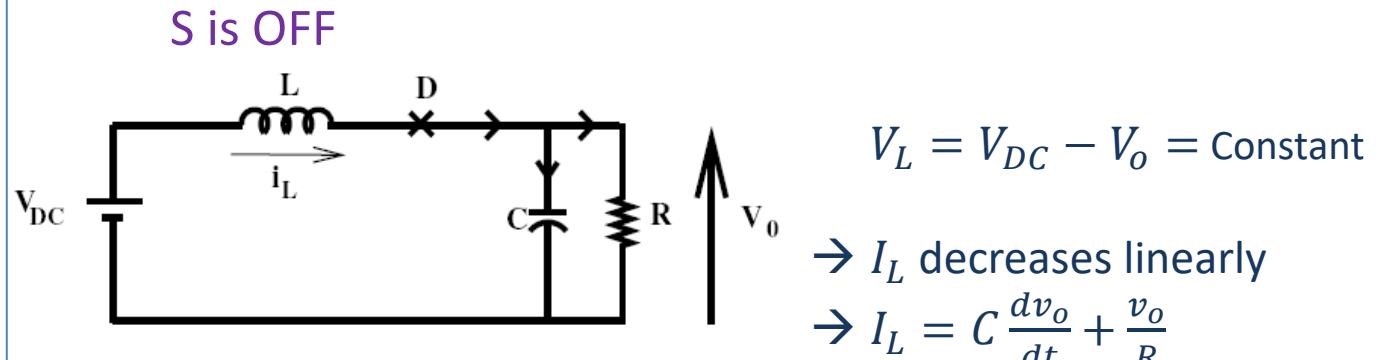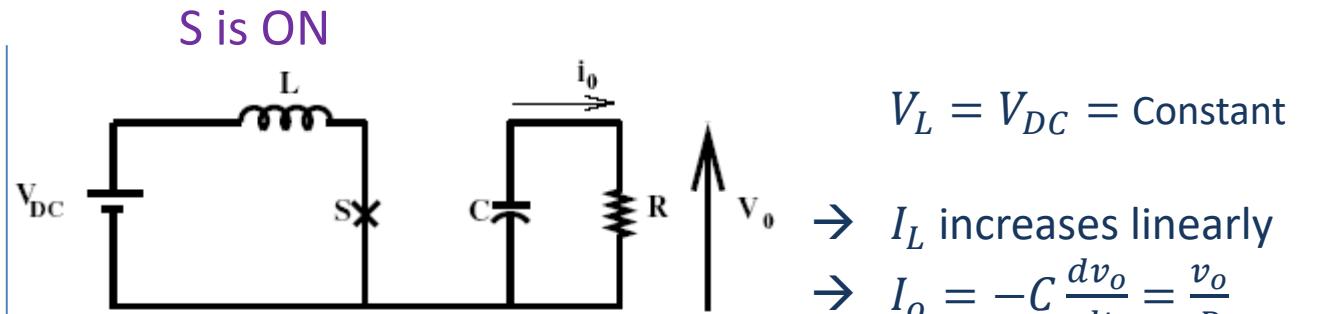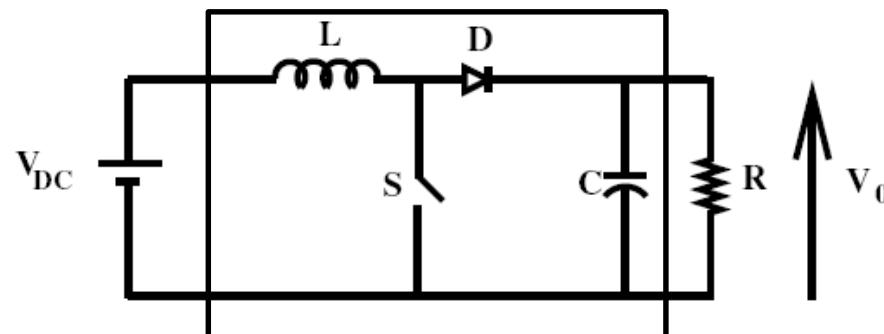- S is ON for DT time
- S is OFF for $(1 - D)T$ time
- T is switching period,
$$T = \frac{1}{f_{sw}}, f_{sw}$$
: switching frequency



DC-DC Conversion: Boost Converter

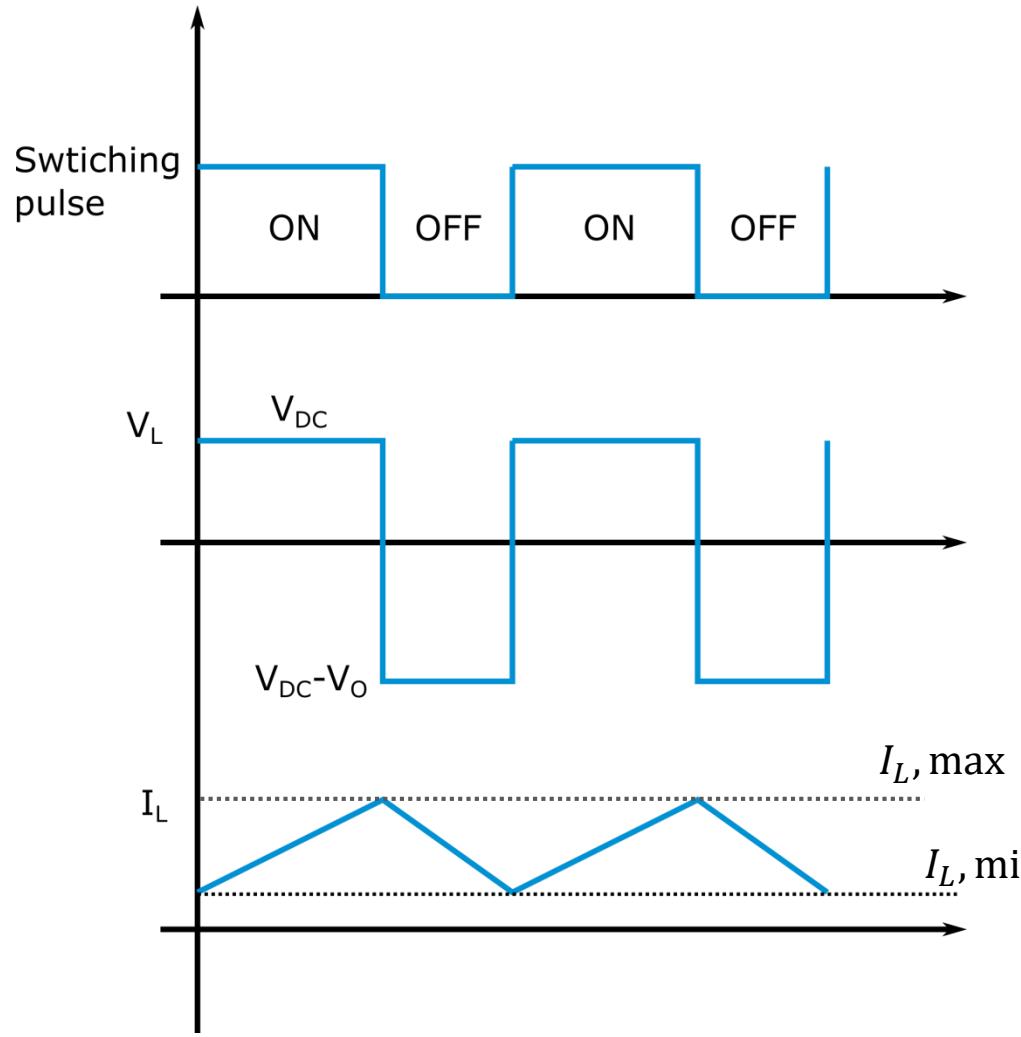

Assume i_L is continuous, and steady-state is assumed
Average voltage across L = 0

$$\therefore (V_{DC})DT + (V_{DC} - V_o)(1 - D)T = 0$$

$$\Rightarrow V_o = \frac{1}{1 - D} V_{DC}$$

→ Boost Converter, Output > Input

Precaution: Boost converter output should never be open circuited! (why??)




DC-DC Conversion: Buck-Boost Converter

This converter can be regarded as cascade connection of Buck and Boost converters

$L \rightarrow$ filter inductor

$C \rightarrow$ filter capacitor

' V_o ' is constant and ripple free

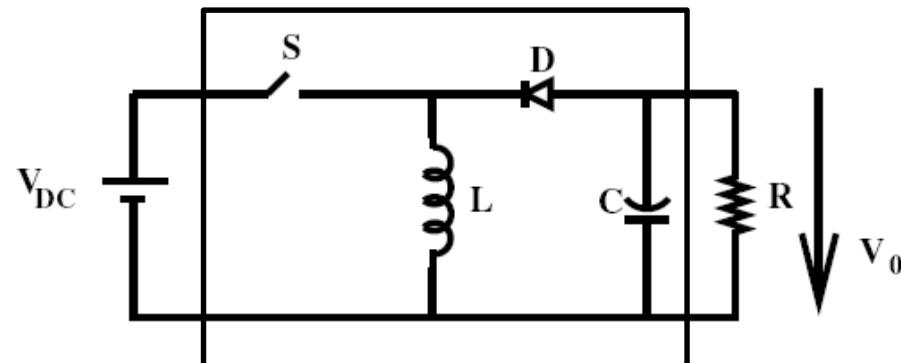

Assume i_L is continuous,

Average voltage across $L = 0$

$$\therefore (V_{DC})DT = V_o(1 - D)T$$



$$\Rightarrow V_o = \frac{D}{1 - D} V_{DC}$$



→ Output is **negative** w.r.t the common point

→ Output can be less than or more than the input depending on the value of D

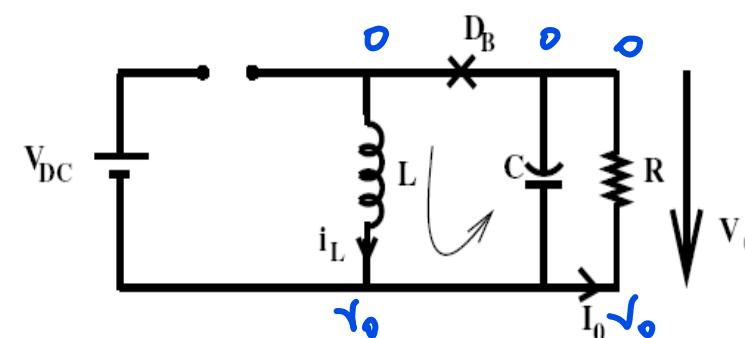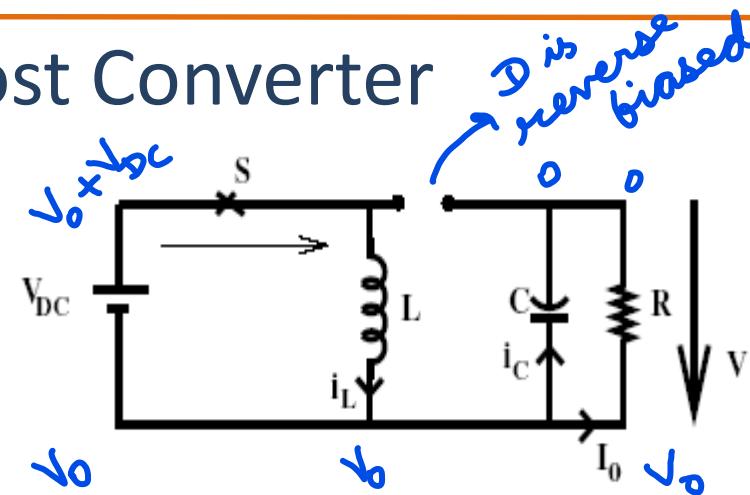→ Assignment: Sketch the waveforms of current through the inductor and voltage across it..



$$V_L = V_{DC} = \text{constant}$$

→ I_L increases linearly

$$\rightarrow C \frac{dv_o}{dt} + \frac{v_o}{R} = 0$$

$$V_L = -V_o = \text{constant}$$



→ I_L decreases linearly

$$\rightarrow I_L = C \frac{dv_o}{dt} + \frac{v_o}{R}$$




Important applications of DC-DC converters

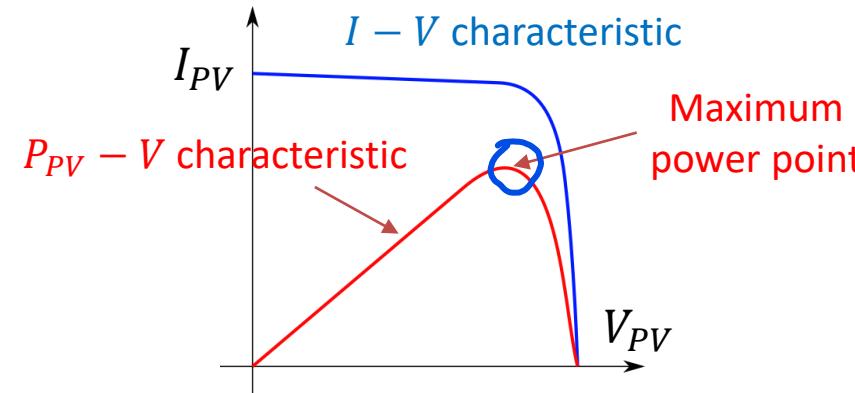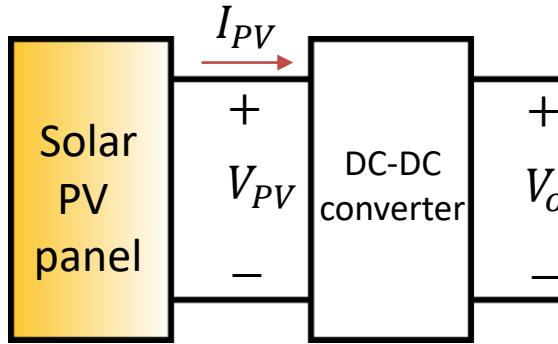- In solar energy harvesting for maximum power tracking



- This "maximum power point"(MPP) varies continuously depending on the environmental conditions
- The DC-DC converter ensures that the PV is operated at MPP

- Battery charging

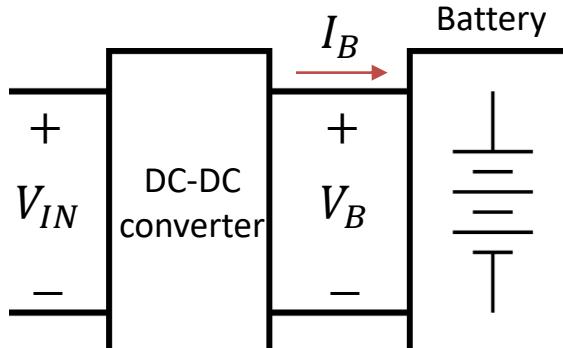

- Up to 85%, the battery is charged with constant current (CC)
- Beyond this level, it is charged with constant voltage (CV)
- This scheme of battery charging is termed as (CC-CV) charging
- A DC-DC converter is essential to perform such charging



DC – AC conversion



DC – AC conversion

Need for DC-AC conversion:

- Electric motor speed control
- Power source during grid failure
- Solar inverter
- Uninterruptible power supplies

Voltage source inverter (VSI)

Basic block: Half-bridge

In VSI, input is the voltage source and it is constant. The current through the VSI can reverse



So... are there other types of inverters??



Requirement of the switches used in VSI:

- It should block the reverse voltage across it
- It should allow the current to flow in both directions

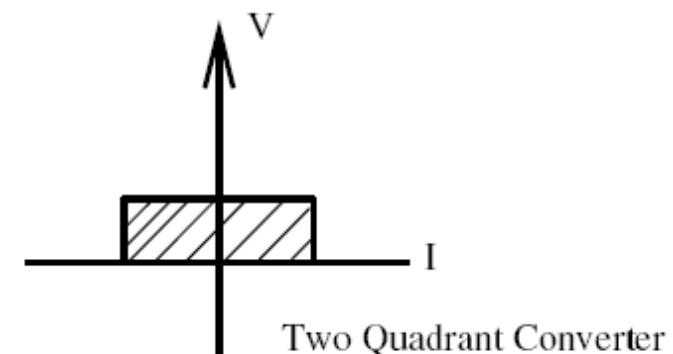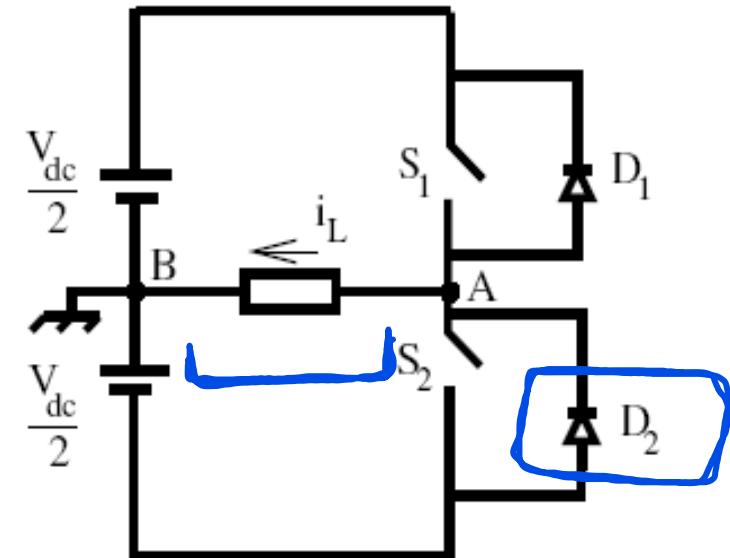→ Connect a diode in anti-parallel to a switch



DC – AC conversion: Half bridge

$$\tau = \frac{L}{R}$$

In VSI, switching signals S_1 and S_2 are always **complementary**

S_1 is ON \rightarrow for $\frac{T}{2}$ duration, $V_{AB} = \frac{V_{DC}}{2}$

If load is $R - L$, Current $i = \frac{V}{R}(1 - e^{-\frac{t}{\tau}})$



S_1 is OFF \rightarrow for $\frac{T}{2}$ duration, $V_{AB} = -\frac{V_{DC}}{2}$

Current, i will decay and become negative

Observations:

Time for which S_1/S_2 is ON will determine the frequency of V_{AB} ,
i.e. the output

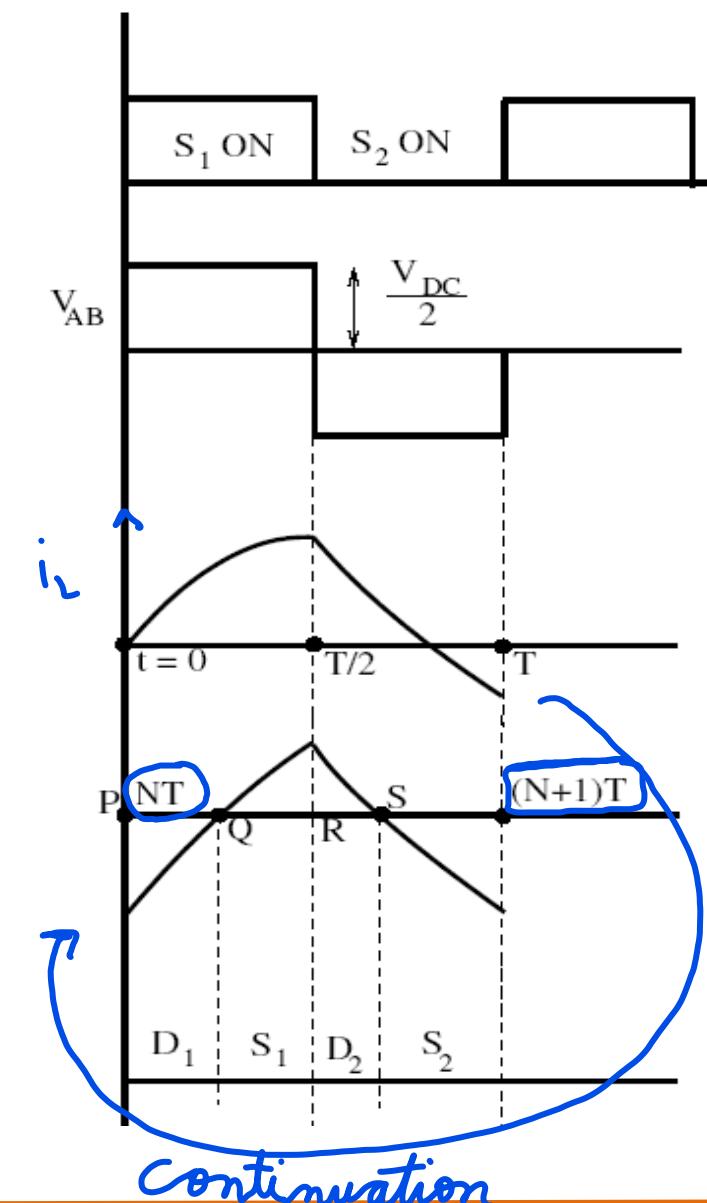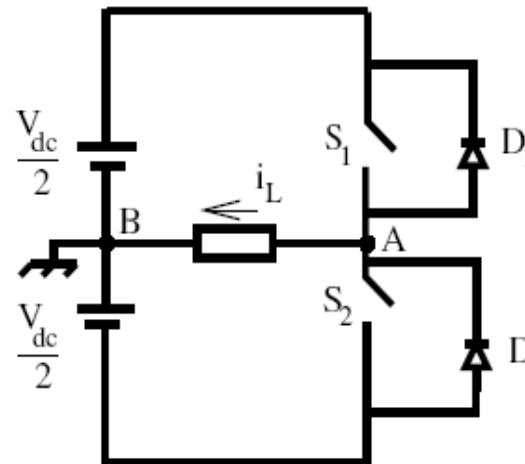\rightarrow If $\frac{T}{2} = 10$ ms, $f = 50$ Hz
 $= 100$ ms, $f = 5$ Hz



DC – AC conversion: Half bridge

At steady state,

During the duration P-Q: Voltage applied to the load is +ve

And i_L is -ve (i flowing from B to A)

→ Diode, D_1 is carrying i

In Q-R: 'V' and 'I' are +ve

S_1 is carrying 'I'



In R-S: 'V' is -ve and 'I' is +ve

D_2 is carrying 'I'

In S-T: 'V' and 'I' are -ve

S_2 is carrying 'I'

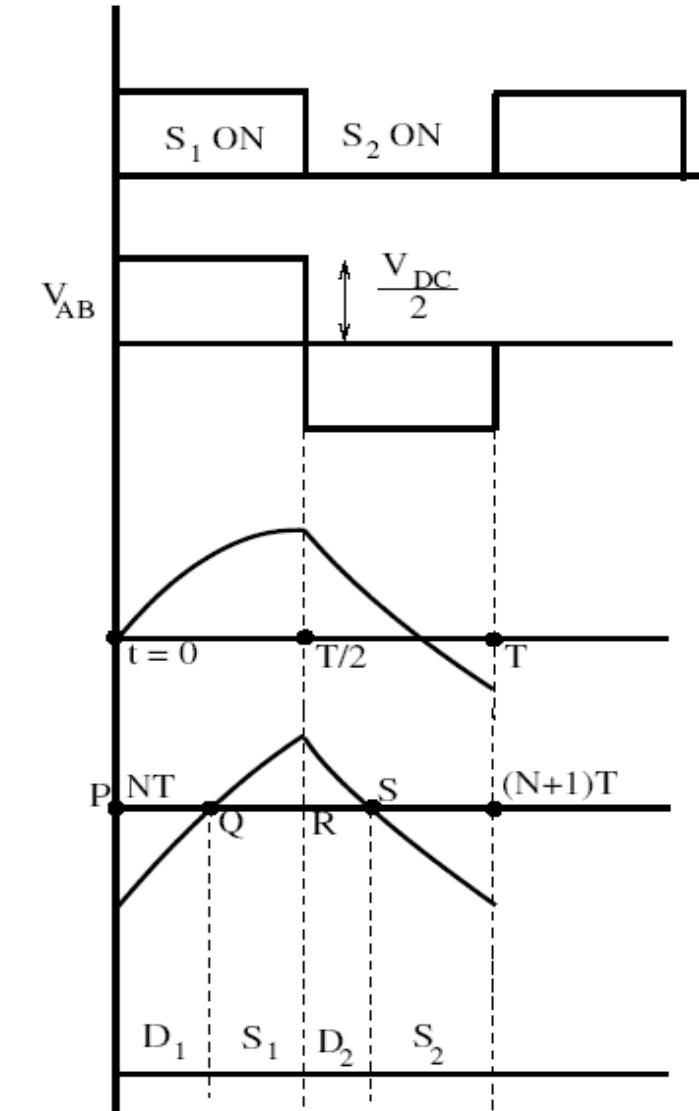
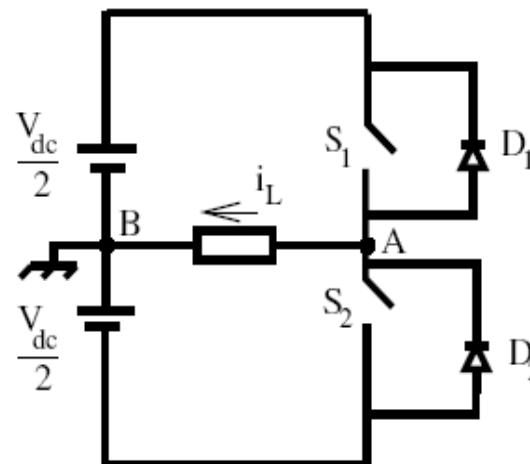
If load is purely resistive, is the diode required??



DC – AC conversion: Half bridge vs Full bridge



Limitations of Half Bridge

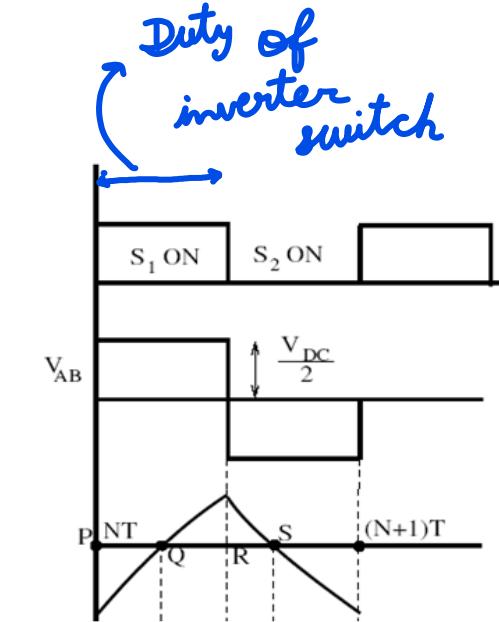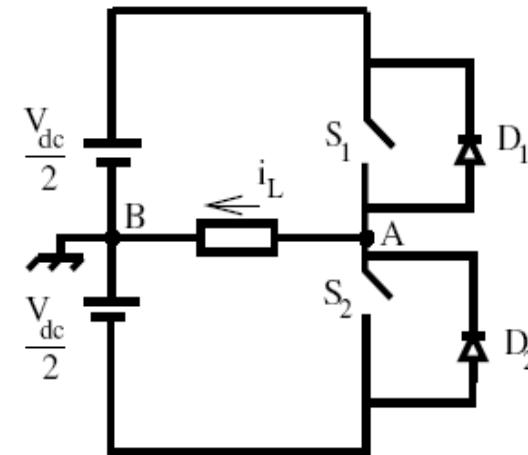- Input is V_{DC} , but Output is $\frac{V_{DC}}{2}$
- Requires the center point of the DC source




Instead, use a **Full Bridge**

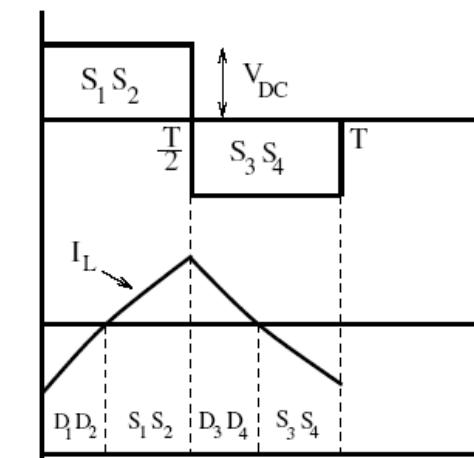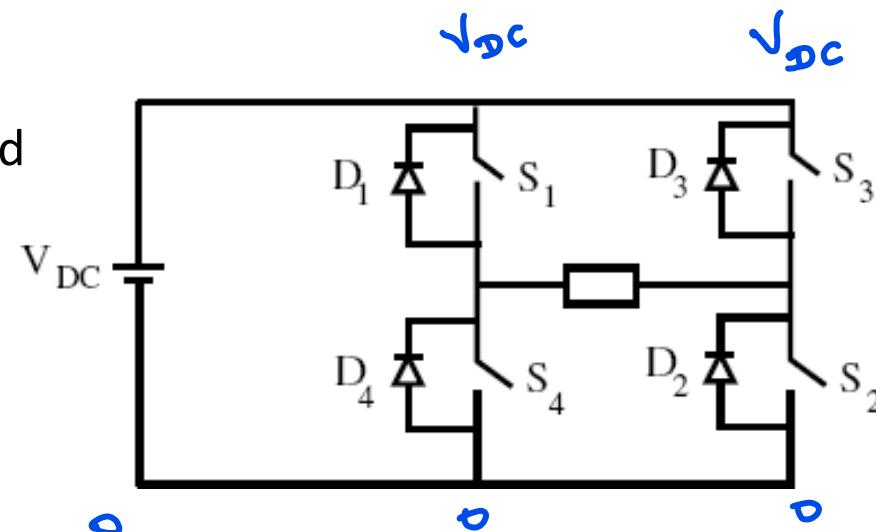- In Full bridge, two devices conduct at a time
- Center point of DC source is not required
- Input is V_{DC} , and Output is V_{DC}



DC-AC Conversion: Varying the Voltage



- Frequency variation can be obtained by changing the value of 'T', the time period
- How to vary the voltage value?
- A straight forward approach: Vary the input DC supply of the inverter (DC-AC Convertor) using a DC-DC converter
- In this method, the efficiency of the system is $\eta_{dc-dc} \times \eta_{dc-ac}$
- Also, the device count is high \rightarrow low reliability
- Here, the switches are allowed to conduct for 180° (50% of T)

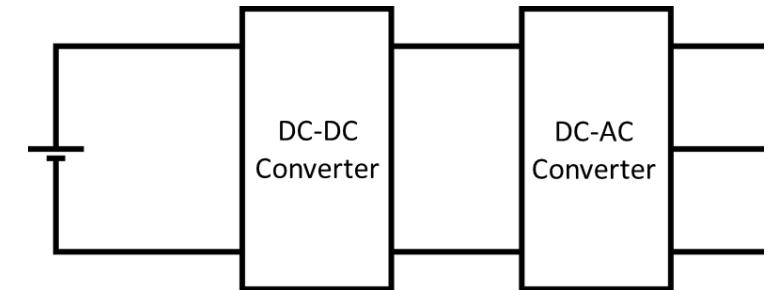


- Instead, keep the DC input to the inverter fixed and vary the duty of the inverter switches
- This scheme is known as Pulse Width Modulation (PWM)



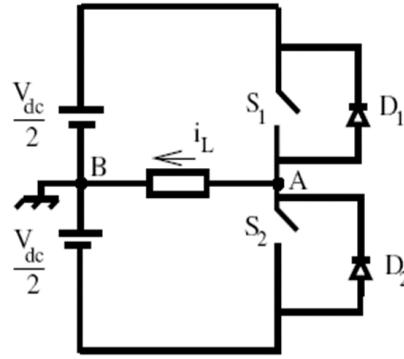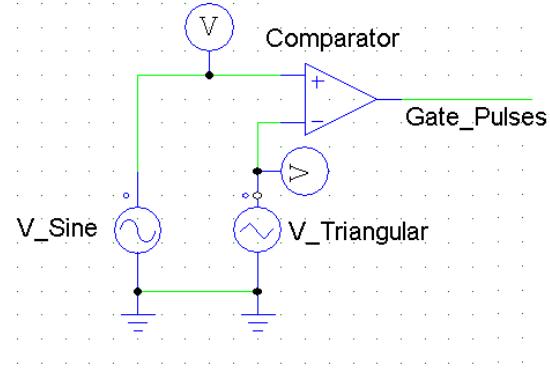Sine Pulse Width Modulation: Switch Gate Pulse Generation





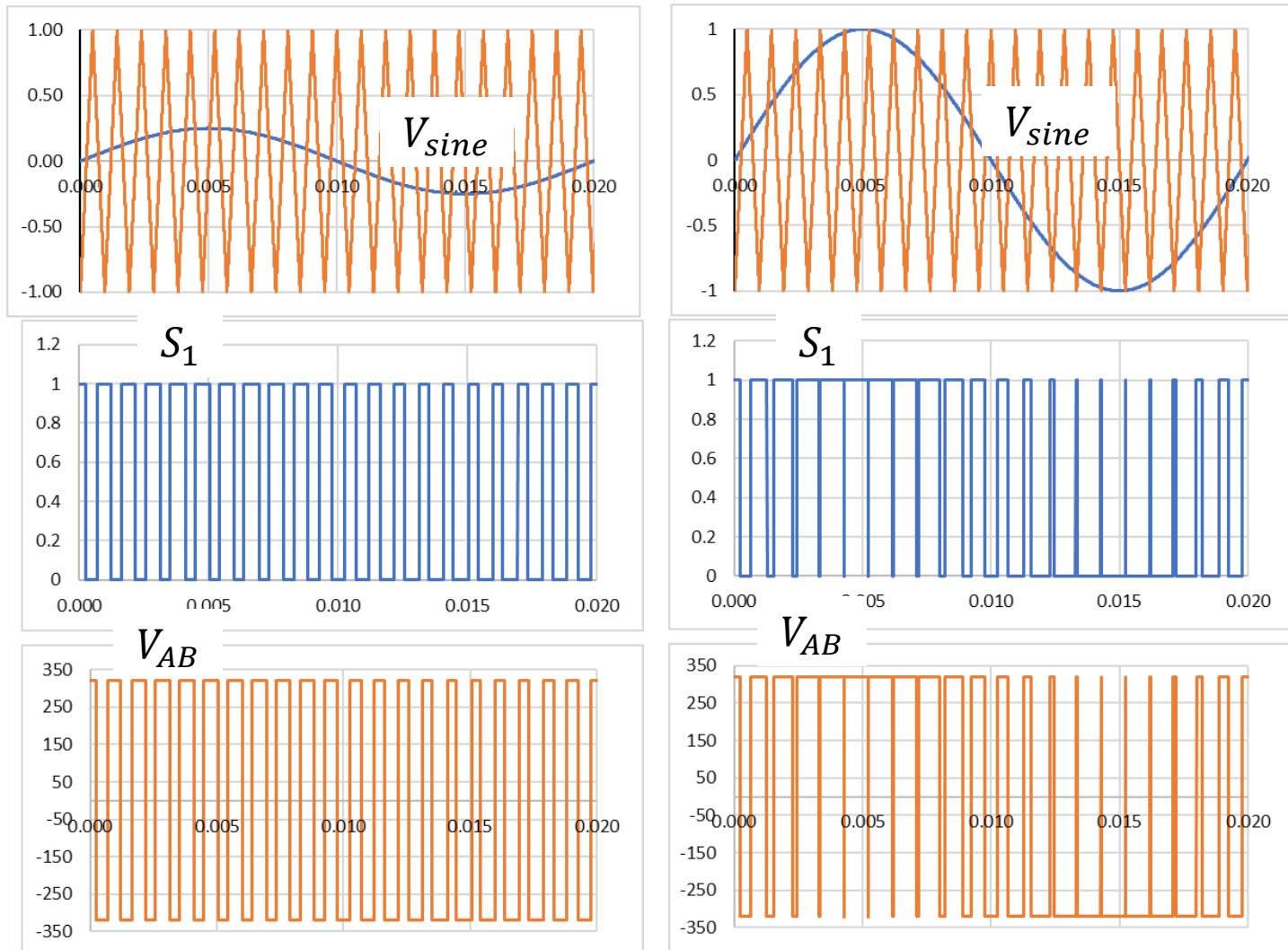
- A sinusoidal voltage (50 Hz) is compared with a triangular wave (High frequency)
- The obtained output is given as gate pulses to the corresponding switch





Sine Pulse Width Modulation

VSI feeding an $R - L$ load,
 $R = 10 \text{ ohm}$, $L = 50 \text{ mH}$,
 $f_s = 1050 \text{ Hz}$

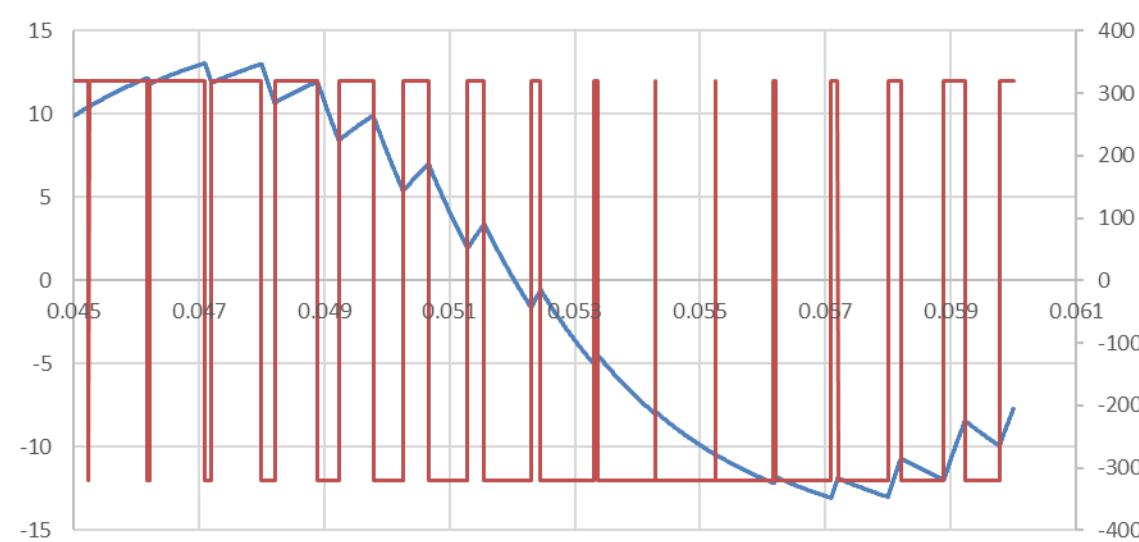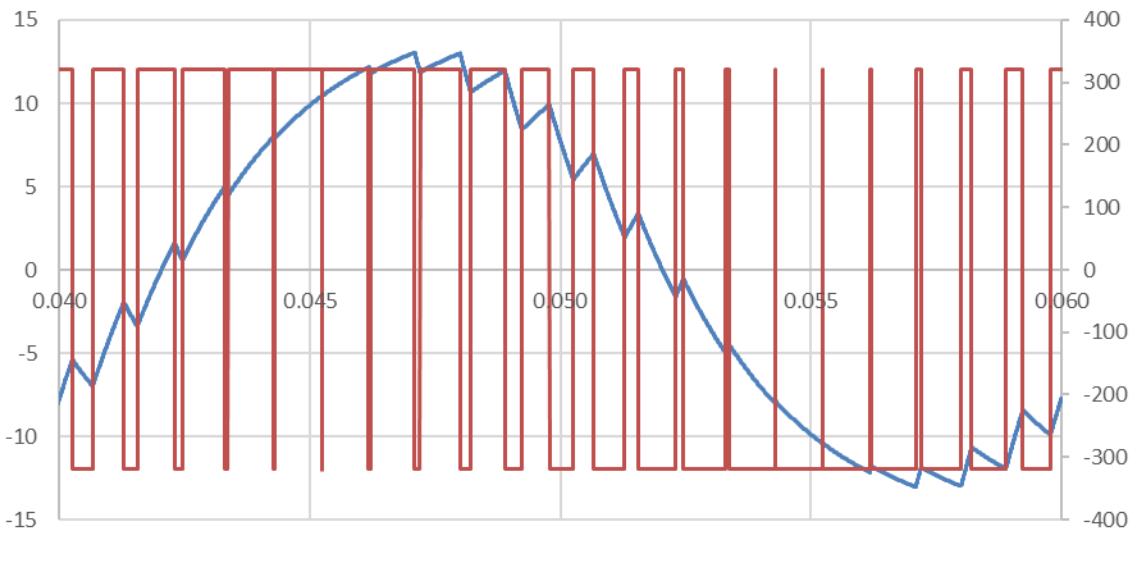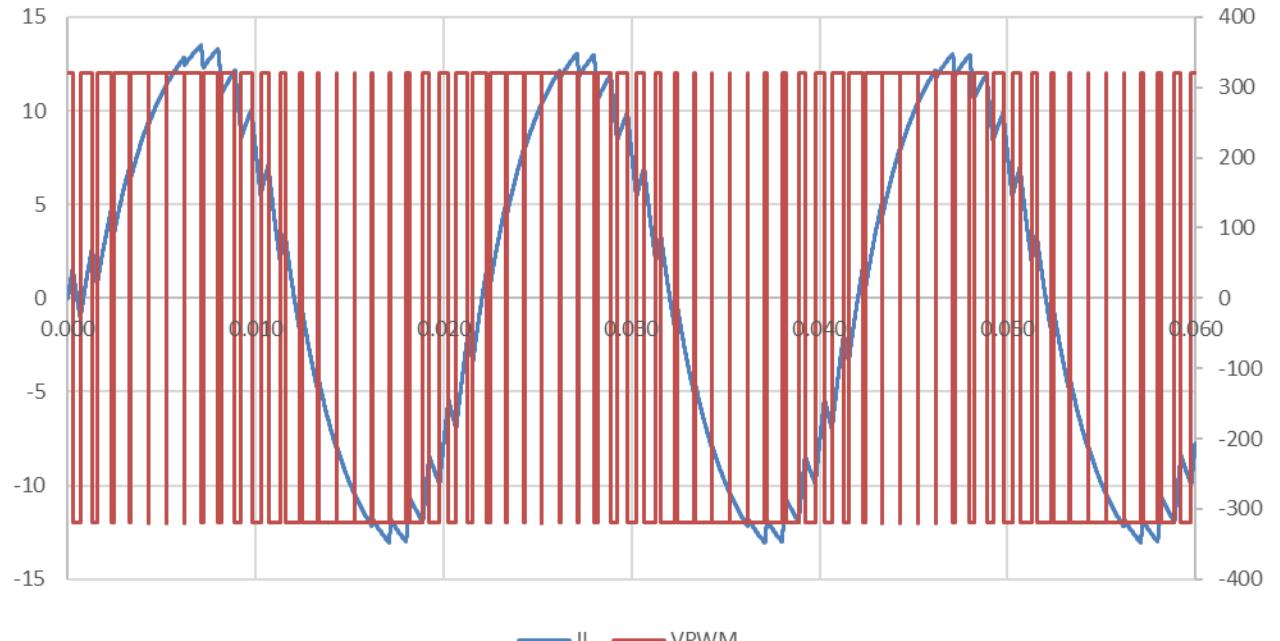→ It is possible to obtain
sinusoidal current waveform



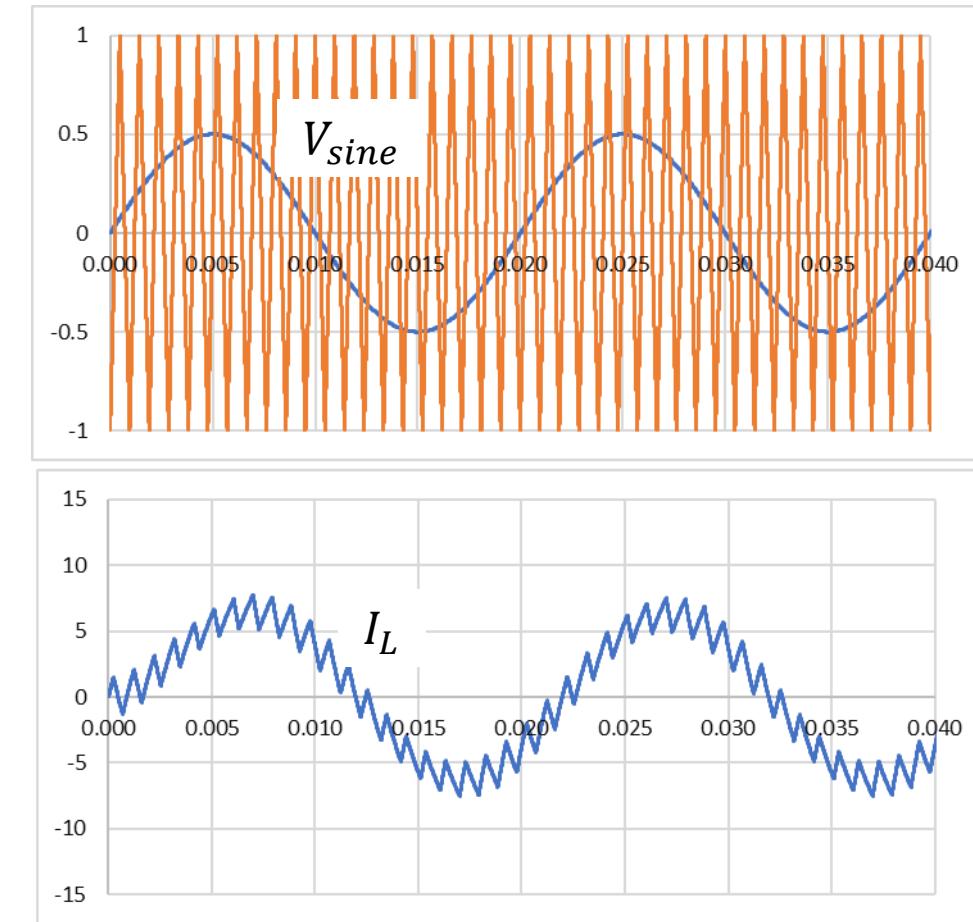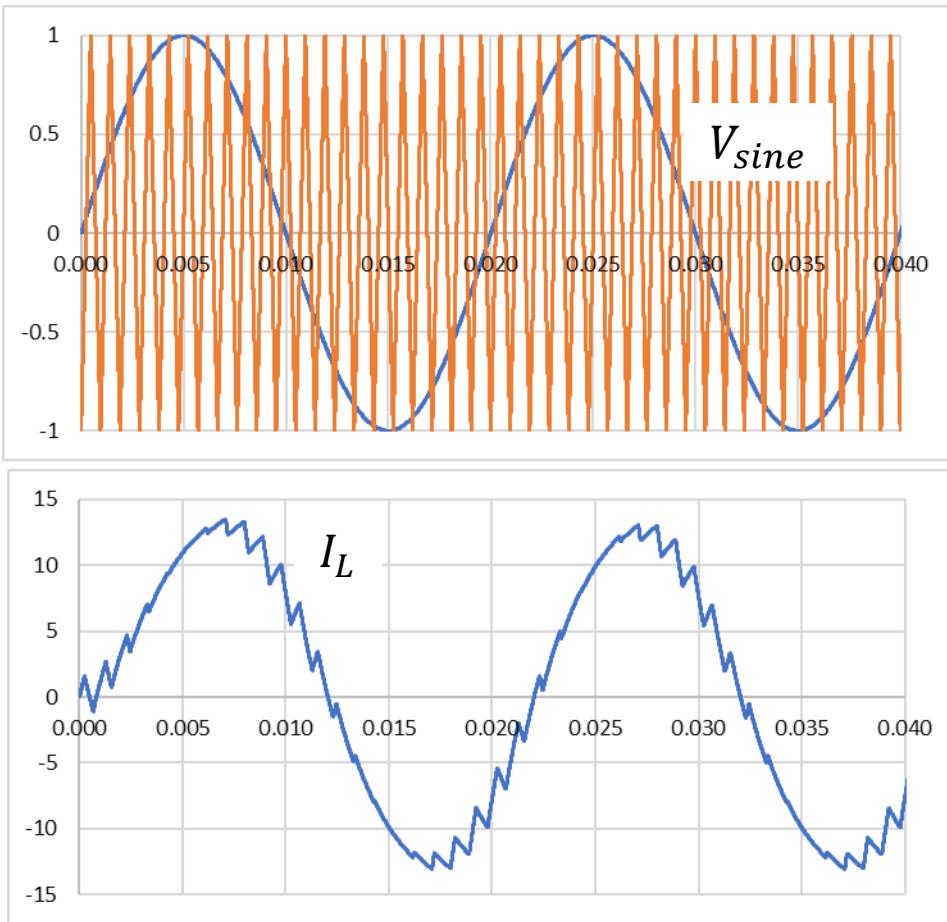Sine Pulse Width Modulation: Variation of Load current with reference sine



Electrical Grounding/Earthing

Ref: Prof. A. M. Kulkarni, EE334, Power Systems, Lecture: Safety, Three-phase neutral and earthing connections, Equipment classes, switches




Ground Path (Earthing)

- A ground is a return path for current
- A ground is also a point to which circuits may be ‘referenced’

Can ground be a regular current path?


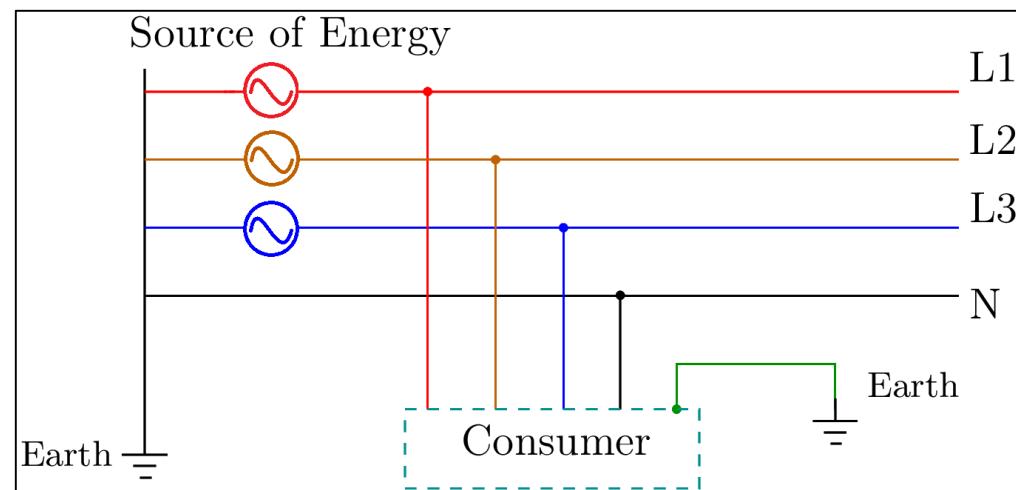
- Not generally used in practice
- For high voltage DC transmission, earth/sea are used as ground returns for short durations
- A few single-wire earth return systems are in existence
- Current can flow through ground during short-circuits



- A three-phase source can be viewed as three single-phase sources with one terminal common to all
- This common terminal is generally grounded to ‘Earth’
- There is a return path from the consumer...



Safety

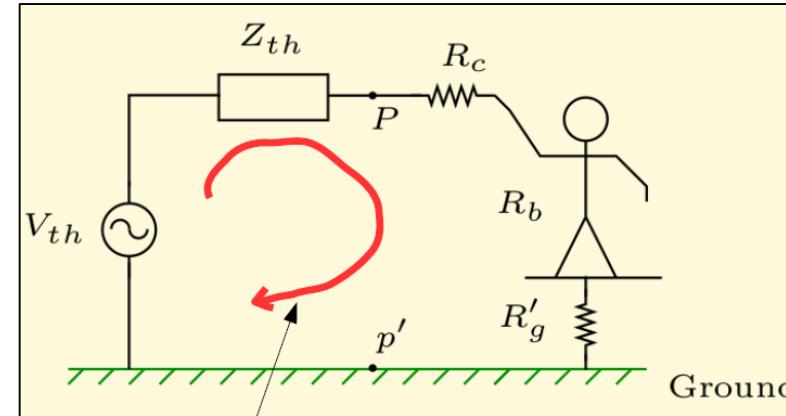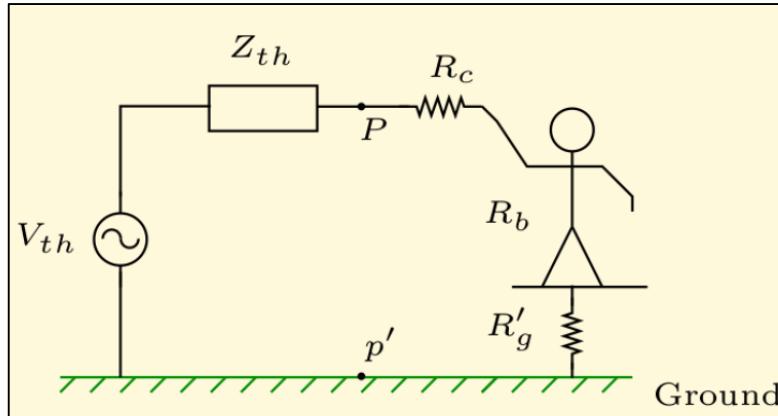

Z_{th} = Equivalent Impedance
 V_{th} = $V_{\text{open-circuit}}$ at P p'
 R_c = $R_{\text{contact}} \approx 500 \Omega$
 R_b = $R_{\text{body}} \approx 1000 \Omega$
 R'_g = $R_{\text{ground}} \approx 600 \Omega$

- The entire power system is represented using a 'Thevenin Equivalent' network between points P and p'
- Depending on the impedance of the path, current flows through the 'person'

Source: Walter Weeks, *Transmission and Distribution of Electrical Energy*, Harper & Row Publishers 1980.




Effects of various magnitude of current through a person

'Let go' current

Sr No.	Effect	Current (mA)			
		Direct Current		60 Hz rms	
		Men	Women	Men	Women
1.	No sensation on hand	1	0.6	0.4	0.3
2.	Slight tingling. Perception threshold	5.2	3.5	1.1	0.7
3.	Shock- not painful but muscular control not lost	9	6	1.8	1.2
4.	Painful shock- painful but muscular control not lost	62	41	9	6
5.	Painful shock- let go threshold	76	51	16.0	10.5
6.	Painful and severe shock, muscular contractions, breathing difficult	90	60	23	15
7.	Possible ventricular fibrillation from short shocks:				
(a)	Shock duration 0.03 s	1300	1300	1000	1000
(b)	Shock duration 3 s	500	500	100	100
(c)	Almost certain ventricular fibrillation (if shock duration is over one heart beat interval)	1375	1375	275	275

Threshold for 50% of males and females tested

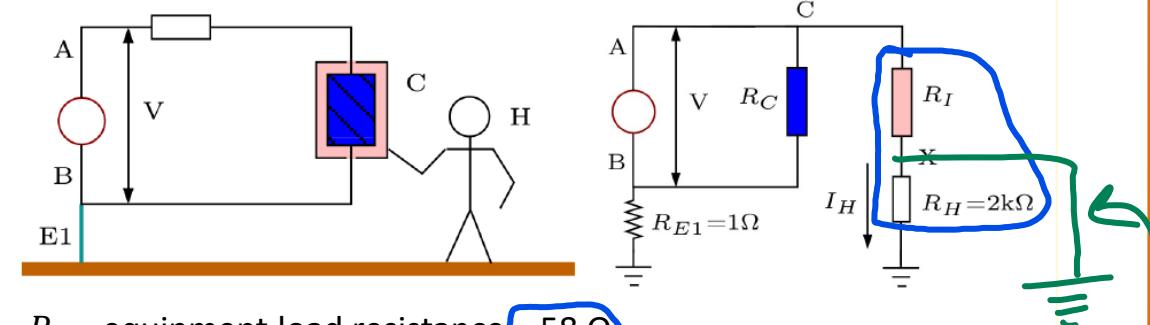Consider that the source is grounded and the equipment is not grounded




$$R_c = \text{equipment load resistance} = 58 \Omega$$

$$R_I = \text{equipment insulation resistance}$$

The current through the person during insulation failure ($R_I = 0 \Omega$)
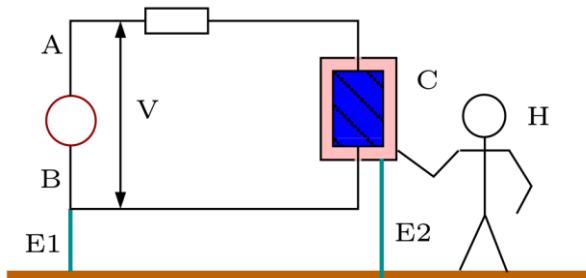
$$I_H = \frac{V}{R_H + R_{E1}} = \frac{240}{2000 + 1} \approx 120 \text{ mA}$$



Instead, if the equipment is grounded, the current will prefer the ground path since it offers low resistance



Some pictures of 'Earthing' in our department

